

## **MACHAKOS UNIVERSITY COLLEGE**

(A Constituent College of Kenyatta University)

**University Examinations for 2015/2016** 

#### SCHOOL OF ENGINEERING AND TECHNOLOGY

#### DEPARTMENT OF MECHANICAL AND MANUFACTURING ENGINEERING

# SECOND SEMESTER EXAMINATION FOR DIPLOMA IN AUTOMOTIVE ENGINEERING

#### **VEHICLE ELECTRIC AND ELECTRONICS 1**

Date: 1/8/2016 Time: 8.30-10.30 AM

#### **INSTRUCTIONS**

- This Examination contains two sections A and B. Section A is compulsory
- Attempt any other Two questions from section B.

#### **SECTION A (COMPULSORY) (30 MARKS)**

1. a) Explain how you would carry out the following on the car battery.

i. General service (5 marks)

ii. Determine the conditions of the electrolyte (5 marks)

iii. Using the high rate discharge tester to determine condition of the battery cell

(5 marks)

iv. Charging the battery using an external charger (5 marks)

b) Explain a procedure for dismantling, testing and assembling the DC motor (10 marks)

### **ANSWER ANY TWO QUESTIONS**

- 2. a) In taking light circuit working off a 12V battery has four lights connected in parallel with the following resistors 60V, 40V, 30V, and 20V. Calculate the total amount of current passing through (6 marks)
  - b) Sketch the indicator circuit and explain how current flows (14 marks)
- 3. a) Name five types of ignition systems. (5 marks)
  - b) Using a diagram explain the operation of the conventional ignition system (15 marks)
- 4. a) Sketch an electrical circuit showing how an ammeter and a voltmeter and connected to measure current and voltage (6 marks)
  - b) Sketch the headlamp circuit and explain how current flows through (14 marks)
- 5. a) By the use of sketches explain the meaning of dwell ample in ignition system (8 marks)
  - b) Explain the function of the following as applied in coil ignition system. Vacuum advance, centrifugal advance mechanisms, capacitor, Ballast resistor and induced E.m.f (12 marks)