



MACHAKOS UNIVERSITY

University Examinations for 2021/2022 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATIONS FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONIC ENGINEERING)

EEE 309: ANALOGUE ELECTRONICS II

DATE:


TIME:

INSTRUCTIONS

Answer question **ONE** and **ANY OTHER TWO** questions

QUESTION ONE (COMPULSORY) (30 MARKS)

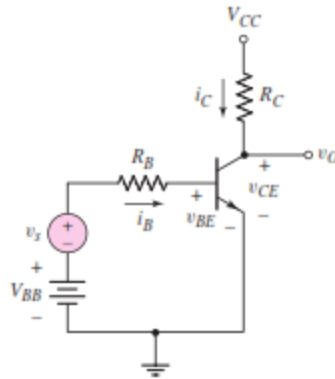- a) Describe how one can measure the following parameters of an op-amp:
- Differential gain;
 - Common mode gain.
- (6 marks)
- b) With inputs $v_{i1} = -50$ mV, and $v_{i2} = +50$ mV, a differential amplifier has output $v_o = 1.0043$ V. With inputs $v_{i1} = v_{i2} = 5$ V the output is $v_o = 0.4153$ V. Determine the CMRR, expressed in dB. (4 marks)
- c) The transistor amplifier in FigQ1 (c) has the following parameters: $V_{CC} = 10$ V, $R_C = 3$ k Ω , $R_B = 100$ k Ω , $V_{BB} = 3$ V, $\beta = 100$ and $r_o = \infty$. Determine the voltage gain $A_v = v_o/v_s$ by performing dc and ac analysis.




FigQ1 (c)

(12 marks)

- d) A series fed class-A amplifier shown in FigQ1 (d) operates from a dc source and an applied sinusoidal signal generates peak base current of 9 mA. Calculate
- i. Quiescent current I_{CQ} ;
 - ii. Quiescent voltage V_{CEQ} ;
 - iii. The efficiency of the amplifier.

Assume $\beta = 50$ and $V_{BE} = 0.7$ V

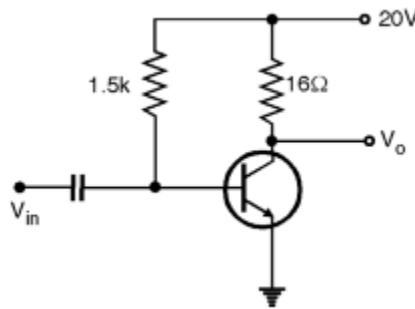

FigQ1 (d)

(8 marks)


QUESTION TWO (20 MARKS)

- a) i. An op-amp with an open-loop gain of $A_v = 7 \times 10^3$ is to be used in an inverting op-amp circuit. Let $R_1 = 10$ k Ω and $R_2 = 100$ k Ω . If the output voltage $v_o = 7$ V, determine the input voltage and the voltage at the inverting terminal of the op-amp.

- ii. If the output voltage $v_o = -5\text{ V}$ and the voltage at the inverting terminal of the op-amp is 0.2 mV , what is the input voltage and the value of A_v ?

(7 marks)

- b) For the circuit shown in FigQ2, find output voltage V_o .

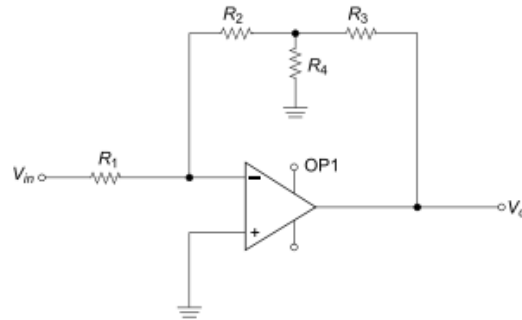

FigQ2


(13 marks)

QUESTION THREE (20 MARKS)

- a) i. Sketch the general characteristics of a low-pass filter, a high-pass filter, and a band-pass filter;
 ii. State the Barkhausen criterion for oscillations.

(7 marks)

- b) Derive the expression for the frequency of oscillation for the Hartley oscillator in FigQ3.

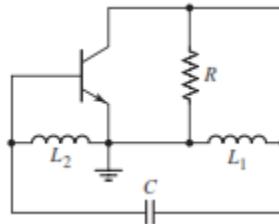


FigQ3

(13 marks)

QUESTION FOUR (20 MARKS)

- a) Consider a CE amplifier in FigQ4 (a) with $R_s = 1\text{ k}\Omega$, $R_1 = 50\text{ k}\Omega$, $R_2 = 2\text{ }\Omega$, $R_C = 1\text{ k}\Omega$, $R_L = 1.2\text{ k}\Omega$, $h_{ie} = 1.1\text{ k}\Omega$, $h_{oe} = 25\text{ }\mu\text{A/V}$ and $h_{re} = 2.5 \times 10^{-4}$. Determine

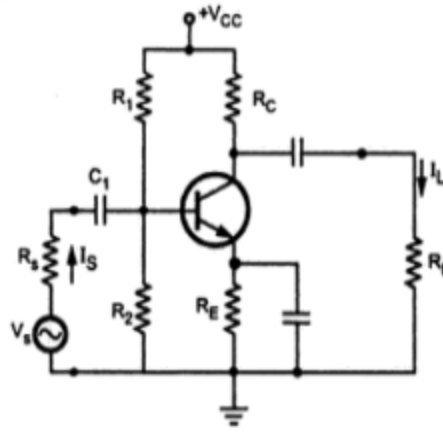- i. Current gain A_i ;
 ii. Input impedance Z_{in} ;
 iii. Voltage gain A_v
 iv. Overall input impedance Z_{in}'




FigQ4 (a)

(8 marks)

- b) The the circuit shown in FigQ4 (b), determine the small-signal
- voltage gain;
 - input resistance;
 - output resistance.

Assume the transistor parameters are: $\beta=100$, $V_{BE}(\text{on})=0.7\text{V}$, and $V_A=100\text{V}$.

(12 marks)

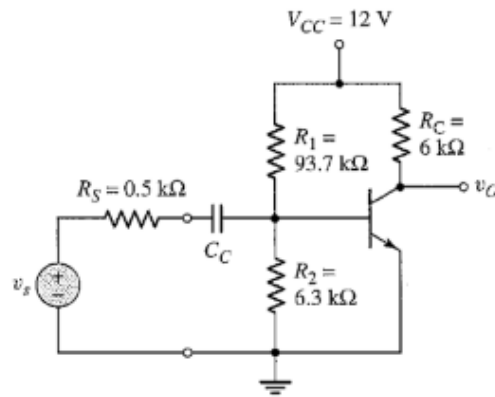

FigQ4 (b)

QUESTION FIVE (20 MARKS)

- (a) Determine the voltage gain, input, and output impedance with feedback for voltage-series feedback having $A = -100$, $R_i = 10\text{ k}\Omega$, and $R_o = 20\text{ k}\Omega$ for feedback of $\beta = 0.1$.

(6 marks)

- (b) i. Given that an amplifier has a bandwidth of 300 KHz and a voltage gain of 100 calculate the new bandwidth and gain when 10% negative feedback is introduced.

- ii. Determine the gain bandwidth product before and after feedback.
- iii. Calculate the amount of feedback if the bandwidth is limited to 800 KHz.

(8 marks)

(c) An amplifier with open loop voltage gain of 1000 delivers 10 W of power and output at 10% second harmonic distortion when the input is 10 mV. If 40dB negative feedback is applied and output power is to remain at 10 W, determine

- i. the required input signal V_s and
- ii. the second harmonic distortion with feedback.

(6 marks)