



MACHAKOS UNIVERSITY

University Examinations for 2022/2023 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR FIRST SEMESTER EXAMINATION FOR
BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)
EEE 305: DIGITAL ELECTRONICS I

DATE:

TIME:


INSTRUCTIONS

1. This paper contains 5 questions.
2. Attempt **Question One** and **Any Other Two** questions
3. Show calculations where applicable

QUESTION ONE (COMPULSORY) (30 MARKS)

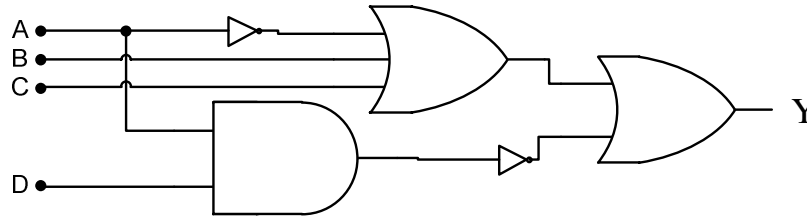- a) Perform the following operation using 9's complement subtraction: $52_{10} - 89_{10}$
(3 marks)
- b) Simplify the following expression using Boolean algebra laws and rules and implement the simplified expression using logic gates.
$$F = xy + xyz + xy\bar{z} + \bar{x}yz$$

(5 marks)
- c) A 4-bit binary number is applied to a circuit on four lines A, B, C, D. The circuit has a single output, F, which is true if the number is in the range three to twelve, inclusive.
 - (i) Draw a truth table to represent the problem
(3 marks)
 - (ii) Use the K-map to obtain a simplified expression for the function
(4 marks)
 - (iii) Construct a circuit to implement the simplified expression in (ii) above using NAND gate only.
(3 marks)
- d) Draw a circuit diagram and a truth table of a J-K flip-flop and explain its operation.
(6 marks)
- e) Write the Boolean expression for output Y for logic circuit shown in the figure below and draw its truth table.
(6 marks)



QUESTION TWO (20 MARKS)

- a) Simplify the following expression function using Quine-McCluskey method and implement the minimum expression using only NOR gates.

$$f(A, B, C, D) = \prod_M (2, 7, 8, 9, 10, 12) \quad (10 \text{ marks})$$

- b) Construct the logic circuits that can implement the Boolean expressions:

$$y = \overline{\overline{A\overline{B} + C \oplus D}} \overline{(A + \overline{B} + C)} \quad (4 \text{ marks})$$

- c) State and explain three advantages of a multiplexer. (3 marks)

- d) Convert 871.84375_{10} to its binary equivalent: (3 marks)

QUESTION THREE (20 MARKS)

- a) Design a full-subtractor and implement it using basic logic gates and an EX-OR gate. (11 marks)

- b) Use 1's complement to perform the following operation:

$$12\frac{1}{2}_{10} - 22\frac{3}{4}_{10} \quad (4 \text{ marks})$$

- c) Perform the following operations using BCD addition:

$$257_8 + AE_{16} + 10111011.11_2 \quad (5 \text{ marks})$$

QUESTION FOUR (20 MARKS)

- a) Using a truth table, K-map, and logic expressions, design a full adder. (7 marks)
 b) Minimize the Boolean function given below using a K-map and implement the minimized expression using logic gates. (7 marks)

$$f(A, B, C, D) = \sum_x (1, 2, 6, 7, 8, 13, 14, 15) + \sum_x (3, 5, 12)$$

- c) With the aid of logic symbols and truth tables, explain the operation of the following two-input gates.
 (i) NOR
 (ii) XOR (6 marks)

QUESTION FIVE (20 MARKS)

- a) Find the canonical sum of products (SOP) and product of sums (POS) form for the expression given below (6 marks)

$$f(A, B, C) = AB + \bar{A}\bar{B} + AC + \bar{A}\bar{C}$$

- b) Using appropriate truth table and Boolean expressions design and implement a 1:4 demultiplexer (7 marks)

- c) Prove the following identity using Boolean algebra and De Morgan's theorems:

$$AB + \overline{AC} + \overline{ABC}(AB + C) = 1 \quad (3 \text{ marks})$$

- d) Perform $22_{10} - 54_{10}$ using 10's complement method. (4 marks)