



MACHAKOS UNIVERSITY

University Examinations for 2019/2020 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST YEAR THIRD SECOND EXAMINATION

DIPLOMA IN ELECTRICAL AND ELECTRONIC ENGINEERING.

2601-105-EIT I : ELECTRICAL INSTALLATION TECHNOLOGY I.

DATE: 16/12/2020

TIME: 2:30 – 5:30 PM

INSTRUCTIONS TO CANDIDATES

Attempt any five questions of the following Eight questions.

1.
 - a) Explain the following terms with regard to electrical wiring circuits;
 - i) Insulation resistance
 - ii) Inspection . (4 marks)
 - b) State the following with regard to an electrical installation wiring circuit ;
 - i) Any two IEE Regulations requirement for IR testing .
 - ii) Any two reasons for carrying out polarity tests . (4 marks)
 - c) Define the following components of an electric bell circuit ;
 - i) A Sounder
 - ii) Indicator Board . (4 marks)
 - d)
 - i) Explain with a labeled diagram the operation of a continuous ringing type of electric bell. (6 marks)
 - ii) State any two advantages of an open – circuit alarm system . (2 marks)
2.
 - a) Define the term" wiring system". (3 marks)
 - b) Describe with the aid of a diagram the operation of an electromagnetic overload trip. (6 marks)

- c) Explain the following terms with regard to consumer circuits;
- i) Distribution Board
 - ii) Final sub – circuit. (4 marks)
- d) Show with the aid of wiring diagram a 3 – point control of three lamps by use of one intermediate switch and two 2 –way switches . (2 marks)
- e) State the following ;
- i) Any three essential features of a consumers intake point as required by the IEE regulations .
 - ii) Any two IEE regulation requirements of a domestic ring final circuit. (5 marks)
3. a) Define the following terms ;
- i) Earth – Continuity Conductor
 - ii) Consumer’s earth resistance . (4 marks)
- b) Explain with a labeled diagram the current operated earth leakage circuit breaker. (6 marks)
- c) Define the following terms with regard to measurements ;
- i) Instrument efficiency
 - ii) Accuracy . (4 marks)
- d) Explain with a labeled diagram the Air Friction damping method used in indicating instruments. (6 marks)
4. a) i) Define a ‘ fire – alarm system ’.
- ii) State any two sensing elements used as heat detectors in fire alarm systems. (4 marks)

- b) Show with a labeled diagram a closed - circuit fire alarm powered by a 24V d.c supply and is installed in a building divided into three sections to meet the following conditions ;
- i) One bell and two call points required in each section .This bell only rings in the respective section when there is fire .
 - ii) A main bell which rings whenever there is fire in any section.
 - iii) Any section that's on fire is shown through an indicator. (5 marks)
- c) State any three IEE regulations regarding bell transformers. (3 marks)
- d) Show with the aid of a labeled diagram the sequence of control equipment at the intake point of a two – wire consumer installation . (4 marks)
- e) State the following
- i) Any two factors to be considered when choosing a wiring system.
 - ii) Any two advantages of a non-metallic conduit wiring system. (4 marks)
5. a) With the aid of a labeled line diagram show a typical power supply system layout indicating standard voltages at every stage. (4 marks)
- b) i) A moving coil instrument with a resistance of 25Ω gives a f.s.d with a voltage of 25mV . The instrument is to be used with a series multiplier to extend its range to 10. Calculate the error caused by 10°C rise in temperature . (6 marks)
- ii) State any two advantages of an Open circuit fire -alarm system as compared to Closed circuit fire alarm system . (2 marks)
- c) Explain with the aid of a labeled diagram the insulation resistance test of conductors to earth for a complete 2 – wire installation . (8 marks)
6. a) A 240 V single – phase motor develops a full – load output of 4 KW at an efficiency of 84% and 0.75 power factor. It is supplied by means of a 2 – core copper cable 200 m long. The cross – sectional area of each conductor of the cable is 25 mm^2 .Calculate ;
- i) The voltage drop in the cable
 - ii) The power wasted in the cable.
- (Take resistivity of copper as $17.5\mu\Omega\text{mm}$). (5 marks)

- b) i) Three different wards in a hospital are provided with a call system .Draw a circuit diagram showing the electrical connections for the system comprising one main bell , reset point , battery and a three - way indicator board . 3mks
- ii) Explain with the aid of a diagram the operation of an open circuit fire alarm system used for two zones. . (7 marks)
- c) State the following ;
- i) Any two Disadvantages of a Hydro – electric power plant .
- ii) Any three Advantages of a Pumped storage hydro – electric plant. (5 marks)
7. a) i) Explain with the aid of a diagram the construction of a Permanent magnet moving coil instrument. (8 marks)
- ii) Define the National Grid system with regard to Kenya . (2 marks)
- b) Describe the following classes of Hydro – electric power plants;
- i) Run off river plants without pondage.
- ii) Low head plants. (4 marks)
- c) Explain the following types of tools used in Electrical workshops ;
- i) Bench Vice. (3 marks)
- ii) Hacksaw. (3 marks)
8. a) Describe the following types of joint methods
- i) Soldering
- ii) Welding (4 marks)
- b) Explain the procedure for making a Tee-twist joint with a single- core conductor. (5 marks)
- c) Define the following terms with regard to protection devices;
- i) Current Rating
- ii) Fusing Factor. (4 marks)
- d) State any three factors considered in the site selection for an Hydro – electric power plant . (3 marks)
- e) Explain the following civil engineering works of an hydro – electric power plant;
- i) Penstock.
- ii) Forebay. (4 marks)