



MACHAKOS UNIVERSITY COLLEGE

(A Constituent College of Kenyatta University)
University Examinations for 2015/2016 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**SECOND SEMESTER EXAMINATION FOR DIPLOMA IN ELECTRICAL AND
ELECTRONICS ENGINEERING**

EED 216: POWER ELECTRONICS

DATE: 8/8/2016

TIME: 2:00 – 4:00 PM

INSTRUCTION TO THE CANDIDATES

- 1. Question 1 Compulsory**
- 2. Do any other 2 questions**

QUESTION ONE (COMPULSORY) (30 MARKS)

- (a) Define the following electronic circuits
 - (i) Integrator
 - (ii) Differentiator (4 marks)
- (b) With an aid of labeled diagram (s) explain the operation of an integrator circuit (7 marks)
- (c) Describe a digital to analogue converter circuit. (10 marks)
- (d) With the aid of block diagrams explain how data is acquired in an electronic system. (9 marks)

QUESTION TWO (MARKS)

- a) Differentiate between digital analogue converters (8 marks)
- b) A voltage to time (A/D) converter is also referred as a feedback circuit. . With aid of block diagrams, explain it's operational. (10 marks)

- c) Explain the function of a frequency counter (2 marks)

QUESTION THREE (20 MARKS)

- a) Logic gates are widely used in analogue to digital converters, with aid of labeled diagrams show a complete conversion process. (7 marks)
- b) Explain how a digital signal is obtained from a voltage to frequency converter (8 marks)
- c) With the aid of a circuit diagrams, explain an inverter as applied in engineering work. (5 marks)

QUESTION FOUR (20 MARKS)

- a) Describe the operation of a thyristor device (10 marks)
- b) Mention any two applications of thyristors. (2 marks)
- c) An oscillator is an electronic device which uses negative feedback with any aid of diagrams explain how it produces output. (8 marks)

QUESTION FIVE (20 MARKS)

- a) State TWO applications of cyclo – converters in DC motor drives. (2 marks)
- b) Describe a cyclo converter (15 marks)
- c) A unipolar junction transistor (UJT) oscillator has the following values
 $R_E = 10K$, $\eta = 0.75$. If the required oscillator frequency is 1KHZ. Find the value of capacitor C given the value of the constant $K = 1.4$ (3 marks)