



MACHAKOS UNIVERSITY

University Examinations for 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR BACHELOR OF SCIENCE
IN ELECTRICAL AND ELECTRONICS ENGINEERING

EEE 209: ELECTRICAL ENGINEERING

DATE:16/6/2017

TIME: 8.30-10.30 AM

INSTRUCTIONS

1. This paper has **FIVE** questions.
2. Attempt Question **ONE (compulsory)** and any other **TWO** questions.
3. All workings must be clearly shown.

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Enumerate the various parts of a dc generator explaining the purpose of each part
(6 marks)
- b) Derive the mathematical relationship between the secondary line voltage and the primary line voltage for the following three-phase transformer connections.
 - i) Star-Star connection
 - ii) Delta-Delta connection
 - iii) Delta-Star connection
 - iv) Star-Delta connection [8 marks]
- c) State two advantages and two disadvantages of the three-phase induction motor. [4 marks]
- d) State the characteristics of the various types of dc motors hence give two application areas for

- each type. **[6 marks]**
- e) A 12 pole, 50 Hz, 11 kV, three-phase induction motor delivers 250 kW at a slip of 2.5% and a power factor of 0.86 lagging. If the rotational losses are 2.5 kW and the motor efficiency is 95.6%, determine:
- i) the rotor copper loss
 - ii) the stator losses
 - iii) the input line current
- [6 marks]**

QUESTION TWO (20 MARKS)

- a) In a 120 V compound dc generator, the resistances of the armature, shunt and series windings are 0.06, 20 and 0.04 respectively. The load takes 84 A at 120 V. Find the armature current, the induced e.m.f., and the machine efficiency when the machine is connected as:
- i) long-shunt
 - ii) short shunt

Neglect the brush contact drop and ignore the armature reaction. **(8 marks)**

- b) Explain how excitation is achieved in self-excited dc generators **2 marks]**
- c) The following data refers to a 2000/120 V single-phase transformer:

primary resistance = 1.6Ω	secondary resistance = 0.006Ω
primary reactance = 4.72Ω	secondary reactance = 0.022Ω
core loss resistance = $85\text{ k}\Omega$	magnetizing inductance = $15.2\text{ k}\Omega$

The transformer secondary supplies a 120V, 4.5 kW load at a power factor of 0.85 lag. Using the exact transformer equivalent circuit, determine:

- i) the primary applied voltage
- ii) the voltage regulation
- iii) the primary power factor
- iv) the transformer efficiency

[10 marks]

QUESTION THREE (20 MARKS)

- a) The transformer is probably one of the most useful electrical devices ever invented. Give

reasons to support this statement. **[4 marks]**

- b) Briefly explain why the Δ - Δ connection of three-phase transformers is far more common than the Y-Y connection. **[3 marks]**
- c) An induction motor may be considered to be a transformer with a rotating short circuited secondary. Despite the similarities, there are a number of fundamental differences. Enumerate these differences. **[5 marks]**
- d) A 200 V dc series motor takes 5 A at no-load when running at 2500 rpm. The armature and field resistances are 0.4 and 0.8 respectively. If the input power at full load is 5 kW, calculate:
- i) the full load speed.
 - ii) the full load torque in N-m.
 - iii) the motor efficiency. **(8 marks)**

QUESTION FOUR (20 MARKS)

- a) What is the significance of back e.m.f. in a dc motor? A dc motor connected to a 400V supply has an armature resistance of 0.12Ω . Calculate:
- i) the value of the back e.m.f. when the armature current is 120 A
 - ii) the value of armature current when the back e.m.f. is 380.8 V **(4 marks)**
- b) A 280 V dc shunt motor has an armature current of 20 A when running at 1200 rpm against a full load torque. The armature resistance is 0.8Ω . Assuming that the flux remains constant and neglecting brush contact drop, calculate:
- i) the resistance that must be inserted in series with the armature to reduce the speed to 800 rpm at the same torque and
 - ii) the speed of the motor if the load torque is halved with the resistance calculated in part (i) in the circuit. **(6 marks)**
- c) A 6-pole, 400-V, 50-Hz, three-phase induction motor has a delta connected stator and a star connected slip-ring rotor with a stator phase voltage-to-rotor phase voltage transformation ratio of 5.2. The rotor resistance and standstill leakage reactance are 0.05Ω and 0.3Ω per phase respectively. Neglecting the stator impedance and magnetizing currents, determine:
- i) the rotor current and power factor at start with slip-rings shorted
 - ii) the rotor current and power factor when running at 960 rpm with slip-rings shorted
 - iii) the external rotor resistance per phase required to obtain a starting current of 20 A in the stator supply lines. How much power is wasted in the starting resistance? **(10 marks)**

QUESTION FIVE (20 MARKS)

- a) Clearly explain the principle of operation of a dc motor. (7 marks)
- b) A three-phase induction motor runs at almost 998 rpm at no load and 912 rpm at full load when supplied from a 50-Hz, three-phase source.
- i) How many poles does this motor have?
 - ii) What is the slip in percent at full load?
 - iii) What is the frequency of the rotor currents at full load?
 - iv) What is the speed of the stator field with respect to the rotor? With respect to the stator? (8 marks)
- c) Explain the difference between a squirrel-cage and a slip-ring three-phase induction motor.
- Which of the two is more widely used and give reasons why. (5 marks)