



MACHAKOS UNIVERSITY

University Examinations 2019/2020 Academic year

SCHOOL OF PURE AND APPLIED SCIENCES

DEPARTMENT OF PHYSICAL SCIENCES

SECOND YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE APPLIED PHYSICS AND TECHNOLOGY

SPH 208: ELECTRICAL CIRCUITS

DATE: 6/12/2019

TIME: 2.00-4.00 PM

INSTRUCTIONS TO CANDIDATES

1. Answer question No 1 and any other two questions.
2. Question No 1 carries 30 marks while the other two carry 20 marks each.
3. Read the instructions on the booklet keenly and adhere to them.

QUESTION ONE (30 MARKS)

- a) Give the polar form of a voltage which is expressed in rectangular form as $V = (5 + j12)$ volts (2 marks)
- b) Determine the charge that enters an element by time t when $i = 8t^2 - 4t$, $t \geq 0$. Assume $q(t) = 0$ for $t < 0$ (2 marks)
- c) Give two differences between series and parallel reactance in RLC circuits (2 marks)
- d) When a voltage of $12e^{-8t}$ V was connected across the element in Figure 1 a current of $5e^{-8t}$ A flowed for $t \geq 0$. Both $V(t)$ and $i(t)$ are zero at $t < 0$. Find the energy supplied by the element over the first 100 ms. (3 marks)


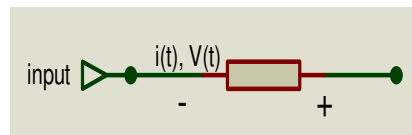



Fig 1

- e) Distinguish between independent and dependent sources (2 marks)
- f) A voltage source $V(t) = 10 \cos t$ V is connected across a resistor of 10Ω . Find the power delivered to the resistor (2 marks)

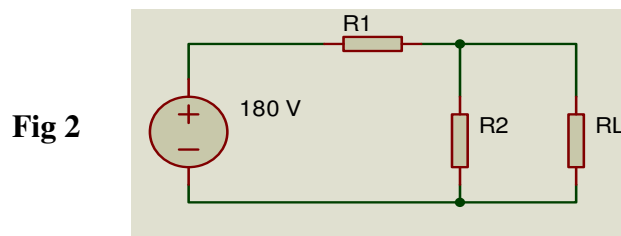- g) Show that the voltage V_n across the n^{th} resistor in a series of resistors connected in series to a voltage source V_s is given by $V_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} V_s$ (3 marks)
- h) i) State the Ampere's circuital law (1 mark)
- ii) Compute the magnetic field of a long straight wire that has a circular loop with a radius of 0.05m carrying a current of 2A. ($\mu_o = 4\pi \times 10^{-7} \text{ H/m}$) (3 marks)
- i) i) State the maximum power transfer theorem in electrical networks (1 mark)
- ii) Given that $R_1 = 150 \Omega$ and $R_2 = 30 \Omega$, find the load resistor R_L that will result into maximum power delivery to the load for the circuit in Figure 2. Hence determine the maximum power (4 marks)



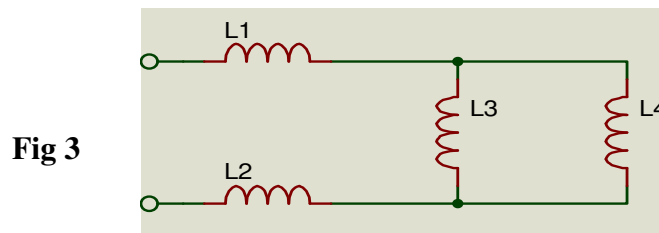- j) The circuit in figure 3 has inductors $L_1 = 2\text{mH}$, $L_2 = 3\text{mH}$, $L_3 = 5\text{mH}$, and $L_4 = 20 \text{ mH}$. Determine the equivalent inductance in the circuit (2 marks)




- k) i) Sketch the magnetization curve of a magnetic material (1 mark)
- ii) A loop having a cross sectional area of 500 mm^2 , circumference of 400 mm and $\Phi = 800 \mu\text{Wb}$ has a coil of 200 turns wound around it. Relative permeability of the ring μ_r is 380. Calculate the magnetic current ($\mu_o = 4\pi \times 10^{-7} \text{ H/m}$) (3 marks)

QUESTION TWO (20 MARKS)


- a) Give circuit descriptions of the wye - delta network transformations and write the equations that relate the two (4 marks)
- b) Using the delta to wye network conversion, find the equivalent resistance in Figure 4 given that $R_1 = 6\Omega$, $R_2 = 10\Omega$, $R_3 = 4\Omega$, $R_4 = 4\Omega$, $R_5 = 6\Omega$ (5 marks)

Fig 4

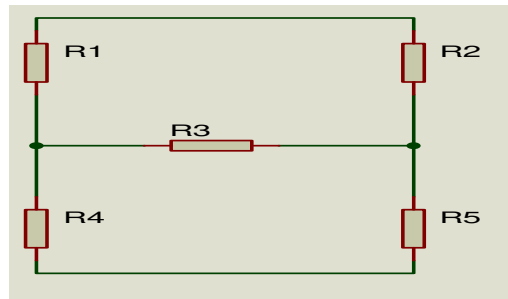

- c) State and prove the reciprocity theorem using the circuit in Figure 5 . $R_1 = 5\Omega$, $R_2 = 7\Omega$ and $R_3 = 6\Omega$ (5 marks)

Fig 5

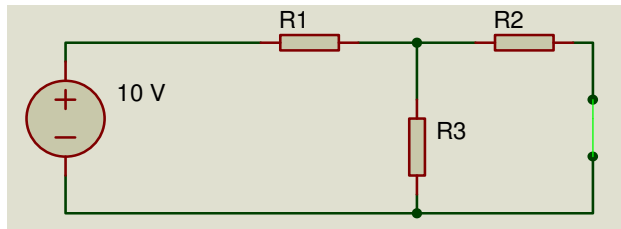


- d) An AC series circuit consists of a resistor with resistance of 90Ω , a coil with inductance of 1.3 H and a capacitor with capacitance of $10\text{ }\mu\text{F}$. The circuit is connected to an AC voltage source with amplitude of 100 V and frequency of 50 Hz . Write the equations for instantaneous values of voltage and current in the circuit if the initial phase of the current is zero (6 marks)

QUESTION THREE (20 MARKS)

- a) Describe the four types of dependent sources showing how the gain and the voltage or current through an element can be determined (6 marks)
- b) i) What is a capacitor (1 mark)
- ii) Using figure 6 find the equivalent capacitance and voltage V_s when $C_1 = C_2 = C_3 = 2\text{mF}$, $V_1(0) = 10\text{ V}$, $V_2(0) = V_3(0) = 20\text{ V}$. (4 marks)


Fig 6

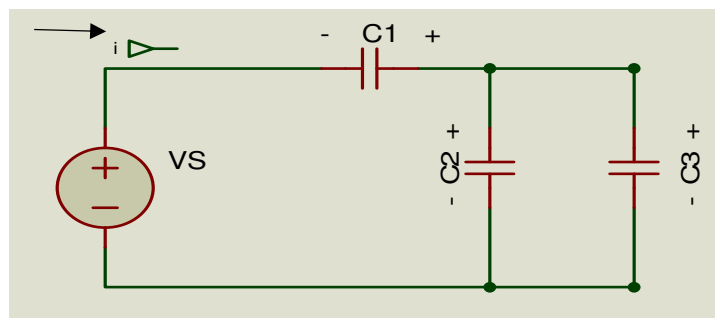

- c) i) Define the term transient response (1 mark)
- ii) Derive expressions to show the transient behavior of a RC and RL circuits then show how the time constant (τ) can be determined in each (8 marks)


QUESTION FOUR (20 MARKS)

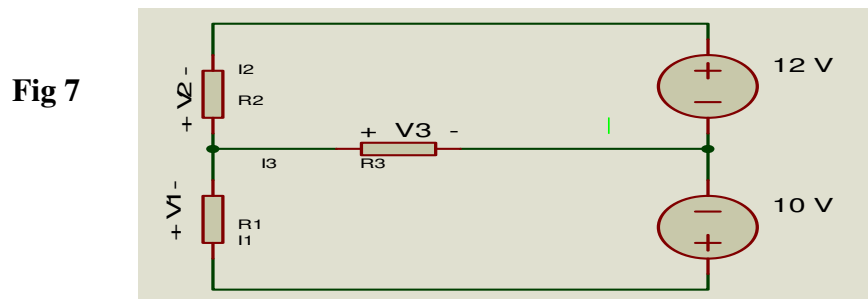- a) State the Kirchhoff's current law in electrical circuits (1 mark)
- b) Consider the circuit in Figure 7



Find each current and each voltage through the elements hence determine resistance R_2 . Currents and voltages through resistors R_1 , R_2 and R_3 are I_1 , I_2 , I_3 and V_1 , V_2 , V_3 respectively. $R_1 = 8\Omega$, $V_2 = -10V$, $I_3 = 2A$ and $R_3 = 1\Omega$. (5 marks)

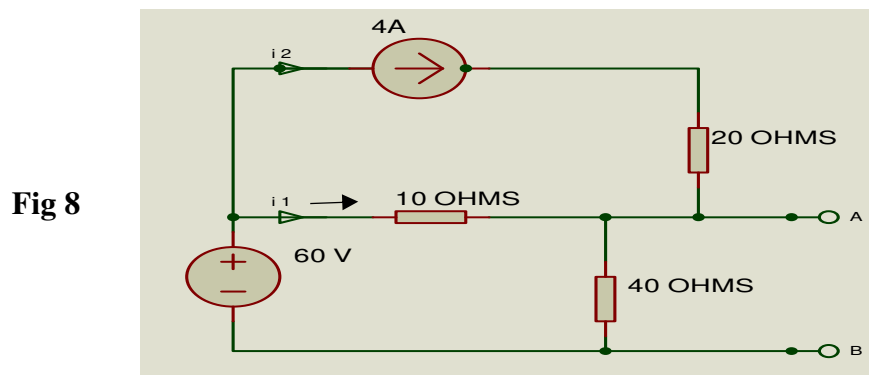- c) i) State the Thevenin's and Norton's network theorems (2 marks)
- ii) Considering the circuit in Figure 8




Find the Thevenin's and Norton's voltage across AB hence sketch the Thevenin's and Norton's equivalent circuits (7 marks)

- d) i) Give one difference between an inductor and a capacitor (1 mark)

- ii) Find the voltage across an inductor $L = 0.1\text{H}$ for $t > 0$ and $t = 0$ when the current in the inductor is $i(t) = 20te^{-2t}\text{ A}$. $i(0) = 0$ (4 marks)

QUESTION FIVE (20 MARKS)

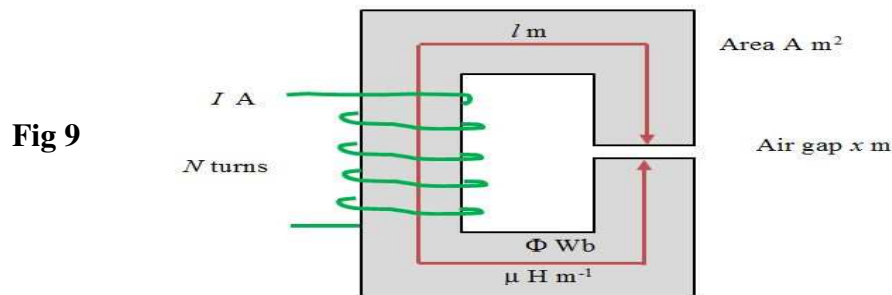- a) State the ohms law of magnetic circuits (1 mark)
- b) The magnetic circuit in figure 9 has a magnetic material of relative permeability of 1.75. It has a cross section of 2.5 cm by 2.5 cm and an average length of 25 cm. The air gap cut into it which is 1mm in length.



Calculate

- Reluctance of the material (3 marks)
 - Reluctance of the air gap (2 marks)
 - Total reluctance (1 mark)
- c) The magnetic circuit in Figure 9 consists of 300 turns that carry a current of 0.75 A. Calculate
- Magnetic motive force (2 marks)
 - Magnetic flux (2 marks)
- d) A series RLC circuit containing a resistance of $12\ \Omega$, an inductance of 0.15 H and a capacitor of $100\mu\text{F}$ are connected in series across a 100 V , 50 Hz supply. Required
- Total impedance, (4 marks)
 - The total current, (1 mark)
 - The power factor (2 marks)
 - Voltage phasor diagram (2 marks)