



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE IN ELECTRICAL & ELECTRONICS ENGINEERING

EEE 204: CIRCUIT THEORY II

DATE:

TIME:

INSTRUCTIONS TO STUDENTS

1. This paper contains 5 questions.
2. Attempt **Question One** and Any Other Two questions
3. Show calculations where applicable

QUESTION ONE (COMPULSORY)(30 MARKS)

- a) Briefly explain **Three** advantages of three-phase circuit over single-phase circuit. (6 marks)
- b) In the parallel RLC circuit shown in Fig.Q1 b)
- (i) Calculate the values of ω_0 , Q-factor, and Bandwidth (3 marks)
 - (ii) Find half-power frequencies, ω_1 and ω_2 (3 marks)
 - (iii) Determine the power dissipated at ω_0 , ω_1 and ω_2 . (4 marks)

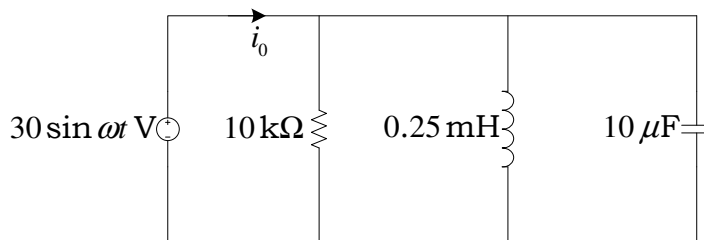


Fig.Q1 b)

- c) Find $i(t)$ for the circuit of Fig. (b) when $i_1(t) = 7e^{-6t}$ A for $t \geq 0$ and $i(0) = 0$ using Laplace transforms. (6 marks)

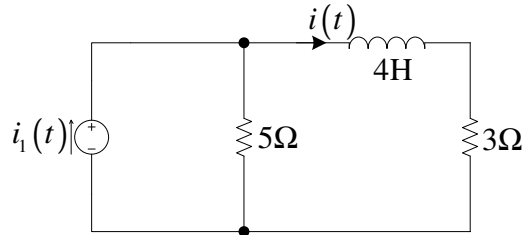


Fig. Q1 c)

- d) Find the natural response of $i_n(t)$ for $t > 0$ for the circuit shown in Fig.Q1 d) given that $i(0) = 2 \text{ A}$. (8 marks)

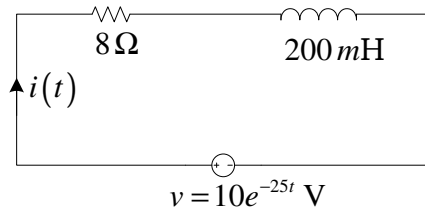


Fig.Q1d)

QUESTION TWO (20 MARKS)

- a) A star connected three phase load has a resistance of 10Ω and a capacitive reactance of 20Ω in each phase. It is fed from a 400 V 3 phase balanced supply. Find
- (i) The magnitude of phase voltage (1 mark)
 - (ii) the line current (1 mark)
 - (iii) apparent power (1 mark)
 - (iv) active power (1 mark)
 - (v) reactive power (1 mark)
 - (vi) Draw phasor diagram showing phase voltages, line voltages and line currents. (9 marks)

- b) Determine the forced response for the circuit current, i_f , for the circuit of Fig. Q2 b). (7 marks)

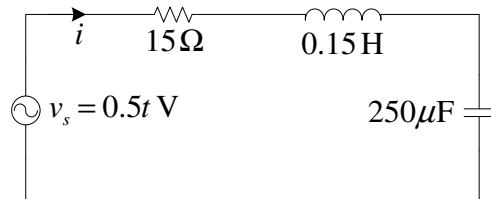


Fig. Q2 b)

QUESTION THREE (20 MARKS)

a) In the circuit shown in Fig. Q3 a), find

(i) The total circuit resistance

(5 marks)

(ii) The supply current I

(1 mark)

(iii) The voltage across $20\ \Omega$ resistor

(2 marks)

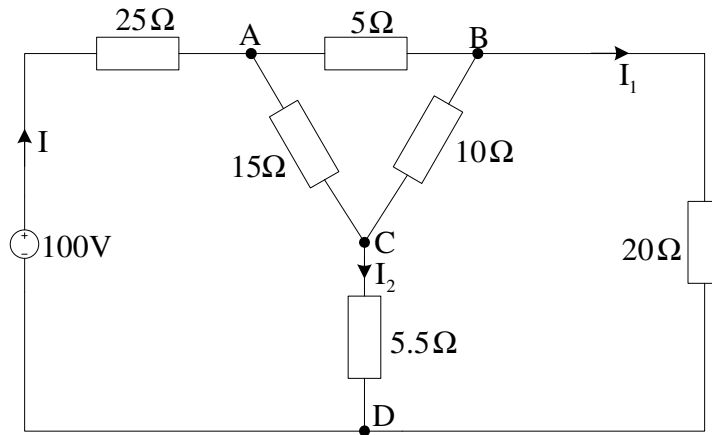


Fig. Q3 a)

b) Find the complete response of the circuit of Fig. Q3 b), given that $i(0) = 0$.

(12 marks)

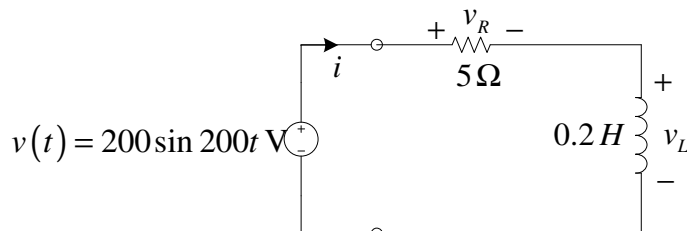


Fig. Q3 b)

QUESTION FOUR (20 MARKS)

a) A series RLC circuit has $R = 25\ \Omega$, $L = 0.05\ H$ and $C = 4\ \mu F$. The applied voltage is $80\ V$.

Find

i) Resonant frequency in Hertz

(2 marks)

ii) Q-factor

(1 mark)

iii) Upper and lower half power frequencies

(3 marks)

iv) Band width in Hertz

(1 mark)

v) Current at resonance

(1 mark)


vi) Current at half power points

(1 mark)

vii) Voltage across inductance at resonance

(1 mark)

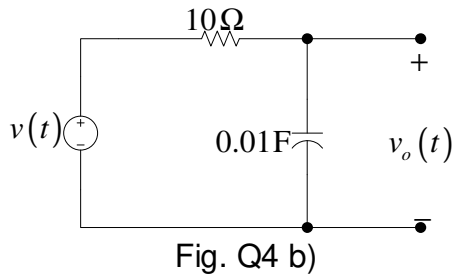- b) Using Fourier transform method, determine, the response $V_o(\omega)$ of the circuit of Fig. Q4b) when $v(t) = 10e^{-5t}u(t)$ V and plot the poles and zeros on the s-plane.



(6 marks)

- c) Briefly explain the following terms as used in circuit analysis:

- | | |
|------------------------|----------|
| i) Resonance | (1 mark) |
| ii) Phase Sequence | (1 mark) |
| iii) Natural Response | (1 mark) |
| iv) Frequency response | (1 mark) |

QUESTION FIVE (20 MARKS)

- a) Construct the Bode plots of the function below for $0.1 < \omega < 100$ rad/s. $H(s) = \frac{10(s+100)}{s+1}$
(7 marks)
- b) A delta-connected 3 phase load has an impedance of $(10 + j15)\Omega$ in each phase. It is fed from a 200 V, 3-phase balanced supply. Find
- | | |
|--|-----------|
| (i) The phase current | (3 marks) |
| (ii) The line current | (1 mark) |
| (iii) The apparent power | (1 mark) |
| (iv) The active power | (1 mark) |
| (v) The Reactive power | (1 mark) |
| (vi) Draw phasor diagram showing phase voltages, line currents and phase currents. | (6 marks) |