



# MACHAKOS UNIVERSITY

University Examination 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)

EEE 313: TRANSMISSION LINES AND WAVEGUIDES

DATE: 20/5/2019

TIME: 8.30-10.30 AM

---

## INSTRUCTIONS

*Answer Question ONE and any other TWO Questions.*

*All workings must be clearly shown*

*The Smith Charts provided should be attached to the Answer Booklet after use.*

*Take the speed of light in free space to be  $c = 3 \times 10^8 \text{ m/s}$ .*

## QUESTION ONE (30 MARKS) (COMPULSORY)

- a) Define a Transmission Line and outline **THREE** broad categories of Transmission Lines. (4 marks)
- b) A 30m long lossless transmission line with  $Z_0 = 50\Omega$  operating at 2MHz is terminated with a load  $Z_L = 60 + j40\Omega$ . If  $u = 0.6c$  on the line, where  $c$  is the speed of light in a vacuum, find the parameters listed below both without using the Smith Chart and by using the Smith Chart and comment on the results. (10 marks)
- The reflection coefficient  $\Gamma$
  - The standing wave ratio  $s$
  - The input Impedance  $Z_{in}$
- c) What do you understand by the following terms as used in Transmission Lines:
- Phase velocity
  - Dispersion
  - Voltage Standing Wave Ratio
  - Characteristic impedance (4 marks)

- d) Fig.Q1 d) shows an L-type equivalent circuit model of a differential length  $\Delta z$  of a two-conductor transmission line. (8 marks)

Use it to derive the transmission line equations (wave equations for both voltage  $V_s(z)$  and current  $I_s(z)$  in the line). State any assumptions made.

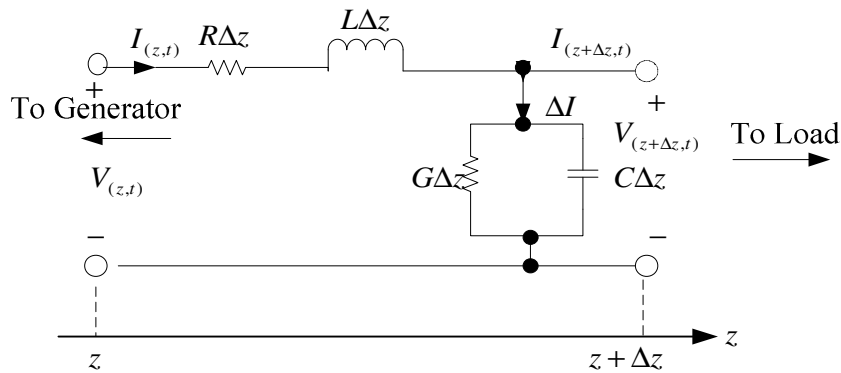


Fig.Q1 d) Two-conductor transmission line model of differential length  $\Delta z$

- e) A generator with an open-circuit voltage  $V_g(t) = 100\sin(8000\pi t)$  and internal impedance  $Z_g = 40 + j30 \Omega$  is connected to a  $50\Omega$  distortionless line. The line has a resistance of  $0.5\Omega/m$ , and its lossy dielectric medium has a loss tangent of  $0.18\%$ . The line is  $50m$  long and is terminated in a matched load. Find the instantaneous expressions for the voltage and current at an arbitrary location on the line. (4 marks)

## QUESTION TWO (20 MARKS)

- a) With practical examples, distinguish between wave propagation in bounded media and unbounded media. (4 marks)
- b) Explain the meaning of transit time and use the concept to distinguish between Lumped and distributed parameters as used in transmission line modelling and analysis. (4 marks)
- c) With the aid of block diagrams and mathematical expressions, distinguish between ABCD –Parameters and  $S$ -parameters as used in two-port networks analysis of transmission lines. Hence, show that for the case where a 2-port network is created by cascading two networks having transmission matrices defined as  $T_A$  and  $T_B$ , respectively, the total transmission  $T$  is given by  $T = T_A T_B$ . (7 marks)
- d) A lossless transmission line is  $80cm$  long and operates at a frequency of  $600MHz$ . The line parameters are  $L = 0.25\mu H/m$  and  $C = 100pF/m$ . Find: (5 marks)
- the characteristic impedance of the line
  - the phase constant

- iii. the velocity on the line
- iv. the input impedance for  $Z_L = 100\Omega$ .

### QUESTION THREE (20 MARKS)

- a) List **FOUR** differences between a transmission line and waveguide. (4 marks)
- b) Using the circuit of Fig. Q3 b) of a finite transmission line connected to a load, show that the input impedance is given by  $Z_i = (Z)_{z=0}^{z'=l} = Z_0 \left( \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \right)$  (6 marks)

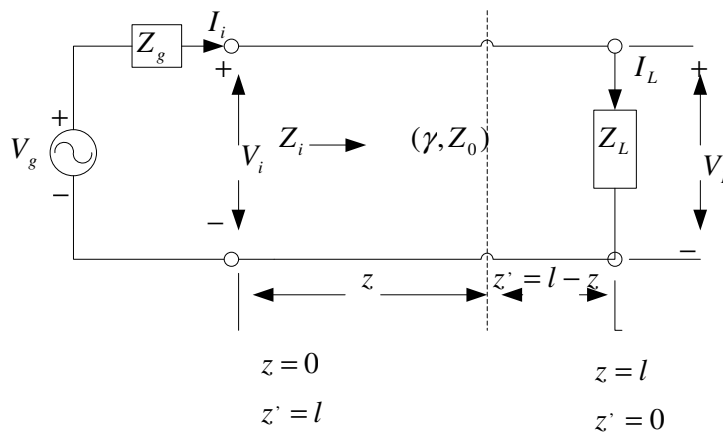


Fig. Q3 b) Finite Transmission Line Connected to Load

- c) A certain transmission line operating at  $\omega = 10^6 \text{ rad/s}$  has  $\alpha = 8 \text{ dB/m}$ ,  $\beta = 1 \text{ rad/m}$ , and  $Z_0 = 60 + j40\Omega$ , and is  $2\text{m}$  long. If the line is connected to a source of  $10\text{V}$ ,  $Z_g = 40\Omega$  and terminated by a load of  $20 + j50\Omega$ , determine: (10 marks)
  - i. The input impedance
  - ii. The sending-end current
  - iii. The current at the middle of the line

### QUESTION FOUR (20 MARKS)

- a) With aid of examples and block diagrams, explain the difference between balanced and unbalanced transmission lines or systems. (4 marks)
- b) Discuss the meaning of Resonant Line and Anti-resonant Line as used in transmission lines. (4 marks)
- c) Prove that a maximum power is transferred from a voltage source with an internal impedance  $Z_g$  to a load impedance  $Z_L$  over a lossless transmission line when  $Z_i = Z_g^*$


where  $Z_i$  is the impedance looking into the loaded line. What is the maximum power transfer efficiency? (4 marks)

- d) A  $100\text{MHz}$  generator with  $V_g = 10\text{V}$  and internal resistance  $50\Omega$  is connected to a lossless  $50\Omega$  air line that is  $3.6\text{m}$  long and terminated in a  $25 + j25\Omega$  load. Find:
- $V(z)$  at a location  $z$  from the generator,
  - $V_i$  at the input terminals and  $V_L$  at the load,
  - the voltage standing-wave ratio on the line, and
  - The average power delivered to the load. (8 marks)

#### QUESTION FIVE (20 MARKS)

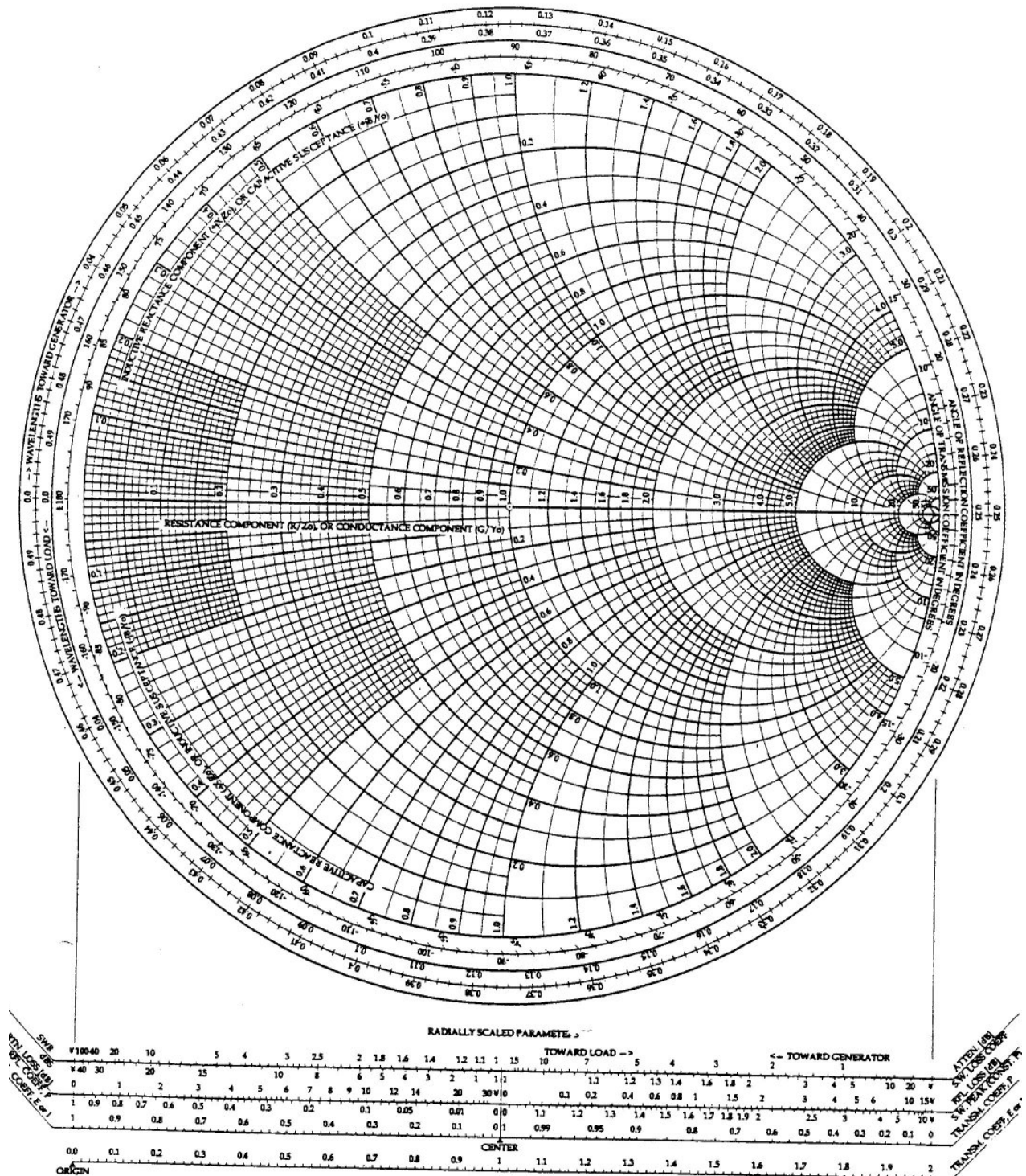- a) In the analysis of transmission lines there are **TWO** main approaches which can be adopted. Give these approaches and justify the selection made between them in this unit. (3 marks)
- b) A distortionless line has  $Z_0 = 60\Omega$ ,  $\alpha = 20\text{mNp/m}$ ,  $u = 0.6c$ , where  $c$  the speed of light in a vacuum is. Determine  $R$ ,  $L$ ,  $G$ ,  $C$  and  $\lambda$  for the line at  $100\text{MHz}$ . (5 marks)
- c) Explain **ONE** Advantage and **ONE** Disadvantage of single-stub matching technique of transmission lines as compared to the quarter wavelength transformer. (4 marks)
- d) A  $50\Omega$  transmission line is connected to a load impedance  $Z_L = 35 - j47.5\Omega$ . Using Smith Chart, find the position and length of a short-circuited stub required to match the line. (8 marks)

CANDIDATE REG. NO.....  
 THE SMITH CHART- NO.1





CANDIDATE REG. NO.....  
**THE SMITH CHART-NO.2**

