



MACHAKOS UNIVERSITY

University Examinations 2017/2018

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERINGB

FIFTH YEAR SECOND SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONIC ENGINEERING)

EEE 519: RADIO FREQUENCY CIRCUIT DESIGN

DATE: 14/12/2017

TIME: 8.30-10.30 AM

INSTRUCTIONS:

- (i) There are a total of **Five** questions.
- (ii) Question No. 1 is **Compulsory** and carries **30 Marks**.
- (iii) Select any **other Two** questions, each of which carries 20 Marks.
- (iv) Define all symbols used.
- (v) Marks will be awarded for procedure, methodologies used and not necessarily the final answer.

-
1. (a) (i) Using relevant schematic diagrams, demonstrate the operations of an oscillator. (4 Marks)
- (ii) Fig. Q1 is an amplifier with the Transistor connected in Common Base configuration. Derive the T-Model equivalent circuit of the circuit. (6 Marks)
- (b) (i) Using symbols of various types, demonstrate thorough understanding of MOSFETs. (4 Marks)
- (ii) Determine the radius of the AWG 26 wire if the diameter of the AWG 44 wire is 1.0 mils (2.54×10^{-3} m). (6 Marks)
- (c) (i) Using relevant schematic diagrams show why Schottky diodes are preferred for *RF* circuits. (4 Marks)
- (ii) Outline the role of the crystal in the Crystal Oscillator circuit.

- (6 Marks)
2. (a) (1) Compute the skin depth for:-
 - (a) Copper ($\sigma_{cu} = 64.516 \times 10^6 \text{ S/m}$) at:-
 - a. 1GHz . (5 Marks)
 - b. 10GHz. (5 Marks)
 - (2) Find the resistance of a 10cm long, with 1mm diameter
 - a. Copper wire (5 Marks)
 - b. Aluminium wire ($\sigma_{Al} = 40 \times 10^7 \text{ S/m}$) (5 Marks)
 3. Consider a Transmission Line with $\lambda = 1.5$ metres, $Z_o = 400 \Omega$, $Z_R = 125 + j60$. The Line is to be matched using a Single Stub Tuner.
 - (i) Show why matching is necessary in a Transmission Line. (4 Marks)
 - (ii) Using a Smith Chart, determine:-
 - a. The appropriate location of the Stub Tuner from the Load. (8 Marks)
 - b. The Length of the Stub. (8 Marks)
 4. (a) Fig. Q4 gives the Characteristics of a MOSFET, Tr , whose Q point is at $V_{GS} = -10\text{V}$, $V_{BS} = +4\text{V}$, $V_{DS} = -10\text{V}$. Determine the Drain Current for Tr when:-
 - (i) $V_{BS} = 0\text{V}$. (2 Marks)
 - (ii) $V_{BS} = +4\text{V}$. (2 Marks)
 - (iii) $V_{BS} = +10\text{V}$ (2 Marks)
 - (b) Calculate the Mutual Conductance (g_m) for Tr at:-
 - (i) $V_{BS} = 0\text{V}$. (2 Marks)
 - (ii) $V_{BS} = +4\text{V}$. (2 Marks)
 - (iii) $V_{BS} = +10\text{V}$ (2 Marks)
 - (c) Draw a plot of g_m versus V_{BS} and give its interpretation. (4 Marks)
 - (d) Draw the equivalent circuit of the MOSFET. (4 Marks)
 5. (a) Using relevant schematic diagrams:-
 - c. Show how a crystal oscillator operates (8 Marks)
 - d. Identify the design considerations. (4 Marks)
 - (b) Consider a Two-Port Network [S].
 - (i) Derive the S parameters for the Network. (4 Marks)
 - (ii) Demonstrate thorough understanding of what the S parameters actually mean in the RF field. (4 Marks)

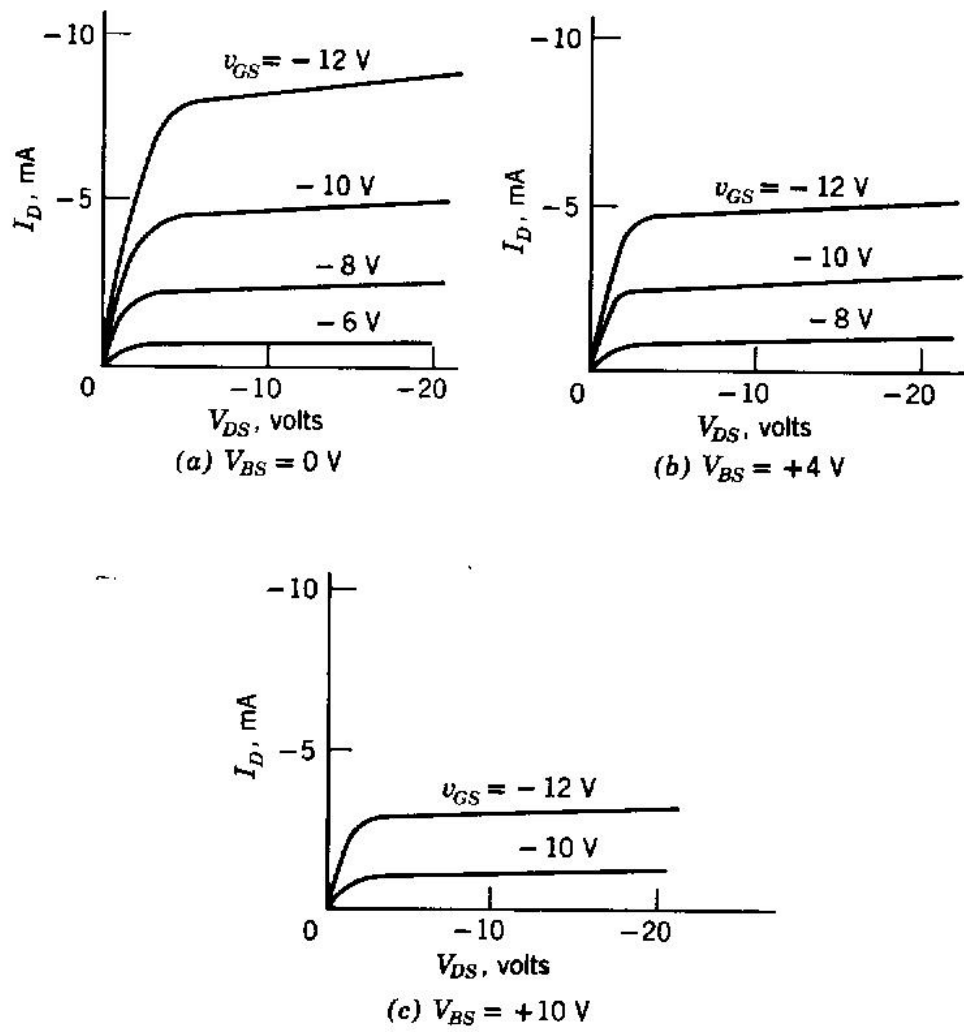


Fig. Q4