



MACHAKOS UNIVERSITY

University Examinations for 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**FOURTH YEAR FIRST SEMESTER EXAMINATION FOR BACHELOR OF SCIENCE
IN ELECTRICAL AND ELECTRONICS ENGINEERING**

EEE 405: POWER ELECTRONICS

DATE: 20/6/2017

TIME: 8.30-10.30 AM

Instructions

- *This paper consists of Five Questions*
- *Attempt **Question One** (Compusory) and any other **Two Questions***

QUESTION ONE (COMPULSORY)

- a) The Figure Q.1 shows the switching characteristics for a power semiconductor device.

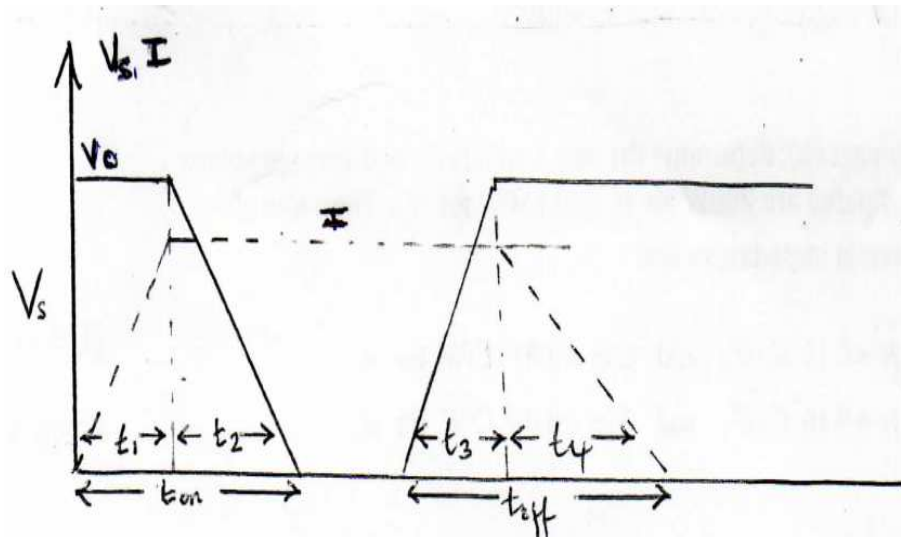


Fig Q. 1 Power Switching Characteristic

- i. Derive the expressions for the energy loss during turn-on and turn-off periods (2 marks)
 - ii. Derive the expression for the average switching energy loss (2 marks)
 - iii. Sketch the variation of the variation of power loss during turn-on and turn-off periods (1 mark)
 - iv. For $V_s = 220V$, $I = 10A$, $t_1 = 1\mu s$, $t_2 = 2\mu s$, $t_3 = 1.5\mu s$, $t_4 = 3\mu s$, determine the average power switching loss in the device for a switching frequency of 1KHz (3 marks)
- b) A Bipolar transistor has a current gain $\beta = 50$, load resistance $R_C = 10\Omega$, DC supply voltage $V_{CC} = 120V$, and input voltage to base circuit $V_B = 10V$. For $V_{CES} = 1.2V$ and $V_{BES} = 1.6V$,
- i. Sketch a well labelled transistor circuit with all the parameters shown (2 marks)
 - ii. Determine the value of R_B for operation in the saturation state (2 marks)
 - iii. Determine the value of R_B for an overdrive factor of 6 (3 marks)
 - iv. Determine forced current gain (1 mark)
 - v. Determine the power loss in the transistor for cases (f) and (g) above (4 marks)

- c) State any Six qualities of a good industrial Inverter (3 marks)
- d) A three phase M-3 converter is operated from a three phase, 230V 50Hz supply with a load resistance of $R = 10\Omega$. An average output voltage of 50% of the maximum possible output voltage is required. Determine from the first principles
- The firing angle
 - Average and Rms load current
 - Rectification Efficiency (7 marks)

QUESTION TWO

- a) Distinguish between *Step Up* and *Step Down* Chopper (1 marks)
- b) For a *Step Up Chopper* show that

$$V_o = \frac{1}{1 - \alpha} V_s$$

All the symbols carry their usual meaning (4 marks)

- c) A step up chopper has input voltage of 220V and output voltage of 660V. The conducting time in the thyristor chopper is $100\mu s$. The pulse width of the output voltage is halved for a constant frequency. Determine the average value of the new output voltage (4 marks)
- d) A step-down chopper, fed from 220V DC supply is connected to RL load with $R = 10\Omega$ and $L = 15mH$. The Chopper frequency is 1250HZ and the duty cycle is 0.5. Determine
- The maximum and minimum load currents (5 marks)
 - The maximum ripple current (1 mark)
 - The average and rms load voltages and currents (4 marks)
 - Rms chopper current (1 mark)

QUESTION THREE

- a) State *Four* Industrial Applications of Inverters (4 marks)
- b) Distinguish between the following
- Line-Commutated and Forced-Commutated inverters
 - Voltage-Source and Current-Source Inverters (4 marks)
- c) A single phase full bridge inverter is connected to an RL load. The Inverter has a DC source voltage of V_s and output frequency of $f = 1/T$.

- i. Sketch a well labelled inverter circuit described in this case (2 marks)
- ii. Obtain the expressions for load currents as a function of time for the first two half cycles of the output voltage (4 marks)
- iii. Obtain the expressions for the steady state currents as a function of time for the first two half cycles (4 marks)
- iv. For $R = 2\ \Omega$, $L=0.1H$, $V_s = 240V\ dc$ and the frequency of output voltage being 50HZ, determine the load currents in (ii) and (iii) above (4 marks)

QUESTION FOUR

A single phase transformer with secondary voltage of 230V 50HZ delivers power to a load $R = 10\ \Omega$ through a half wave controlled rectifier circuit. For a firing angle delay of 60° ,

- a) Sketch a well labeled diagram of the Rectifier Circuit plus transformer (2 marks)
- b) Determine from the *First Principles*
 - i. Average voltage current and DC power (4 marks)
 - ii. Rms output voltage, current and AC power (4 marks)
 - iii. Rectification efficiency (2 marks)
 - iv. Form factor (2 marks)
 - v. Voltage ripple factor (2 marks)
 - vi. Transformer utilization factor (2 marks)
 - vii. PIV of the thyristor (2 marks)

QUESTION FIVE

- a) State the various anode voltage ratings as applicable to an SCR. Indicate these voltage ratings on a relevant voltage waveform (5 marks)
- b) State *Any Four* Methods (Techniques) of Mounting Thyristors based on the thermal considerations (2 marks)
- c) A Thyristor is rated to carry full-loads current with an allowable case temperature of 100°C for a maximum allowable junction temperature of 125°C . The thermal resistance between case and ambient is 0.5°C/W and that between the sink and the ambient is 0.4°C/W . Determine the sink temperature for an ambient temperature of 40°C (3 marks)
- d) Figure Q.5 shows a snubber network connected across an SCR.

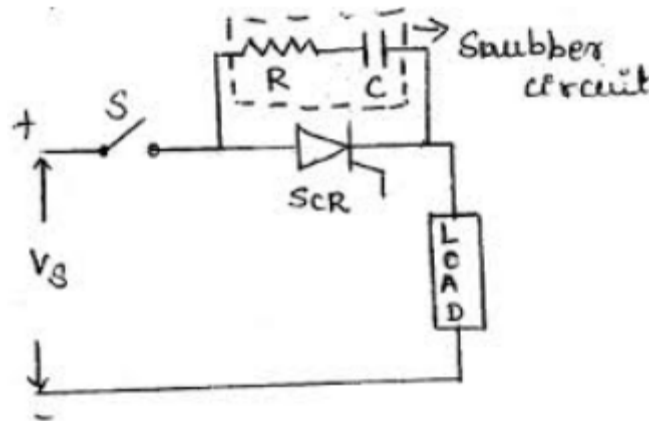


Fig Q. 5 Snubber Circuit for SCR

- i. From the first principles, derive the expressions for the $\frac{di}{dt}$ and $\frac{dv}{dt}$ in terms of the circuit parameters (4 marks)
 - ii. Derive the expressions of the R-L-C circuit parameters in terms of the damping ratio and snubber network quantities (2 marks)
- e) A thyristor is placed between a constant DC voltage source of 240V and a resistive load R. The specified limits of $\frac{di}{dt}$ and $\frac{dv}{dt}$ for the SCR are $60A/\mu s$ and $300V/\mu s$ respectively. The damping ratio is 0.5.
- i. Determine the $\frac{di}{dt}$ inductor and the Snubber Circuit parameters (3 marks)
 - ii. Explain how these parameters may be modified to suit the working conditions in the circuit (1 mark)