



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR

**BACHELOR OF SCIENCE (TELECOMMUNICATION AND INFORMATION
TECHNOLOGY)**

SPH 207: DIGITAL ELECTRONICS AND DEVICES

DATE: 15/12/2021

TIME: 8.30-10.30 AM


INSTRUCTIONS:

Answer Question One And Any Other Two Questions

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) It is proposed to construct an eight-input NAND gate using only two-input AND gates and two-input NAND gates. Draw the logic arrangement that uses the minimum number of logic gates. (5 marks)
- b) Briefly describe the operational aspects of bistable, monostable and astable multivibrators with their corresponding timing diagrams (9 marks)
- c) Simplify the following Boolean functions
 - (i) $AB' + A'B + AB + A'B$
 - (ii) $A[B + C(AB + AC)]$ (6 marks)
- d) Describe the following
 - (i) Logic gate propagation delay
 - (ii) Set-up time and hold time
 - (iii) Maximum clock frequency (6 marks)
 - (iv)

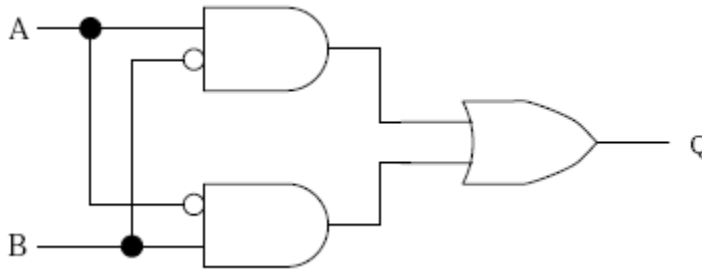- e) Draw the truth table of the logic circuit shown in below



(4 marks)

QUESTION TWO (20 MARKS)

Show how a power source, a lamp and a number of switches can be used to represent the following logical functions.

- $L = A.B.C$
- $L = A + B + C$
- $L = (A.B) + (C.D)$
- $L = A + B$

(10 marks)

QUESTIONTHREE (20 MARKS)

Convert the following hexadecimal numbers to binary and octal:

- EF69, 98AB5 (4 marks)
- Compare the standard TTL, low-power Schottky TTL and Schottky TTL on the basis of speed, power dissipation and fan-out capability (6 marks)
- With the help of the logic diagram, describe the operation of a clocked R-S flip-flop with active LOW R and S inputs. (10 marks)

QUESTION FOUR (20 MARKS)

- Design a decade ripple counter using a J-K negative going edge triggered flip flops (10 marks)

b)


Calculate $A + B$, $A - B$, $A \times B$, and $A \div B$ for the following pairs of binary numbers.

- 10101, 1011
- 1011010, 101111
- 101, 1011

(10 marks)

QUESTION FIVE (20 MARKS)

 - (a) Explain three advantages of CMOS logic compared to NMOS, stating which logic families that are most suitable for applications that requires
- (i) High speed
 - (ii) low power consumption
 - (iii) high noise immunity (6 marks)
- (b) Find the boolean expression for the out put of fig below and compute the output value when $A=0$, $B=1$, $C=0$ and $D=1$



(4 marks)

- (c) From the truth table below, derive
- (i) logic expression for F
 - (ii) simplify the expression as far as possible
 - (iii) draw the logic diagram to implement this (10 marks)

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1