



MACHAKOS UNIVERSITY

University Examination 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (MECHANICAL ENGINEERING)

EMM 300: ENGINEERING ELECTRONICS

DATE: 16/5/2019

TIME: 8.30-10.30 AM

INSTRUCTIONS

Answer Question ONE and any other TWO Questions.

QUESTION ONE (30 MARKS)

- a)
 - i Design a four-resistor bias network for an *npn* transistor to give $I_C = 10 \mu\text{A}$ and $V_{CE} = 6 \text{ V}$ if $V_{CC} = 18 \text{ V}$ and $\beta_F = 75$.
 - ii. Replace your exact values with the nearest values from the resistor table in Appendix and find the resulting Q-point. (10 marks)
- b) Derive the relationship between base current amplification factor β and emitter current amplification factor α . (6 marks)
 - i. State the two types of complement for a number system whose radix = r.
 - ii. Find the 2's complement of the decimal number 1/16.
 - ii. Determine the nine's complement of the decimal number 25.638?[7 marks]
- c) For the network of Fig.Q1 (c)
 - i. Determine I_{CQ} and V_{CEQ} ;
 - ii. Find V_B , V_C , V_E and V_{BC} .

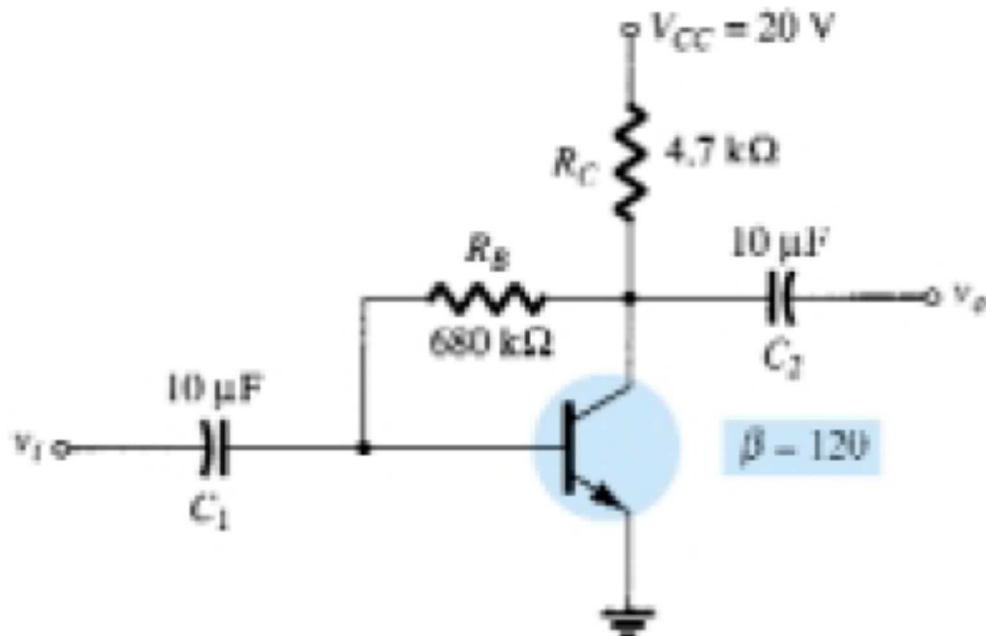


Fig.Q1 (c)

(7 marks)

QUESTION TWO (20 MARKS)

- a) Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider configuration of Fig.Q2 (a).

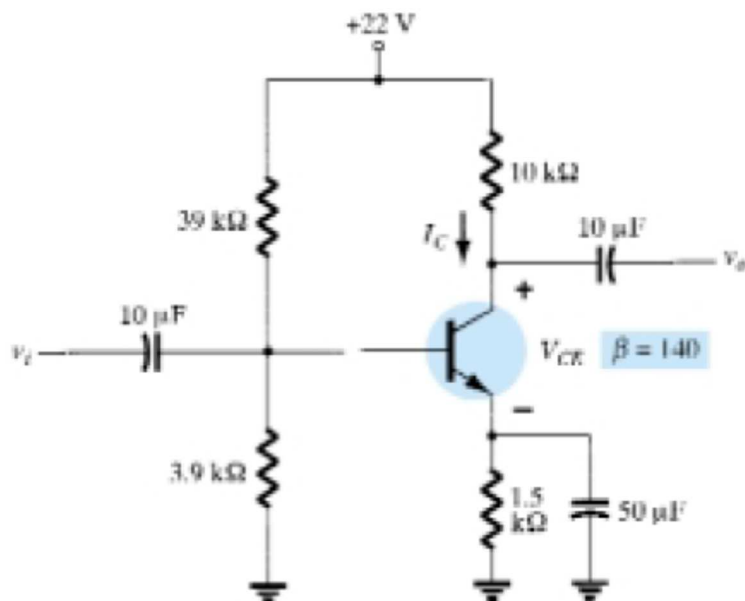


Fig.Q2 (a).

(8 marks)

- b) The parameters of the zener diode for the voltage regulator of the circuit of Fig. Q2 (b) are $V_Z = 4.7 \text{ V}$ at test current $I_{ZT} = 53 \text{ mA}$, $R_Z = 8 \Omega$, and $R_{ZK} = 500 \Omega$ at $I_{ZK} = 1 \text{ mA}$. The supply voltage $v_S = V_S = 12 \pm 2 \text{ V}$, and $R_S = 220 \Omega$.
- Find the nominal value of the output voltage v_O under no-load condition $R_L = \infty$;
 - Find the maximum and minimum value of the output voltage for a load resistance $R_L = 470 \Omega$;
 - Find the nominal value of the output voltage v_O for a load resistance $R_L = 100 \Omega$;
 - Find the minimum value of R_L for which the zener diode operates in the breakdown region.


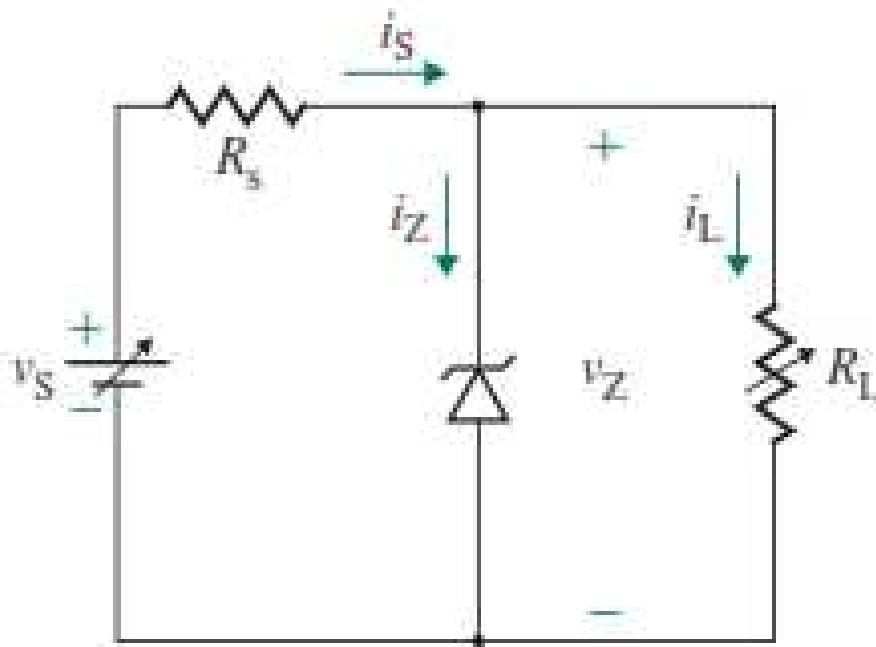


Fig.Q2 (b)

(12 marks)

QUESTION THREE (20 MARKS)

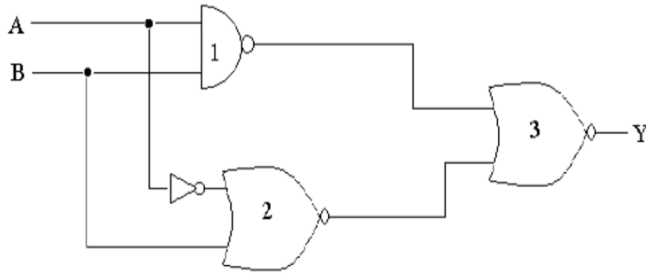- a) Find the Boolean expression for the logic circuit in FigQ3 (a).



FigQ3 (a)

(6 marks)

- b) A single-phase rectifier can be employed as a battery charger, as shown in Fig. Q3 (b). The battery capacity is 100 Wh, and the battery voltage is $E = 12$ V. The average charging current should be $I_{O(av)} = 5$ A. The primary AC input voltage is $V_p = 120$ V (rms), 60 Hz, and the transformer has a turns ratio of $n = 2:1$.

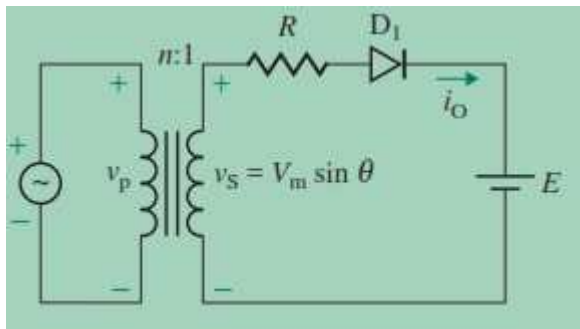


Fig.Q3 (b).

Calculate

- the angle δ over which the diode conducts;
- The current limiting resistance R ;
- The power rating P_R of the resistance R ;
- The charging time h in hours;
- the rectifier efficiency η_R ;
- The peak inverse voltage PIV of the diode.

(14 marks)

QUESTION FOUR (20 MARKS)

- a) Consider the ac equivalent circuit of the Hartley oscillator in Fig.Q4 (a)
- Derive the expression for the frequency of oscillation;
 - Determine the condition for sustained oscillations.

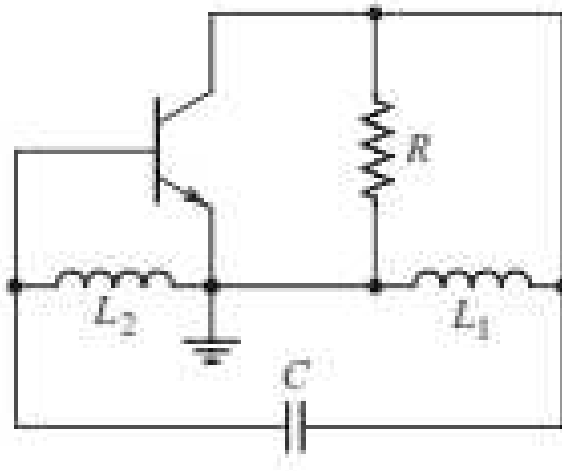


Fig.Q4 (a)


(14 marks)

- b) Draw a block diagram of a BCD-to-7 segment decoder indicating the output given that the input is 0101. (6 marks)

QUESTION FIVE (20 MARKS)

- a)
 - Define synchronous counters.
 - Design a **MODULO-5** synchronous counter using **JK** flip-flops. (13 marks)
- b) Explain how a shift register can be used as a ring counter giving the wave forms at the output of the flip-flops. (7 marks)

Appendix

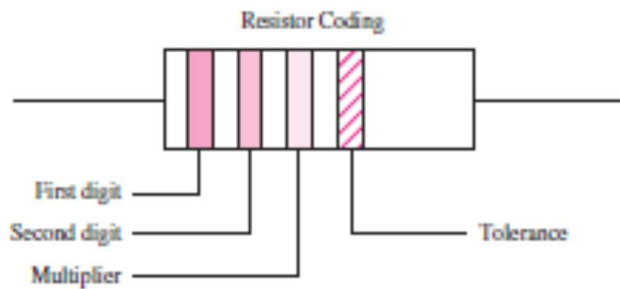

Resistor Color Code			
COLOR	DIGIT	MULTIPLIER	TOLERANCE, %
Silver	...	0.01	10
Gold	...	0.1	5
Black	0	1	
Brown	1	10	
Red	2	10 ²	
Orange	3	10 ³	
Yellow	4	10 ⁴	
Green	5	10 ⁵	
Blue	6	10 ⁶	
Violet	7	10 ⁷	
Gray	8	10 ⁸	
White	9	10 ⁹	

Standard resistor values: All values available with a 5 percent tolerance. Bold values are available with 10 percent tolerance.

OHMS								MEGOHMS	
1.0	5.6	33	180	1000	5600	33000	180000	1.0	5.6
1.1	6.2	36	200	1100	6200	36000	200000	1.1	6.2
1.2	6.8	39	220	1200	6800	39000	220000	1.2	6.8
1.3	7.5	43	240	1300	7500	43000	240000	1.3	7.5
1.5	8.2	47	270	1500	8200	47000	270000	1.5	8.2
1.6	9.1	51	300	1600	9100	51000	300000	1.6	9.1
1.8	10	56	330	1800	10000	56000	330000	1.8	10
2.0	11	62	360	2000	11000	62000	360000	2.0	11
2.2	12	68	390	2200	12000	68000	390000	2.2	12
2.4	13	75	430	2400	13000	75000	430000	2.4	13
2.7	15	82	470	2700	15000	82000	470000	2.7	15
3.0	16	91	510	3000	16000	91000	510000	3.0	16
3.3	18	100	560	3300	18000	100000	560000	3.3	18
3.6	20	110	620	3600	20000	110000	620000	3.6	20
3.9	22	120	680	3900	22000	120000	680000	3.9	22
4.3	24	130	750	4300	24000	130000	750000	4.3	
4.7	27	150	820	4700	27000	150000	820000	4.7	
5.1	30	160	910	5100	30000	160000	910000	5.1	

PRECISION (±%) RESISTORS																	
10.0	19.1	36.5	69.8	133	255	487	931	1.78K	3.40K	6.49K	12.4K	23.7K	45.3K	84.5K	158K	294K	549K
10.2	19.6	37.4	71.5	137	261	499	953	1.82K	3.48K	6.65K	12.7K	24.3K	46.4K	86.6K	162K	301K	562K
10.5	20.0	38.3	73.2	140	267	511	976	1.87K	3.57K	6.81K	13.0K	24.9K	47.5K	88.7K	165K	309K	576K
10.7	20.5	39.2	75.0	143	274	523	1.00K	1.91K	3.65K	6.98K	13.3K	25.5K	48.7K	90.9K	169K	316K	590K
11.0	21.0	40.2	76.8	147	280	536	1.02K	1.96K	3.74K	7.15K	13.7K	26.1K	49.9K	93.1K	174K	324K	604K
11.3	21.5	41.2	78.7	150	287	549	1.05K	2.00K	3.83K	7.32K	14.0K	26.7K	51.1K	95.3K	178K	332K	619K
11.5	22.1	42.2	80.6	154	294	562	1.07K	2.05K	3.92K	7.50K	14.3K	27.4K	52.3K	97.6K	182K	340K	634K
11.8	22.6	43.2	82.5	158	301	576	1.10K	2.10K	4.02K	7.68K	14.7K	28.0K	53.6K	100K	187K	348K	649K
12.1	23.2	44.2	84.5	162	309	590	1.13K	2.15K	4.12K	7.87K	15.0K	28.7K	54.9K	102K	191K	357K	665K
12.4	23.7	45.3	86.6	165	316	604	1.15K	2.21K	4.22K	8.06K	15.4K	29.4K	56.2K	105K	196K	365K	681K
12.7	24.3	46.4	88.7	169	324	619	1.18K	2.26K	4.32K	8.25K	15.8K	30.1K	57.6K	107K	200K	374K	698K
13.0	24.9	47.5	90.9	174	332	634	1.21K	2.32K	4.42K	8.45K	16.2K	30.9K	59.0K	110K	205K	383K	715K
13.3	25.5	48.7	93.1	178	340	649	1.24K	2.37K	4.53K	8.66K	16.5K	31.6K	60.4K	113K	210K	392K	732K
13.7	26.1	49.9	95.3	182	348	665	1.27K	2.43K	4.64K	8.87K	16.9K	32.4K	61.9K	115K	215K	402K	750K
14.0	26.7	51.1	97.6	187	357	681	1.30K	2.49K	4.75K	9.09K	17.4K	33.2K	63.4K	118K	221K	412K	768K
14.3	27.4	52.3	100	191	365	698	1.33K	2.55K	4.87K	9.31K	17.8K	34.0K	64.9K	121K	226K	422K	787K
14.7	28.0	53.6	102	196	374	715	1.37K	2.61K	4.99K	9.53K	18.2K	34.8K	66.5K	124K	232K	432K	806K
15.0	28.8	54.9	105	200	383	732	1.40K	2.67K	5.11K	9.76K	18.7K	35.7K	68.1K	127K	237K	442K	825K
15.4	29.4	56.2	107	205	392	750	1.43K	2.74K	5.23K	10.0K	19.1K	36.5K	69.8K	130K	243K	453K	845K
15.8	30.1	57.6	110	210	402	768	1.47K	2.80K	5.36K	10.2K	19.6K	37.4K	71.5K	133K	249K	464K	866K
16.2	30.9	59.0	113	215	412	787	1.50K	2.87K	5.49K	10.5K	20.0K	38.3K	73.2K	137K	255K	475K	887K
16.5	31.6	60.4	115	221	422	806	1.54K	2.94K	5.62K	10.7K	20.5K	39.2K	75.0K	140K	261K	487K	909K
16.9	32.4	61.9	118	226	432	825	1.58K	3.01K	5.76K	11.0K	21.0K	40.2K	76.8K	143K	267K	499K	931K
17.4	33.2	63.4	121	232	443	845	1.62K	3.09K	5.90K	11.3K	21.5K	41.2K	78.7K	147K	274K	511K	953K
17.8	34.0	64.9	124	237	453	866	1.65K	3.16K	6.04K	11.5K	22.1K	42.2K	80.6K	150K	280K	523K	976K
18.2	34.8	66.5	127	243	464	887	1.69K	3.24K	6.19K	11.8K	22.6K	43.2K	82.5K	154K	287K	536K	1.00M
18.7	35.7	68.1	130	249	475	909	1.74K	3.32K	6.34K	12.1K	23.2K	44.2K					