



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATIONS FOR BACHELOR OF

SCIENCE IN ELECTRICAL AND ELECTRONICS ENGINEERING

EEE 306: DIGITAL ELECTRONICS II

DATE: 15/12/2021

TIME: 8.30-10.30 AM

INSTRUCTIONS

ANSWER QUESTION ONE AND ANY OTHER TWO

QUESTION ONE (30 MARKS)

- (a) For a 4×1 Multiplexer, give the truth table and the gate-level circuit implementation of the same. (5 marks)
- (b) Show how the full adder can be implemented using a decoder of your choice and OR gates. (6 marks)
- (c) Differentiate between combinational and sequential logic circuits. (4 marks)
- (d) Show the implementation of the following Boolean function using a 8×1 multiplexer. (5 marks)

$$F = \Sigma (0, 2, 5, 7, 11, 14)$$

- (e) Differentiate between a PLA, PAL and PROM in terms of the AND and OR arrays. (3 marks)
- (f) Design a 3-bit counter which counts in the sequence: 001, 011, 010, 110, 111, 101, 001. (7 marks)
Use clocked T flip-flops.

QUESTION TWO (20 MARKS)

- (a) Implement the logic function below using a 4×1 Multiplexer. (6 marks)

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

- (b) Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number. (6 marks)

- (c) A 6-bit R-2R ladder D/A converter has a reference voltage of 6.5V. It meets standard linearity.

Find: (i) The Resolution in Percent.

(ii) The output voltage for the word 011100. (4 marks)

- (d) 6-bit Dual Slope A/D converter uses a reference of –6V and a 1 MHz clock. It uses a fixed count of 40 (101000). Find Maximum Conversion Time. (4 marks)

QUESTION THREE (20 MARKS)

- (a) Show how the functions below can be implemented using a PLA. (6 marks)

$$F1 = AB' + AC + A'BC'$$

$$F2 = (AC + BC)'$$


- (b) With the help of a neat diagram, explain the working of a successive approximation A/D converter. (6 marks)
- (c) Implement a 1×8 demultiplexer using 1×4 demultiplexers. (4 marks)
- (d) Implement a 3 to 8 decoder using 2 to 4 decoders. (4 marks)

QUESTION FOUR (20 MARKS)

- (a) Implement the full adder circuit using a dual 4×1 multiplexer. (6 marks)
- (b) Implement the functions below using a decoder and OR gates. (4 marks)

$$\begin{aligned}F_1 &= x(y + y')z = x'y'z' = \Sigma(0, 5, 7) \\F_2 &= xy'z' + x'y + x'y(z + z') = \Sigma(2, 3, 4) \\F_3 &= x'y'z + xy(z + z') = \Sigma(1, 6, 7)\end{aligned}$$

 - (c) A certain 8-bit DAC has a full-scale output of 2mA and a full-scale error of $\pm 0.5\%$ Full Scale. What is the range of possible outputs for an input of 10000000? (3 marks)
- (d) Design a three bit gray counter whose state diagram is shown below using JK flip flops. (7 marks)



QUESTION FIVE (20 MARKS)

We wish to design a sequence detector circuit, which detects three or more consecutive 1's in a string of bits coming through an input line.

- (a) Find the state diagram. (4 marks)
- (b) Determine the type of the circuit (Moore or Mealy model). (3 marks)
- (c) Tabulate state (or transition) table of sequence detector. (5 marks)
- (d) Implement the circuit using D and J-K flip-flops. (8 marks)