



MACHAKOS UNIVERSITY

University Examinations for 2023/2024 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (TELECOMMUNICATION AND INFORMATION
TECHNOLOGY)

EEE 308: ANALOGUE ELECTRONICS I

DATE:

TIME:

INSTRUCTIONS

Answer question **ONE** and **ANY OTHER TWO** questions

QUESTION ONE (COMPULSORY) [30 MARKS]

- (a) Figure 2 represents a portion of battery-charger circuit for a battery with a voltage V_B . The sine-wave input $V_S = 12V(\text{rms})$, while the battery voltage varies from 12V to 14V from the discharged to fully charged states. The charging source resistance $R_S = 10\Omega$. Assuming that D is an ideal diode, and $R_C = 50\Omega$ is a current-controlling resistor established by the designer:

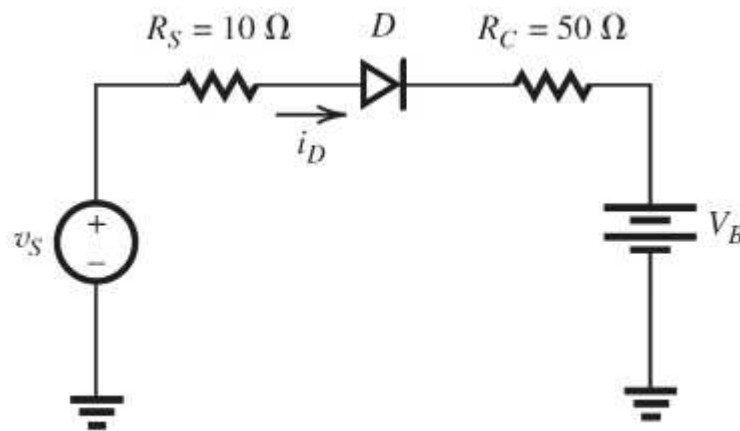


FIGURE 2. Battery-charger circuit

- (i) Sketch and label the voltage wave forms of the voltage across the diode and the current through the diode for $V_B = 12\text{V}$.
(5 marks)
- (ii) What is the peak diode current?
(5 marks)
- (b) For the common-emitter circuit in Figure 4
 - (i) Calculate the base current, collector current, emitter currents, the V_{CE} voltage and the transistor power dissipation. Assume $\beta = 200$ and $V_{BE(\text{on})} = 0.7\text{V}$
(5 marks)
 - (ii) What is the mode of operation for the BJT in figure 4? Briefly explain your answer.
(5 marks)

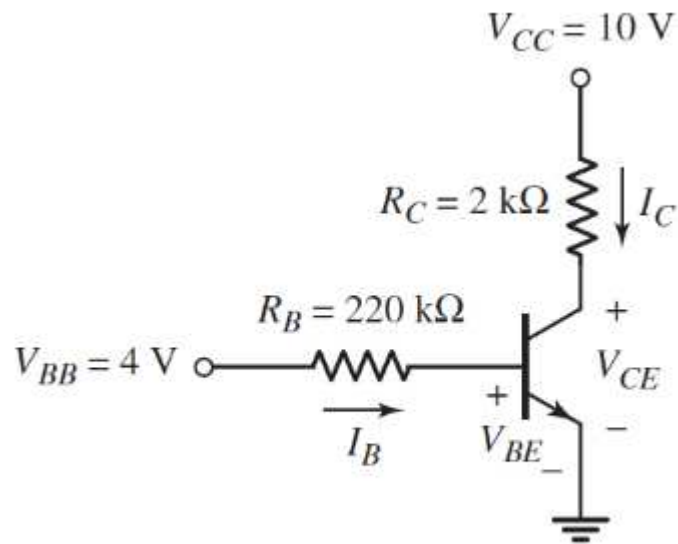


FIGURE 4. Common-emitter BJT circuit

- (c) For the NMOS transistor in Figure 3, determine the values of R_D and R_S so that the transistor operates at $i_D = 0.4\text{mA}$ and $V_D = +0.5\text{V}$. The NMOS transistor has $V_t = 0.7\text{V}$, $\mu_n C_{ox} = 100\mu\text{A/V}^2$, $L = 1\mu\text{m}$, and $W = 32\mu\text{m}$. Neglect the channel-length modulation effect (i.e., $\lambda = 0$).

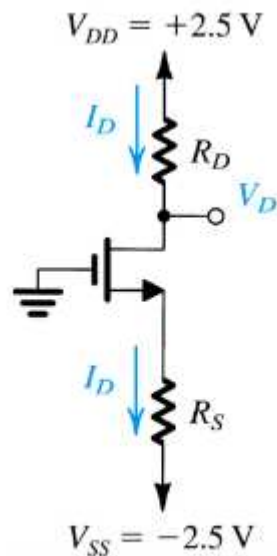


FIGURE 3. NMOS transistor

(6 marks)

- (d) For the network of Fig 2.188, determine the range of V_1 that will maintain V_L at 8 V and not exceed the maximum power rating of the Zener diode.


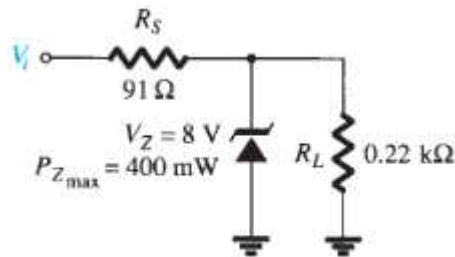


FIG. 2.188
Problems 44 and 52.

(4 marks)

QUESTION TWO (20 MARKS)

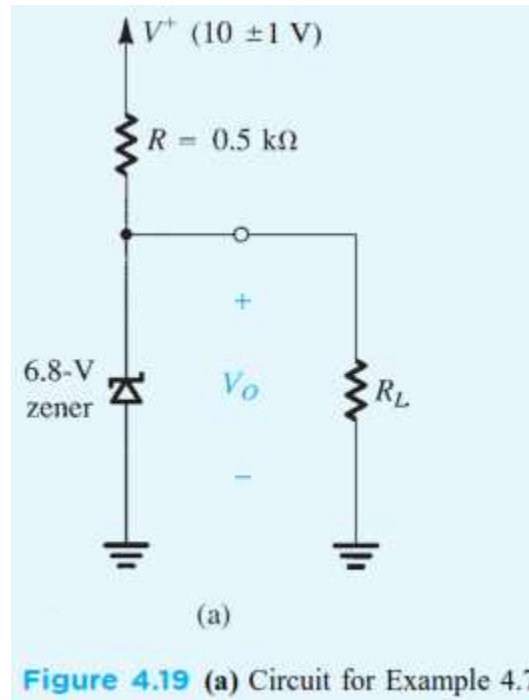- (a) The 6.8.V zener diode in the circuit of Fig. 4.19(a) is specified to have $V_Z=6.8\text{V}$ AT $I_Z=5\text{mA}$, $r_Z = 20\Omega$, and $I_{ZK}= 0.2 \text{ mA}$. The supply voltage V_+ is nominally 10 V but can vary by $\pm 1 \text{ V}$.
- Find V_o with no load and with V^+ and its nominal value.
 - Find the change in V_o resulting from the $\pm 1\text{-V}$ change in V^+ . Note that $(\Delta V_o/\Delta V^+)$, usually expressed in mV/V , is known line regulation.
 - Find the change in V_o resulting from connecting a load resistance R_L that draws a current $I_L = 1 \text{ mA}$, and hence find the load regulation $(\Delta V_o/\Delta I_L)$ in mV/mA
 - Find the change in V_o when $R_L = 2\text{k}\Omega$ (10 marks)



(10 marks)

- (b) A full-wave bridge rectifier with a 120-V rms sinusoidal input has a load resistor of 1 kΩ
- If silicon diodes are employed, what is the dc voltage available at the load?
 - Determine the required PIV rating of each diode.
 - Find the maximum current through each diode during conduction.
 - What is the required power rating of each diode?

(10 marks)


QUESTION THREE (20 MARKS)

- (a) An NMOS Transistor is fabricated in a 0.13 μm CMOS process (i.e., $L_{\min}=0.13\mu\text{m}$) with $L = 1.5 L_{\min}$, $W = 1.3 \mu\text{m}$. The process technology is specified to have an oxide layer $t_{\text{ox}}=2.7 \text{ nm}$, $\mu_n = 400 \text{ cm}^2 \text{ V}^{-1} \text{ s}$ and $V_{\text{tn}}=0.4\text{V}$
- Find the oxide capacitance, C_{ox} , the process trans-conductance, k'_n and the MOSFET transconductance parameter, K_n . The permittivity of the silicon dioxide, $\epsilon_{\text{ox}} = 3.45 \times 10^{-11} \text{ F} \cdot \text{m}^{-1}$

- ii. Find the overdrive voltage V_{ov} and the minimum value of V_{DS} required to operate the transistor in saturation at a current $I_D = 100\mu A$. What gate-to-source voltage is required? (12 marks)
- (b) An npn transistor having $I_S = 10^{-15} A$ and $\beta = 100$ is connected as follows: The emitter is grounded, the base is fed with a constant-current source supplying a dc current of $10\mu A$, and the collector is connected to a 5-V dc supply via a resistance R_C of $3 k\Omega$. Assuming that the transistor is operating in the active mode, find V_{BE} and V_{CE} . Use these values to verify active-mode operation. Replace the current source with a resistance connected from the base to the 5-V dc supply. What resistance value is needed to result in the same operating conditions? (8 marks)

QUESTION FOUR (20 MARKS)

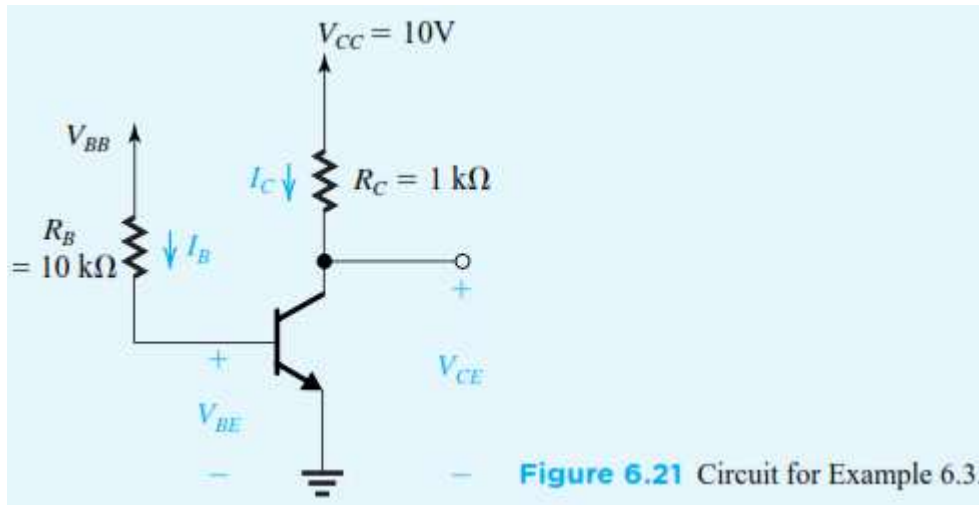- (a) Consider a process technology for which $L_{min} = 0.4\mu m$, $t_{ox} = 8nm$, $\mu_n = 450 cm^2/V \cdot s$, and $V_t = 0.7 V$.
- (i) Find C_{ox} and k'_n .
- (ii) For a MOSFET with $W/L = 8\mu m/0.8\mu m$, calculate the values of V_{OV} , V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 100\mu A$.
- (iii) For the device in (b), find the values of V_{OV} and V_{GS} required to cause the device to operate as a $1000-\Omega$ resistor for very small v_{DS} . (10 marks)
- (b) For the circuit in fig 6.21, it is required to determine the value of the voltage V_{BB} that result in the transistor operating
- (i) In the active mode with $V_{CE} = 5 V$
- (ii) at the edge of saturation
- (iii) deep in saturation with $\beta_{forced} = 10$
- For simplicity, assume that V_{BE} remains constant at $0.7 V$. The transistor β is specified to be 50.



(10 marks)

QUESTION FIVE (20 MARKS)

- (a) The NMOS transistor in the circuit in Figure 5 has $V_{tn} = 0.5\text{ V}$, $k'_n = 400\text{ }\mu\text{A V}^{-2}$, $W/L=10$ and $\lambda = 0$
- Find the transistors operating mode when $V_D = +0.5\text{ V}$;
(2 marks)
 - Find the required values of R_S and R_D to obtain $i_D = 180\text{ }\mu\text{A}$ and $V_D = +0.5\text{ V}$. Also, find the voltage V_S that results;
(4 marks)
 - What is the largest value to which R_D can be increased while the transistor remains in the saturation mode?
(4 marks)

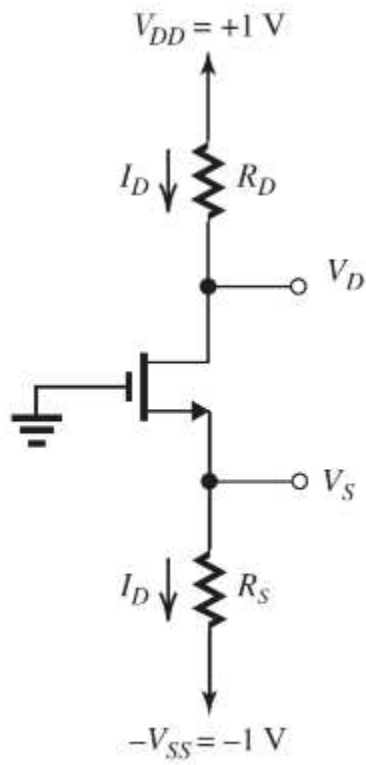


FIGURE 5

(b) The BJT figure 6 has $\beta = 100$, $V_{CE\text{Sat}} = 0.3$ V $V_B(\text{on}) = 0.7$ V. Find V_E , V_C and I_B and the transistors mode of operation:

(i) When $V_B = 0$ V;

(3 marks)

(ii) When $V_B = 3$ V;

(3 marks)

(iii) When $V_B = 5$ V

(4 marks)

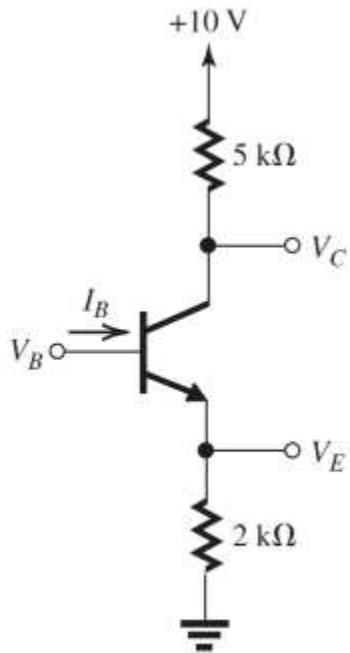


FIGURE 6

(10 marks)

END