



MACHAKOS UNIVERSITY

University Examinations for 2020/2021

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONICS

ENGINEERING

EEE 305: DIGITAL ELECTRONICS I

DATE: 11/8/2021

TIME: 8:30 – 10:30 AM

INSTRUCTIONS TO STUDENTS

1. This paper contains 5 questions.
2. Attempt **Question One** and **Any Other Two questions**

QUESTION ONE(COMPULSORY)(30 MARKS)

- a) Perform the following binary operation: $11.001_2 + 0.11011_2 + 111.111_2$
(2 marks)
- b) Perform the following operation using 9's complement subtraction:
 $125.35_{10} - 94.7_{10}$
(3 marks)
- c) Convert $D2763_{16}$ to decimal.
(2 marks)
- d) Simplify the logic function $f(A, B, C, D) = \sum_m (1, 3, 7, 11, 15) + d(0, 2, 5)$ using the Quine-McCluskey method.
(7 marks)
- e) Using the following truth table below,
 - (i) Derive the Boolean expression representing the function Y using products of sum.
(2 marks)
 - (ii) Draw the simplest circuit possible
(4 marks)

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

where A, B and C are the inputs and Y is the output.

- f) Perform the following binary subtraction using 1's complement arithmetic
 $10111.1_2 - 10011.1_2$ (3 marks)
- g) Perform the following operation in BCD: $89_{10} + 276_{10}$ (2 marks)
- h) Prove the following identity: $AB + \overline{AC} + A\overline{BC}(AB + C) = 1$ (5 marks)

QUESTION TWO (20 MARKS)

- a) With the aid of a well labelled diagram, explain the implementation of NAND gate using TTL logic family with a totem pole output. (7 marks)
- b) Obtain the minimal POS expression for the Boolean function given below using a K-map and implement the minimum expression using logic gates.
 $f(A, B, C, D) = \prod(3, 4, 6, 7, 11, 12, 13, 14, 15)$ (8 marks)
- c) With aid of a well labeled logic circuit and truth table, explain the operation of a clocked D flip-flop. (5 marks)

QUESTION THREE (20 MARKS)


- a) Perform the following BCD subtraction using 10's complement:
 $75E_{16} - 87_{10}$. (3 marks)
- b) Differentiate between synchronous and asynchronous sequential circuits. (2 marks)
- c) Draw a circuit diagram and a truth table of a J-K flip-flop and explain its operation. (7 marks)
- d) Simplify the following Boolean expressions: $AB + A\overline{BC}(\overline{BC} + C) + \overline{AC}$. (5 marks)
- e) Perform the following using binary multiplication: $11.11_2 \times 0.111_2$ (1½ marks)
- f) Perform the following binary division: $10.01_2 \div 1.1_2$ (1½ marks)

QUESTION FOUR (20 MARKS)


- a) A 4-bit binary number is applied to a circuit on four lines A, B, C, D. The circuit has a single output, F, which is true if the number is in the range three to twelve, inclusive.
- (i) Draw a truth table to represent the problem (3 marks)
 - (ii) Use the K-map to obtain a simplified expression for the function (4 marks)
 - (iii) Construct a circuit to implement the simplified expression in (ii) above using NAND gate only. (3 marks)
- b) Briefly explain the following terms:-
- (i) Registers
 - (ii) Shift-registers (4 marks)
- c) With the aid of logic symbols and truth tables, explain the operation of the following two-input gates.
- (i) NOR
 - (ii) XOR (6 marks)

QUESTION FIVE (20 MARKS)

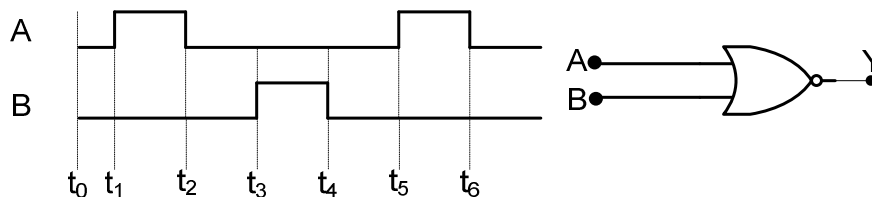- a) The figure below shows the two waveforms applied to the NOR gate. Determine the resulting output waveform. (4 marks)



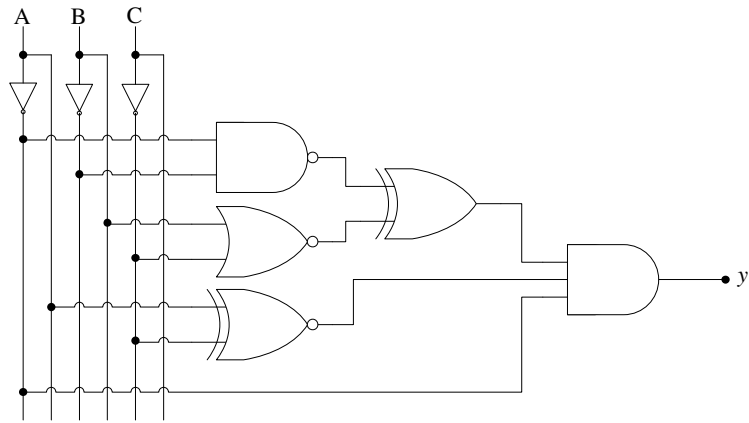- b) Differentiate between combinational and sequential circuits. (5 marks)
- c) Determine the Boolean expression and the truth table for the output of the logic circuit shown below. (4 marks)



- d) Explain any four advantages of digital systems over analogue systems (4 marks)
- e) Use 2's complement to subtract 1101_2 from 1010_2 (3 marks)