



MACHAKOS UNIVERSITY

University Examinations 2019/2020 Academic year

SCHOOL OF PURE AND APPLIED SCIENCES

DEPARTMENT OF PHYSICAL SCIENCES

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF EDUCATION (SCIENCE)

SPH 304: A.C. CIRCUIT THEORY

DATE: 4/12/2019

TIME: 2.00-4.00 PM

INSTRUCTIONS TO CANDIDATES

*This paper consists of **FIVE** questions in **FIVE** printed pages. Answer **Question One** (compulsory) and any **TWO** questions from the rest of the questions.*

QUESTION ONE (30 MARKS)

- a) Define the following quantities and state their SI units
- i. Admittance (2 marks)
 - ii. Susceptance (2 marks)
- b) If the current in a series RL circuit is given by $i = 10 \sin (1.0 \times 10^3 t - 25^\circ)$ ampere and the applied e.m.f is given by $e = 400 \sin (1.0 \times 10^3 t + 20^\circ)$ volts, what are the values of R and L ? (5 marks)
- c) A transmission line has the following per-unit-length parameters: $L = 0.5 \mu\text{H/m}$, $C = 200 \text{ pF/m}$, $R = 4.0 \Omega/\text{m}$, and $G = 0.02 \text{ S/m}$. Calculate the following parameters of the line at 800 MHz:
- i. the propagation constant γ , and (3 marks)
 - ii. the characteristic impedance Z_0 . (3 marks)
 - iii. If the line is 30 cm long, what is the attenuation in dB? (3 marks)

- d) A 100- Ω transmission line is connected to a load consisting of a 50- Ω resistor in series with a 10-pF capacitor as shown in Fig. 1.1. Find the reflection coefficient at the load for a 100-MHz signal. (3 marks)

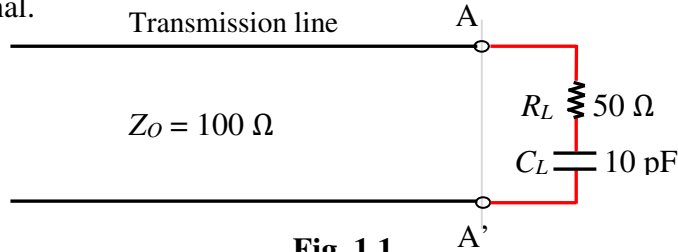


Fig. 1.1

- e) Two circuits with impedances of $Z_1 = 10 + j15 \Omega$ and $Z_2 = 6 - j8 \Omega$ are connected in parallel. If the total current supplied is 15A, determine,
- Power taken by each branch (4 marks)
 - Power factor for the combination (3 marks)
 - Draw the circuit vector diagram. (2 marks)

QUESTION TWO (20 MARKS)

- a) Define the following terms as used in transmission lines
- Propagation constant (2 marks)
 - Characteristic impedance (2 marks)
- b) A transmission line has the propagation constant $\gamma = 0.1 + j10 \text{ /m}$, and characteristic impedance $Z_0 = 50 + j5 \Omega$. The line is terminated with impedance $100 - j30 \Omega$. Find the impedance at a distance of 1.5 m from the load. (4 marks)
- c) A series RLC circuit consists of a 100 Ω resistor, an inductor of 0.318 H and a capacitor of unknown value. When this circuit is energized by $230\sqrt{2} \sin 100\pi t$ volts a.c. supply, the current is found to be $2.3\sqrt{2} \sin 100\pi t$. Find:
- The value of capacitor in microfarads. (3 marks)
 - Voltage across the inductor. (2 marks)
 - The total power consumed. (2 marks)
- d) If a variable frequency e.m.f. is applied to a series RLC circuit consisting of $R = 5 \Omega$, $L = 200 \text{ mH}$ and $C = 0.05 \mu\text{F}$, determine the values of angular frequency ω for which the current will
- be in-phase with applied voltage (2 marks)
 - lead the applied voltage by 30° (3 marks)

QUESTION THREE (20 MARKS)

- a) Define the following terms as used in RLC circuits
- Resonance (2 marks)
 - Q-Factor (2 marks)
- b) Figure 3.1 shows a transmission line with voltage input $v(x, t)$ and lumped components as functions of time and distance (x, t) : resistance R , inductance L , conductance G and capacitance C per unit length. Derive the second derivative of current wave motion $i(x, t)$ with respect to the distance, in terms of the propagation constant γ . (8 marks)

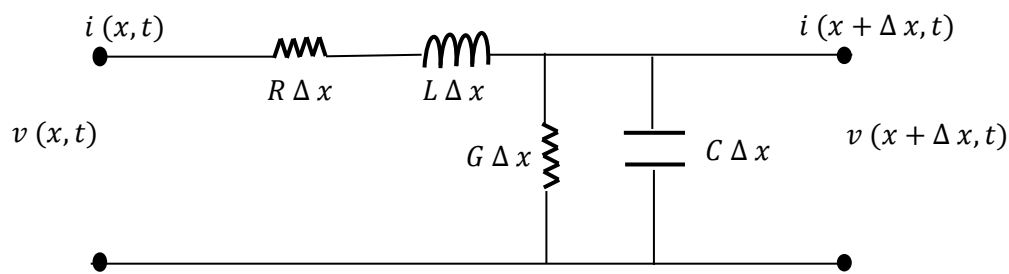


Fig. 3.1 1

- c) One resistor R_1 is connected in parallel with an inductor L , this connection is in series with another parallel connection of resistor R_2 and capacitor C as shown in Fig 3.1 2. The entire connection is in resonance. Determine the resonance frequency f of the network in terms of R_1 , R_2 , L and C . (8 marks)

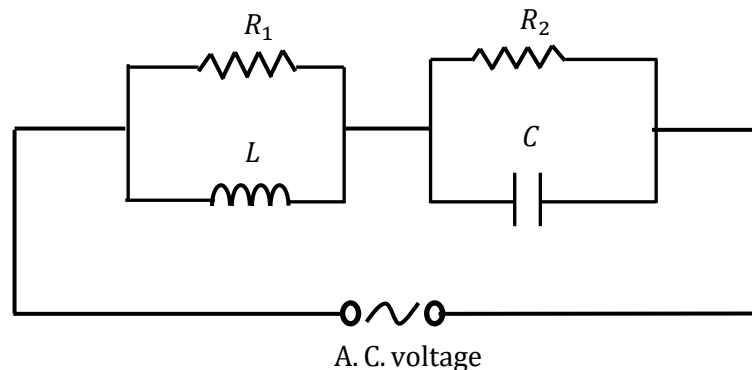


Fig. 3.1 2

QUESTION FOUR (20 MARKS)

- a) With the aid of diagrams, distinguish between the following types of transmission lines
- i. Co-axial line (2 marks)
 - ii. Open line wire (2 marks)
- b) A two-wire air-line has the following line parameters: $R = 0.404 \text{ (m}\Omega \text{ /m)}$, $L = 2.0 \text{ (}\mu\text{H/m)}$, $G = 0$, and $C = 5.56 \text{ (pF/m)}$. For operation at 5 kHz, determine
- i. the attenuation constant α , (4 marks)
 - ii. the phase constant β , (3 marks)
 - iii. the characteristic impedance Z_0 (3 marks)
- c) If the current in a series RC circuit is given by $i = 2 \cos (1000t + 10^\circ)$ ampere and the applied voltage is given by $e = 100 \cos (1000t + 55^\circ)$ volts, what are the values of R and C? (6 marks)

QUESTION FIVE (20 MARKS)

- a) What do you understand by the following terms
- i. Electrical filter circuits (2 marks)
 - ii. Cut-off frequency of a filter circuit (2 marks)
- b) A high-pass RC filter consists of a $100 \text{ k}\Omega$ resistor and a 50-pF capacitor.
- i. What is the cut-off frequency f_c of the filter? (2 marks)
 - ii. What is the ratio of the peak output voltage and peak input voltage at frequency of $0.1 f_c$? (2 marks)
 - iii. At what frequency is the peak output voltage one half the peak input voltage? (3 marks)
- c) Two admittances, $Y_1 = (0.167 - j0.167) \text{ S/m}$, and $Y_2 = (0.1 + j0.05) \text{ S/m}$ are connected across a 100 V , 50 Hz single-phase supply. Find
- i. the current in each branch and the total current. (4 marks)
 - ii. the power factor of the combination. (3 marks)
 - iii. Sketch a neat phasor diagram. (2 marks)