



MACHAKOS UNIVERSITY

University Examinations for 2020/2021


SCHOOL OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
FIRST YEAR SECOND SEMESTER EXAMINATION FOR
DIPLOMA IN ELECTRICAL ENGINEERING
ELECTRICAL MEASUREMENTS

DATE: 30/8/2021

TIME: 2:30 – 5:30 PM

INSTRUCTIONS: answer question and any other two questions

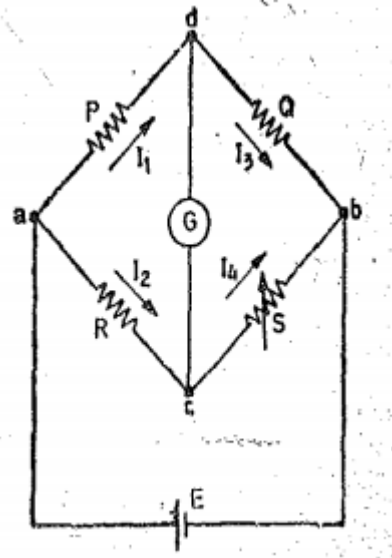1. a) i) State two advantages of SI units (2 marks)
 ii) Explain what is meant by a measurement (3 marks)
 b) i) Define the term maintenance as used in electrical equipment
 ii) State any three benefits of preventive maintenance. (5 marks)
 c) i) Name three types of solder
 ii) Explain what soldering is as used in electrical measurements (6 marks)
 iii) Explain the following types of errors stating how they are minimized
 i) Systematic
 ii) Gross (4 marks)
2. a) i) Name four ways of measuring resistances
 ii) Explain how a Ammeter - Voltmeter instrument measure resistances. (8 marks)
 c) A Wheatstone bridge has resistors $P=Q=R=S=1K\Omega$. The Galvanometer, G, can detect as low as 0.1mA. Determine the;
 i) Internal resistance of the bridge measured across terminals b-d
 ii) Output voltage due to unbalance
 iii) Current through the galvanometer for unbalance condition
 iv) Smallest change in resistance that can be detected




(12 marks)

3. a) i) Explain what primary units means in measurements.
 ii) The dimensional equation of resistance in the LMTI system of dimensions is $[R] = [ML^2I^{-2}T^{-3}]$. Use this equation to obtain the dimensions.
 (10 marks)
- b) Derive the dimensional equation for capacitance in c. g. s. electrostatic units. Take the dimensional equation for charge $[Q] = [\epsilon^{1/2} M^{1/2} L^{3/2} T^{-1}]$ (10 marks)
4. a) Show that, from a Carey Foster slide wire bridge, a linear relationship exists between two adjacent resistors separated by a wire of known length and known resistance per unit.
 (10 marks)
- b) An unknown inductance L_u is measured using a deflection type of bridge as shown in the figure below.

The components in the bridge have the following values:

$$V_s = 10 \text{ V r.m.s.}, L_1 = 20 \text{ mH}, R_2 = 100 \Omega, R_3 = 100 \Omega$$

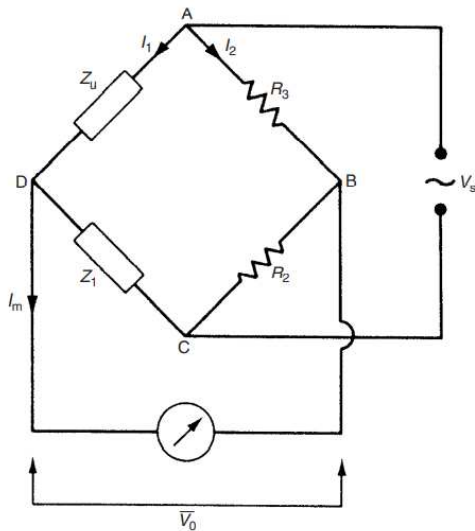
If the output voltage V_0 is 1 V r.m.s., calculate the value of L_u .



(5 marks)

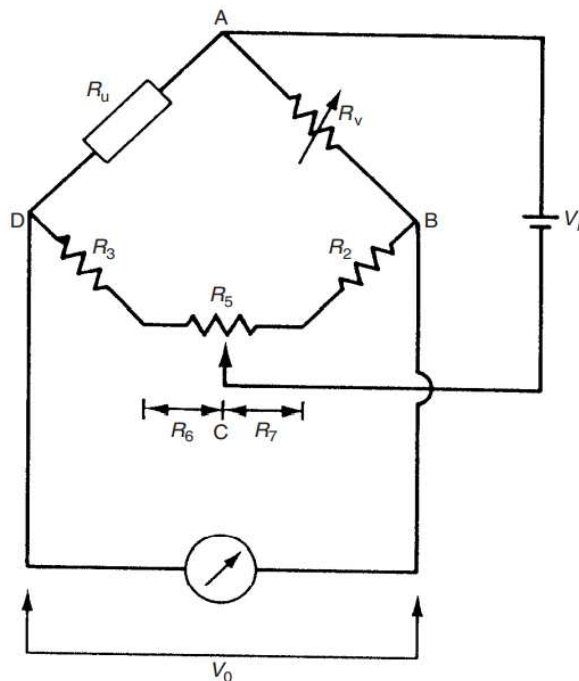- c) A potentiometer R_5 is put into the apex of a bridge as shown below to balance the circuit. The bridge components have the following values:

$R_u = 500 \, \Omega$, $R_v = 500 \, \Omega$, $R_2 = 515 \, \Omega$, $R_3 = 480 \, \Omega$, $R_5 = 100 \, \Omega$.



Determine the required value of the resistances R_6 and R_7 of the parts of the potentiometer track either side of the slider in order to balance the bridge and compensate for the unequal values of R_2 and R_3 .

(5 marks)

5. a) i) Explain the three **(3)** classified categories of drifts. (3 marks)
- ii) Explain how a galvanometer can be converted to measure a
- i) Current
- ii) Voltage (4 marks)
- b) i) A 5Ω galvanometer with a full scale deflection of 10mA is used to measure a current of 10A. Calculate the value of the shunt resistance needed. (5 marks)
- ii) A moving-coil instrument having a resistance of 10Ω , gives a f.s.d. when the current is 8 mA. Calculate the value of the multiplier to be connected in series with the instrument so that it can be used as a voltmeter for measuring p.d.s. up to 100V. (4 marks)
- iii) In a Wheatstone bridge circuit, calculate the unknown resistor given that $R_1 = 300\Omega$, $R_2 = 150\Omega$ and $R_3 = 250\Omega$ named clockwise. (4 marks)