



MACHAKOS UNIVERSITY

University Examination 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)

EEE 306: DIGITAL ELECTRONICS II

DATE: 23/5/2019

TIME: 8.30-10.30 AM

INSTRUCTIONS

Answer Question ONE and any other TWO Questions.

QUESTION ONE (30 MARKS)

- a) Implement the function below using 4×1 multiplexer. Apply x and y to the select lines.

$$F(x,y,z) = \sum m(1, 2, 6, 7) \quad (5 \text{ marks})$$

- b) Draw the block diagram representation of a 8-Word×4-Bit ROM and give its truth table.

(5 marks)

- c) List down the three types of ROM devices and explain the differences between them.

(6 marks)

- d) Prepare the PLA programming table for the following functions.

(4 marks)

$$F_0 = A'B' + AC'$$


$$F_1 = AC' + B$$

$$F_2 = A'B' + BC'$$

$$F_3 = B + AC$$


- e) A counter is first described by a state diagram, which shows the sequence of states through which the counter advances when it is clocked. The figure below shows a state diagram of a 3-bit binary counter. Design the counter using JK flips flops.

(10 marks)

 

 QUESTION TWO (20 MARKS)


- Show the gate level implementation of a 1-to-4 demultiplexer. Draw the circuit diagram and explain how it works. (5 marks)
- Draw the circuit diagram of a full adder and explain its working using a truth table. (5 marks)
- Design a 3-bit counter that advances through the sequence 000, 010, 011, 101, 110, 000 and repeats. Not all of the possible combinations of the 3 bits represent a valid state. The unused states, 001, 100, and 111, should be used as don't-care conditions to simplify the logic. Use T flip flops. (6 marks)
- The R-2R ladder network uses resistors of only two sizes, R and 2R. Derive an expression for the output voltage of the R-2R ladder network shown below. (4 marks)



QUESTION THREE (20 MARKS)

- a) Design a MOD-5, 3-bit synchronous counter to count in the following sequence: 2, 3, 5, 1, 7. The counter must be self-starting with the count states of 0, 4, and 6 leading directly to 2. The operation of the counter is shown in the state diagram below. Use JK flip flops.

(6 marks)

 

- b) Design a counter with the following counting sequence: 0, 1, 2, 4, 6 and repeat. Use D-flip flops. Do not use a decoder in your design. Treat the unused states as don't cares in your design. (6 marks)
- c) Draw the internal logic of a 32x8 ROM. (4 marks)
- d) Design a combinational circuit using a ROM. The circuit accepts a three bit number and outputs a binary number equal to the square of the input number. (4 marks)

QUESTION FOUR (20 MARKS)

- a) Tabulate the PLA programming table for the four Boolean functions listed below. Minimize the product terms. (6 marks)

$$A(x, y, z) = \sum(1, 2, 4, 6)$$

$$B(x, y, z) = \sum(0, 1, 6, 7)$$

$$C(x, y, z) = \sum(2, 6)$$

$$D(x, y, z) = \sum(1, 2, 3, 5, 7)$$

- b) Tabulate the truth table for a 8x4 ROM that implements the Boolean functions listed below. Considering now the ROM as a memory, specify the memory contents at addresses 1 and 4. (4 marks)

$$A(x, y, z) = \sum(0, 3, 4, 6)$$

$$B(x, y, z) = \sum(0, 1, 3, 7)$$

$$C(x, y, z) = \sum(1, 5)$$

$$D(x, y, z) = \sum(0, 1, 4, 5, 7)$$

- c) The following is a table of a three-input, four-output combinational circuit. Tabulate the PAL programming table for the circuit and mark the fuse map in a PAL diagram.

(6 marks)

Inputs			Outputs			
<i>x</i>	<i>y</i>	<i>z</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>
0	0	0	0	1	0	0
0	0	1	1	1	1	1
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	0	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1

- d) What are the differences between static RAM and dynamic RAM? (4 marks)

QUESTION FIVE (20 MARKS)

- a) A 6-bit Dual Slope A/D converter uses a reference of $-6V$ and a 1 MHz clock. It uses a fixed count of 40 (101000). Find Maximum Conversion Time. (4 marks)
- b) Determine the analog output voltage of 6-bit DAC (R-2R ladder network) with V_{ref} as 5V when the digital input is 011100 (4 marks)
- c) A 6-bit R-2R ladder D/A converter has a reference voltage of 6.5V. It meets standard linearity. Find
- The Resolution in Percent.
 - The output voltage for the word 011100. (4 marks)
- d) Find the conversion time of a Successive Approximation A/D converter which uses a 2 MHz clock and a 5-bit binary ladder containing 8V reference. What is the Conversion Rate? (4 marks)
- e) A microprocessor uses RAM chips of 1024×1 capacity.
- How many chips will be required and how many address lines will be connected to provide capacity of 1024 bytes.
 - How many chips will be required to obtain a memory of capacity of 16 K bytes? (4 marks)