



MACHAKOS UNIVERSITY COLLEGE

**(A Constituent College of Kenyatta University)
University Examinations for 2015/2016 Academic Year**

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**SECOND SEMESTER EXAMINATION FOR DIPLOMA IN MECHANICAL ENGINEERING
DIPLOMA IN ELECTRICAL AND ELECTRONICS ENGINEERING**

EED 113: ANALOGUE ELECTRONICS 1

DATE: 4/8/2016

TIME: 2:00 – 4:00 PM

INSTRUCTIONS:

Answer Question One and Any Two Questions from Section B

1. a) With the aid of well labeled diagrams, explain the Bohr atomic structures of the following elements.
 - i. Conductors
 - iii. Semi conductors(4 marks)
- b) Explain the effect of temperature on a semi conductor under the following conditions
 - i) Below zero degrees
 - ii) At absolute zero
 - iii) Above absolute zero(6 marks)

- c) i) With the aid of well labeled diagrams, explain the formation of a P-N junction (6 marks)
- ii) If an external voltage is added to the P-N junction in (i) above, explain what could be the effect. (4 marks)
- d) With the aid of a circuit diagram, explain the operation of a single stage amplifier (10 marks)

SECTION B: ANSWER ANY OTHER TWO QUESTIONS

2. a) Explain three properties of semi conductors. (6 marks)
- b) Differentiate between Intrinsic semiconductors and Extrinsic semiconductors (4marks)
- c) i) Calculate the operating point of a transistor whose collector load is $8k\Omega$ and the transistors' quiescent current is 2mA. Take VCC as 20V. (6 marks)
- ii) If RC was to be put to $10K\Omega$, what could be the operating point of the transistor in (i) above (4 marks)
3. a) i) In a common base connection the emitter current is 10mA. If the emitter circuit is open, the collector current is 100mA. Find the total collector current given that $\alpha = 0.98$ (6 marks)
- ii) With respect to a common emitter connection, derive the relationship between β and α . (6 marks)
- b) Find the values of collector and emitter currents in a transistor having $ICBO=3\mu A$, and $dc = 0.98$ when its base current is $60\mu A$. (8 marks)
4. a) With the aid of well labeled diagram, explain the V-I characteristics on the following considerations:-
- i) Forward biasing
- ii) Reverse biasing (12 marks)

- b) Explain the effect of using filters along with rectifier's output waveforms. (8 marks)
5. a) What are the advantages of the FET over a conventional bipolar junction transistor? (4 marks)
- b) Define Pinch off voltage, transconductance, amplification factor and drain resistance of a FET. (8 marks)
- c) Explain with the help of circuit diagram how an FET is used as a voltage amplifier and as voltage dependent resistor (VDR). (8 marks)