



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)

EEE 307: NETWORK ANALYSIS & SYNTHESIS

DATE: _____


TIME: _____

INSTRUCTIONS TO STUDENTS

1. This paper contains 5 questions.
2. Attempt **Question One** and **Any Other Two** questions
3. Show calculations where applicable

QUESTION ONE (30 MARKS)

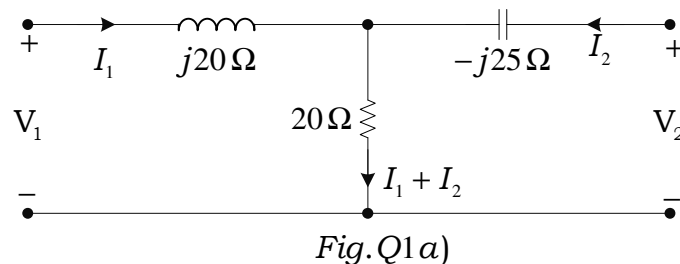- a) Determine the Z-parameters of the network shown in Fig. Q1 a). (8 marks)



- b) Given that the desired specifications of a Chebyshev Type I lowpass filter are as follows: $\alpha_{\max} = 0.85 \text{ dB}$, $\alpha_{\min} = 35 \text{ dB}$, $\omega_p = 3,500 \text{ rad/s}$, and $\omega_s = 7,500 \text{ rad/s}$, design the filter the meet the specifications given. (9 marks)
- c) Sketch the Chebyshev type I attenuation response for $n = 6$ (2 marks)
- d) Test whether the polynomial $F(s)$ is a Hurwitz polynomial. (5 marks)

$$F(s) = s^4 + s^3 + 5s^2 + 3s + 4$$

e) Synthesize the following impedance function using basic synthesis procedures:

$$Z(s) = \frac{s^2 + 6s + 60}{s(s+10)} \quad (6 \text{ marks})$$

QUESTION TWO (20 MARKS)

a) Given the following specifications of a low pass filter: $\alpha_{\max} = 0.4$, $\alpha_{\min} = 12 \text{ dB}$, $\omega_p = 1000 \text{ rad/s}$, $\omega_s = 2200 \text{ rad/s}$. Design the filter with a Butterworth response that satisfy the above specifications and show the poles on an s-plane. (7 marks)

b) Test whether the following functions satisfy analog filter design theorem. (6 marks)

$$Z(\omega) = \frac{\omega^2 + 7\omega + 10}{\omega^2 + 5\omega + 4}$$

c) For the circuit shown in Fig. Q2 c), Use ladder network method to find

(i) the transfer impedance $V_1(s)/I_1(s)$

(ii) the voltage ratio $V_2(s)/V_1(s)$ (7 marks)

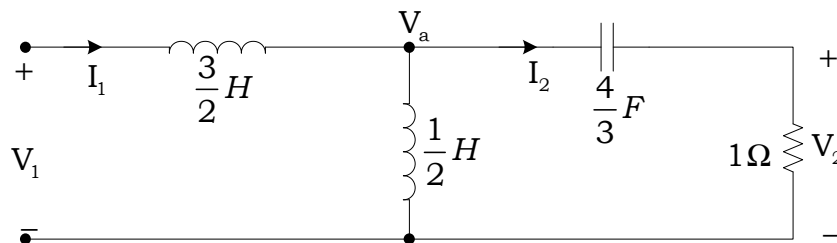


Fig. Q2 c)

QUESTION THREE (20 MARKS)

a) Briefly explain the following terms as used in network synthesis:

(i) Causality

(ii) Hurwitz polynomials

(iii) Positive real functions

(3 marks)

b) Test whether the following function is a positive real function: $F(s) = \frac{s+3}{s(s+1)(s+2)}$

(5 marks)

c) Synthesis the following LC network in Foster form I: $Z(s) = \frac{s(s^2 + 9)(s^2 + 25)}{(s^2 + 4)(s^2 + 16)}$

(8 marks)


d) State the Four properties of an RC network.

(4 marks)

QUESTION FOUR (20 MARKS)

a) Find the h-parameters for the circuit shown in Fig. Q4 a).

(10 marks)

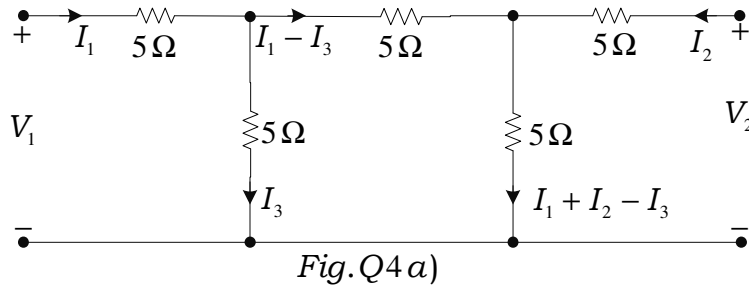

b) Synthesize the RC impedance function using Cauer form II:

$$Z(s) = \frac{3(s+2)(s+4)}{s(s+3)} \quad (5 \text{ marks})$$

c) State the **Five** properties of an LC networks.

(5 marks)

QUESTION FIVE (20 MARKS)

a) Design an inverse Chebyshev low pass filter to satisfy the following specifications: $\alpha_{\max} = 0.3 \text{ dB}$, $\alpha_{\min} = 22 \text{ dB}$, $\omega_s = 3000 \text{ rad/s}$ and $\omega_s = 1000 \text{ rad/s}$

(11 marks)

b) Synthesize the following RL function using first Cauer form:

$$Z(s) = \frac{s(s+4)(s+6)}{(s+2)(s+5)} \quad (9 \text{ marks})$$