



# MACHAKOS UNIVERSITY COLLEGE

(A Constituent College of Kenyatta University)  
University Examinations for 2015/2016 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST SEMESTER EXAMINATION FOR DIPLOMA IN TELECOMMUNICATION  
ENGINEERING

EED 101: ELECTRICAL ENGINEERING PRINCIPLES 1

DATE:

TIME:

---

## INSTRUCTIONS

**Attempt Question ONE And Any Other Two Questions**

1.
  - (a)
    - (i) Two resistors  $R_1$  and  $R_2$  connected in parallel. Using the current-divider rule write the expressions for current through each resistor.
    - (ii) Three resistors connected in parallel have a total resistance of  $60\ \Omega$ . The resistances of two of the resistors are  $15\ \Omega$  and  $20\ \Omega$ . If the supply voltage is  $240\text{ V}$  and the circuit is operated for 2 minutes. Determine ;
      - I. The resistance of the third resistor
      - II. Power developed in the circuit
      - III. Energy dissipated (8 marks)
  - (b)
    - (i) State the Kirchhoff's laws
    - (ii) Figure 1 shows an electrical network .By means of the Kirchhoff's laws calculate the
      - I. Supply current,  $I$

II. Supply voltage, E.

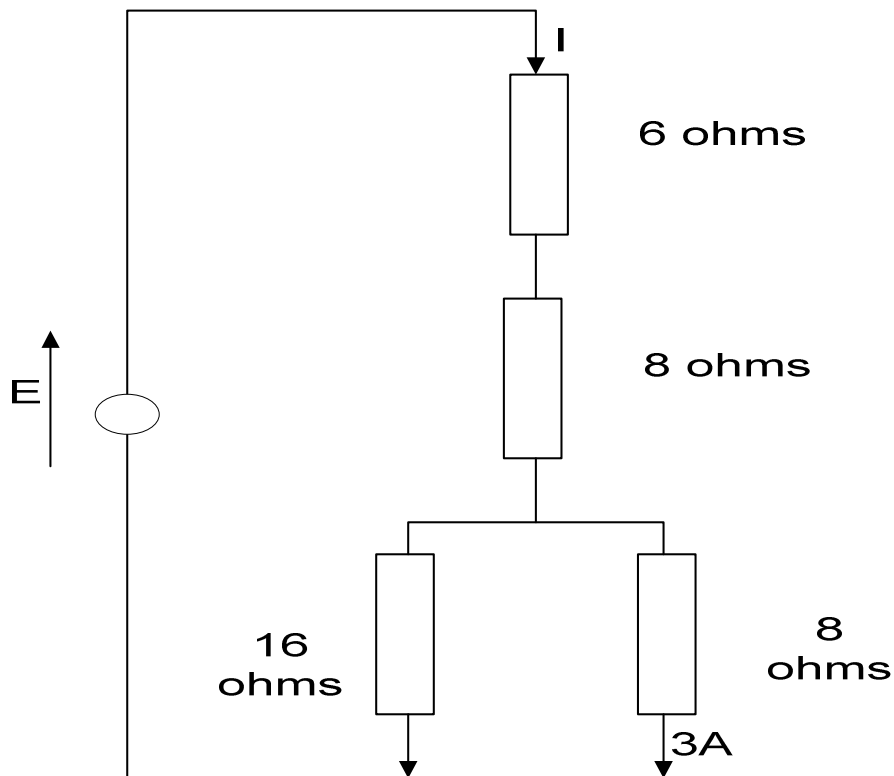


Fig 1

(8 marks)

- (c) (i) Describe the principle of operation of a the wireless battery charging
- (ii) State four characteristics of lines of magnetic flux. (8 marks)
- (d) A circuit consisting of two capacitors  $18\ \mu\text{F}$  and  $32\ \mu\text{F}$  connected in series are supplied by a 12V dc source. Determine for the circuit;
- I. total capacitance
- II. voltage across each capacitor
- II. energy in the  $18\ \mu\text{F}$  capacitor (6 marks)

2. (a) (i) Explain the effect of temperature on conduction on semiconductors.
- (ii) Explain the term ‘ temperature coefficient of resistance’ (6 marks)
- (b) The primary winding of a transformer is connected to a 240 V supply. When the copper winding is 22 °C, the current is 2 A. After the transformer is operated for some hours, the current fell to 1.8A ,the voltage remaining unaltered. Assuming the temperature coefficient of resistance of copper to be 0.00426/°C .Determine the temperature the winding after this duration. (5 marks)
- (c) (i) a circuit has two resistors 1 K $\Omega$  and 2.2 K $\Omega$  in parallel connected in series with a 3.3 K $\Omega$  resistor. The network is supplied by a 10 V dc source. Determine;
- I. total resistance
- II. supply current
- III. power (6 marks)
- (ii) A conductor 100 metres long has a of diameter 0.5mm. If the conductor has a resistance of 300 $\Omega$ . Determine the resistivity of the conductor material. (3 marks)
3. (a) (i) State Faraday’s induction law
- (ii) A copper conductor 20 cm long is carrying current of 15 A. If the conductor is placed in a magnetic field with density 0.5 T. Calculate the force on the conductor. (4 marks)
- (b) (i) Define the following terms with respect to electrostatics;
- I. Dielectric
- II. Absolute permittivity
- (ii) A capacitor is made of three metal plates separated by a 2 mm thick mica sheet . The area of each plate is 400 cm<sup>2</sup>. If mica has relative permittivity of 5 and absolute permittivity is 8.85 X 10<sup>-12</sup> F/m and a p.d of 110 V is maintained across the terminals of the capacitor. Calculate
- (i) capacitance
- (ii) charge

- (iii) electric field strength
- (iv) energy stored (12 marks)

(iii) Describe an experiment to confirm presence of lines of magnetic flux.

(4 marks)

4. (a) (i) Distinguish between primary and secondary cells
- (ii) State four measures when handling lead acid batteries (6 marks)
- (b) With an aid of a labeled diagram describe the application of a syringe hydrometer in lead acid battery checks. (6 marks)
- (c) A coil of 400 turns is wound uniformly over a wooden ring having a mean circumference of 500mm and a uniform cross-sectional area of  $800 \text{ mm}^2$ . If the current through the coil is 2 A and permeability of free space is  $4\pi \times 10^{-7} \text{ H/m}$ . Calculate the;
- (i) magnetic field strength
  - (ii) flux density
  - (iii) total flux (8 marks)

5. (a) (i) State the superposition theorem
- (ii) Figure 2 shows an electrical network .By means of superposition theorem, calculate the currents  $I_1, I_2$  and  $I_3$ .

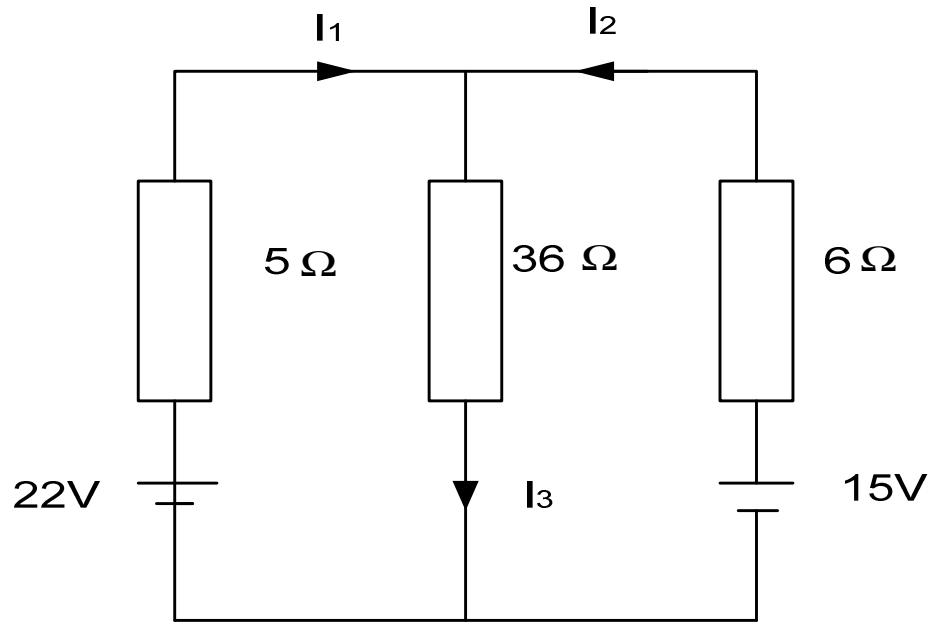


Fig 2

(10 marks)

(b) Draw labeled diagrams of each of the following battery charging systems.

- i. Constant voltage
- ii. Constant current

(10 marks)