



MACHAKOS UNIVERSITY

University Examinations 2020/2021 Academic Year

SCHOOL OF PURE AND APPLIED SCIENCES

DEPARTMENT OF PHYSICAL SCIENCES

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF EDUCATION (SCIENCE)

SPH 304: AC CIRCUIT THEORY

DATE: 13/8/2021

TIME: 2.00-4.00 PM

INSTRUCTIONS:

- The paper consists of **two** sections.
- Section **A** is **compulsory** (30 marks).
- Answer any **two** questions from section **B** (each 20 marks).

SECTION A

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Define the following quantities and state their SI units
- i. Impedance (2 marks)
 - ii. Susceptance (2 marks)
- b) A transmission line has the following parameters measured per-unit-length: $L = 0.5 \mu\text{H}/\text{m}$, $C = 200 \text{ pF}/\text{m}$, $R = 4.0 \Omega/\text{m}$, and $G = 0.02 \text{ S}/\text{m}$. Calculate the following parameters of the line at 800 MHz:
- i. The propagation constant γ , and (3 marks)
 - ii. The characteristic impedance Z_0 . (3 marks)
- c) If the current in a series RL circuit is given by $i = 10 \sin (1.0 \times 10^3 t - 25^\circ)$ amperes and the applied e.m.f is given by $e = 400 \sin (1.0 \times 10^3 t + 20^\circ)$ volts, calculate the values of R and L . (6 marks)

- d) Two circuits with impedances of $Z_1 = 10 + j15 \Omega$ and $Z_2 = 6 - j8 \Omega$ are connected in parallel. If the total current supplied is 15A, determine,
- Power taken by each branch (4 marks)
 - Power factor for the combination (4 marks)
 - Draw the circuit vector diagram. (3 marks)
- e) A 100- Ω transmission line is connected to a load consisting of a 50- Ω resistor in series with a 10-pF capacitor as shown in Figure 1, calculate the reflection coefficient of a 100-MHz signal at the load end. (3 marks)

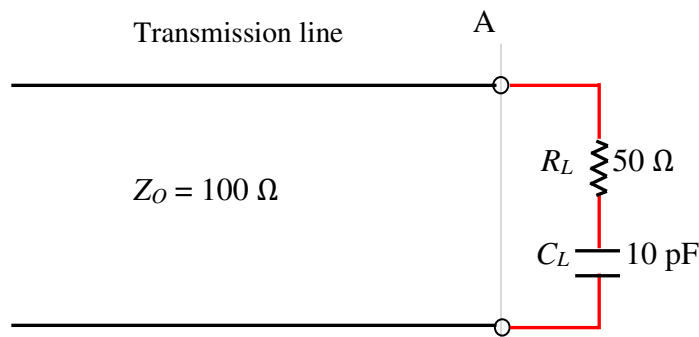


Figure 1

SECTION B

QUESTION TWO (20 MARKS)

- a) Define the following terms for series AC circuits
- Resonance (2 marks)
 - Q-factor (2 marks)
- b) A 15 mH inductor is in series with a parallel combination of an 80 Ω resistor and a 20 μF capacitor. If the angular frequency of the applied voltage is $\omega = 1000 \text{ rad/s}$, calculate the admittance of the network. (3 marks)
- c) For the RC series circuit shown in Figure 2, determine the frequency of the ideal generator, if the current flowing in the circuit is 1 mA (r.m.s). (3 marks)

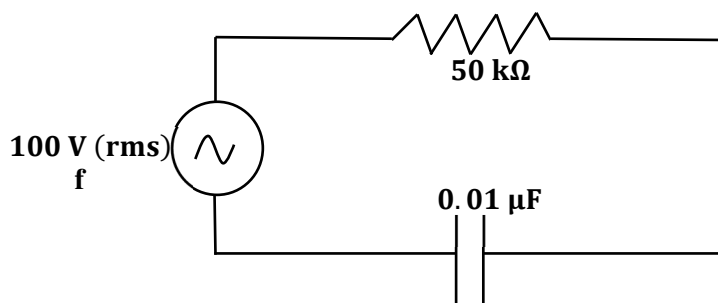


Figure 2

- d) A 32 V, 1000 Hz supply voltage is applied across a series connection of 100 ohm resistor, 400 mH inductor and 20 uF capacitor. Calculate
- The rms current in the circuit? (3 marks)
 - The phase angle between the voltage E and current I (3 marks)
- e) A generator whose internal resistance is $1\ \Omega$ furnishes an e.m.f of 10 V at a frequency of $\frac{10,000}{\pi}$ Hz. Design a series RLC circuit so that a potential difference of 1000 V may be developed across the capacitor. (4 marks)

QUESTION THREE (20 MARKS)

- a) Define the following terms as used in transmission lines
- Propagation constant (2 marks)
 - Characteristic impedance (2 marks)
- b) A transmission line has the propagation constant $\gamma = 0.1 + j10$ /m, and characteristic impedance $Z_0 = 50 + j5\ \Omega$. The line is terminated with impedance $100 - j30\ \Omega$. Determine the impedance at a distance of 1.5 m from the load. (4 marks)
- c) A series RLC circuit consists of a $100\ \Omega$ resistor, an inductor of 0.318 H and a capacitor of unknown value. When this circuit is energized by an a.c. supply of $230\sqrt{2} \sin 100\pi t$ volts, a current of $2.3\sqrt{2} \sin 100\pi t$ flows. Calculate: -
- the value of capacitor in microfarads. (3 marks)
 - the voltage across the inductor. (3 marks)
- d) If an e.m.f. of variable frequency is applied to a series RLC circuit consisting of $R = 5\ \Omega$, $L = 200$ mH and $C = 0.05\ \mu\text{F}$, determine the values of angular frequency ω for which the current will: -
- be in-phase with applied voltage (3 marks)
 - lead the applied voltage by 30° (3 marks)

QUESTION FOUR (20 MARKS)

- a) With the aid of diagrams, distinguish between the following types of transmission lines
- i. Co-axial line (2 marks)
 - ii. Open line wire (2 marks)
- b) A two-wire air-line has the following line parameters: $R = 0.404 \text{ (m}\Omega \text{ /m)}$, $L = 2.0 \text{ (}\mu\text{H/m)}$, $G = 0$, and $C = 5.56 \text{ (pF/m)}$. For operation at 5 kHz, determine
- i. The attenuation constant α , (4 marks)
 - ii. The phase constant β , (3 marks)
 - iii. The characteristic impedance Z_0 (3 marks)
- c) If the current in a series RC circuit is given by $i = 2 \cos (1000t + 10^\circ)$ amperes and the applied voltage is given by $e = 100 \cos (1000t + 55^\circ)$ volts, calculate the values of R and C. (6 marks)

QUESTION FIVE (20 MARKS)

- a) What is meant by the following: -
- i. Electrical filter circuits (2 marks)
 - ii. Cut-off frequency of a filter circuit (2 marks)
- b) A high-pass RC filter consists of a $100 \text{ k}\Omega$ resistor and a 50 pF capacitor. Calculate
- i. the cut-off frequency f_c of the filter (2 marks)
 - ii. the ratio of the peak output voltage and peak input voltage at frequency of $0.1 f_c$ (2 marks)
 - iii. At what frequency is the peak output voltage one half the peak input voltage? (3 marks)
- c) Two admittances, $Y_1 = (0.167 - j0.167) \text{ S/m}$, and $Y_2 = (0.1 + j0.05) \text{ S/m}$ are connected across a 100 V , 50 Hz single-phase supply. Determine: -
- i. The current in each branch and the total current. (4 marks)
 - ii. The power factor of the combination. (3 marks)
 - iii. Sketch a neat phasor diagram. (2 marks)