



MACHAKOS UNIVERSITY

University Examinations for 2023/2024 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

FOURTH YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)

EEE 403: ANALOGUE ELECTRONICS III

DATE:

TIME:

INSTRUCTIONS

Instructions: Attempt question ONE (Compulsory) and any other TWO questions.

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) State any THREE important features of instrumentation amplifier. (3 marks)
- b) Explain why op-amps are used most commonly as integrator and not as differentiator. (3 marks)
- c) With the aid of a suitable diagram explain how external offset compensation network for an inverting amplifier. (5 marks)
- d) Determine the output voltage of the following op-amp circuit shown in Figure Q1 (d).

 


Figure Q1 (d)

- e) Using suitable diagrams discuss a comparator used as a zero crossing detector. (7 marks)
- f) Prove that maximum collector efficiency of a Class B amplifier is 78.5%. (8 marks)

QUESTION TWO (20 MARKS)

- a) Briefly explain the necessity of differential amplifier stage in construction of operational amplifiers. (3 marks)
- b) Design and hence describe the working principle of first stage of an op-amp using bipolar junction transistors (BJT) and other relevant circuit components. (9 marks)
- c) Operational amplifier has differential gain of 80 dB and CMRR of 100 dB . If $V_1 = 2\mu\text{V}$ and $V_2 = 1.6\mu\text{V}$, then calculate output voltages for differential and common-mode input signal operations. (8 marks)

QUESTION THREE (20 MARKS)

- a) Explain the meaning of the term conversion efficiency as used in power amplifiers. (2 marks)
- b) Discuss crossover distortion in power amplifiers and how it is minimized. (6 marks)
- c) Draw the circuit diagram of a Class A amplifier and explain its operation briefly. (6 marks)
- d) A Class A power amplifier has zero signal collector current of 50 mA . If the collector supply voltage is 5 V , determine:
 - i. The maximum ac power output,
 - ii. Power rating of the transistor, and
 - iii. Maximum collector efficiency. (6 marks)

QUESTION FOUR (20 MARKS)

- a) Explain the following parameters of operational amplifier:
 - i. Slew rate
 - ii. CMRR (4 marks)
- b) Show that the closed loop gain of practical inverting amplifier (assume finite open loop gain of A_{OL}) is given by

$$A_{CL} = \frac{-R_2/R_1}{1 + \frac{1}{A_{OL}}(1 + \frac{R_2}{R_1})}$$

(6 marks)

- c) Determine the common-mode rejection ratio (CMRR) of the differential amplifier as shown in Figure Q4 (c).

 


Figure Q4 (c)

(10 marks)

QUESTION FIVE (20 MARKS)

- State THREE disadvantages of logarithmic amplifier. (3 marks)
- Prove that the operational amplifier circuit as shown in Figure Q5 (b) is an integrator. Assume the operational amplifier is an ideal one. (6 marks)

 


Figure Q5 (b)

- Draw circuit diagram of a current to voltage converter and hence explain its operation. Give also a brief account of practical applications. (6 marks)
- Explain the main problem with basic half-wave precision rectifier why it's rarely being used and hence illustrate how to remedy this problem. (5 marks)