



MACHAKOS UNIVERSITY

UNIVERSITY EXAMINATIONS 2021/2022

**THIRD YEAR SECOND SEMESTER EXAMINATIONS FOR THE DEGREE OF
BACHELOR OF SCIENCE IN MECHANICAL ENGINEERING**

EMM 300: ENGINEERING ELECTRONICS

DATE: December, 2021

TIME: 2 Hours

INSTRUCTIONS

Answer question **ONE** and **ANY OTHER TWO** questions

Question One [30 marks]

- (a) Use a K map to simplify

$$y = \overline{C}(\overline{A}\overline{B}\overline{D} + D) + A\overline{B}C + \overline{D}.$$

(7 marks)

- (b) Prove that the ripple factor of a half-wave rectifier is 1.21 and that of a full-wave rectifier is 0.482.

(6 marks)

- (c) A diode having internal resistance $20\ \Omega$ is used for half-wave rectification. If the applied voltage $V = 50 \sin \omega t$ and load resistance is 800Ω , find

- (i) $I_{\max}$, I_{dc} , I_{rms}
- (ii) ac power input and dc power input
- (iii) dc output voltage
- (iv) efficiency of rectification

(7 marks)

- (d) With the aid of a circuit diagram describe the operation of a Hartley oscillator.

(10 marks)

Question Two.

- (a) A full wave bridge rectifier is supplied from 230 V, 50 Hz and uses a transformer of turns ratio of 15: 1. It uses load resistance of $50\ \Omega$. Calculate load voltage and ripple voltage. Assume ideal diode and transformer. Assume standard value of ripple factor for full wave rectifier.

(10 marks)

- (b) A full wave rectifier circuit is fed from a transformer having a center-tapped secondary winding. The r.m.s. voltage from either end of secondary to center tap is 30 V. If the diode forward resistance is $2\ \Omega$ and that of the half secondary is $8\ \Omega$, for a load of $1\ \text{k}\Omega$, calculate,
- Power delivered to load,
 - % Regulation at full load,
 - Efficiency of rectification,
 - T.U.F. of secondary.

(10 marks)

Question Three.

- (a)
- The tuned collector oscillator circuit used in the local oscillator of a radio receiver makes use of an LC tuned circuit with $L_1 = 58.6\ \mu\text{H}$ and $C_1 = 300\ \text{pF}$. Calculate the frequency of oscillations;
 - Find the capacitance of the capacitor required to build an LC oscillator that uses an inductance of $L_1 = 1\ \text{mH}$ to produce a sine wave of frequency 1 GHz;
 - A Colpitt's oscillator has the following parameters: capacitance $C_1 = 0.001\ \mu\text{F}$, $C_2 = 0.01\ \mu\text{F}$ and inductor $L = 15\ \mu\text{H}$. Determine the operating frequency and the feedback fraction for the oscillator.

(8 marks)

- (b)
- A silicon transistor using the voltage divider bias method has the following parameters: $R_1 = 33\ \text{k}\Omega$, $R_2 = 15\ \text{k}\Omega$, $R_C = 1\ \text{k}\Omega$, $R_E = 680\ \Omega$ and $V_{CC} = 9\ \text{V}$. Determine the operating point of this transistor.
 - Given that the load resistor for the transistor in (b) i $R_L = 1\ \text{k}\Omega$ and that input and output coupling and emitter bypass capacitors are used draw the ac equivalent circuit.

(12 marks)

Question Four.

- (a) Add -118 and -32 firstly using eight-bit 2's complement arithmetic and then using 16-bit 2's complement arithmetic. Comment on the results.

(10 marks)

- (b) Consider the two circuits in Fig.Q4. The parameters of each transistor are $I_s = 5 \times 10^{-16} \text{ A}$ and $\beta = 90$. Determine V_{BB} in each circuit such that $V_{CE} = 1.10 \text{ V}$.

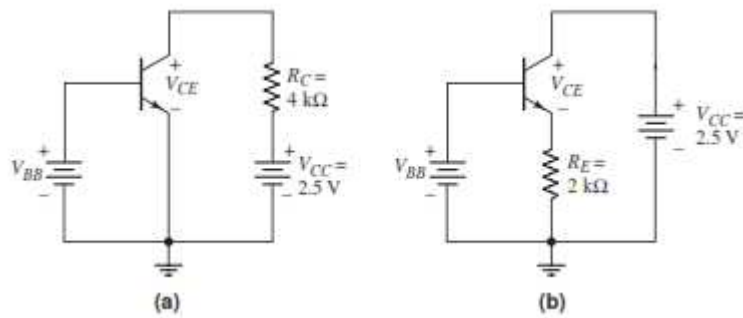


Fig.Q4

(10 marks)

Question Five.

- (a) (i) Define synchronous counters.
(ii) Design a **MODULO-5** synchronous counter using **JK** flip-flops.

[13 marks]

- (b) Explain how a shift register can be used as a ring counter giving the wave forms at the output of the flip-flops.

[7 marks]

END