



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

SECOND YEAR SPECIAL/SUPPLEMENTARY EXAMINATION FOR

BACHELOR OF SCIENCE (MECHANICAL ENGINEERING)

EMM 209: ELECTRICAL ENGINEERING 1

DATE: 29/8/2022

TIME: 2.00-4:00 PM

INSTRUCTIONS:

- (i) There are **Five** questions.
- (ii) Question No.1 is **Compulsory** and carries **30 Marks**.
- (iii) Select any **other Two** questions, each of which carries 20 Marks.
- (iv) Define all symbols used .
- (v) Marks will be awarded for procedure, methodologies used and not necessarily on the final answer.

1.
 - (a)
 - (i) Show that the energy stored in a capacitor C is $\frac{1}{2} C v^2$. (4 marks)
 - (ii) Fig Q1 (a) depicts a coil on a toroid iron core. Sketch the equivalent magnetic circuit and give the mean magnetic path length. (6 marks)
 - (b)
 - (i) Using relevant diagrams and examples, distinguish between mutual-inductance and self-inductance (5 marks)
 - (iii) Demonstrate thorough understanding of the term “*Reactive Power*”. (5 marks)
 - (c)
 - (i) Use Mesh-Current analysis techniques to solve for the current in each element of the circuit shown in Fig. Q 1(c). (7 marks)
 - (ii) State Ampere’s Law and write its formula. (3 marks)

2. (a) The *Network* in Fig. Q2. Has the switch closed at time $t = 0$. After the steady state is reached with the switch closed the switch is opened.
Obtain: -
- (i) An expression for the current in the circuit when the switch is closed. (4 marks)
 - (ii) An expression for the current after the switch is opened. (4 marks)
 - (iii) For both cases in (i) and (ii) above sketch the current waveforms. (2 marks)
- (b) For the circuit shown in Fig. Q2(b) determine: -
- i Apparent power. (3 marks)
 - ii Average power. (3 marks)
 - iii Power factor. (4 marks)
3. (a) For the network in Fig. Q3 (a) assume that R, L, C have magnitudes all equal to unity. If $V_R(t)$ has the wave form shown in Fig. Q3 (b) obtain the wave form for: -
- (i) $i(t)$ (2 marks)
 - (ii) $v_L(t)$ (4 marks)
 - (iii) $v_C(t)$ (4 marks)
- (b) (i) Demonstrate thorough understanding of what hysteresis is. (5 marks)
- (ii) Find the unknown impedance Z_1 in Fig. Q3 (c). (5 marks)
4. Consider the circuit shown in Fig. Q4. The switch is opened at time $t = 0$ after the circuit has reached in steady state.
- (a) Derive the expressions for the current $i(t)$ and the voltage $v(t)$. (4 marks)
 - (b) Give the time constant for the circuit after the switch opens. (4 marks)
 - (c) Determine the maximum magnitude of $v(t)$. (4 marks)
 - (d) Find the time at which $v(t)$ is one-half of its value immediately after the switch opens. (4 marks)
 - (e) Sketch the wave forms for $i(t)$ and $v(t)$. (4 marks)
5. (a) Consider the magnetic core with an air gap depicted in Fig. Q5. The core material has $\mu_r = 7000$. Taking $\mu_0 = 4\pi \times 10^{-7}$,
- (i) Sketch the magnetic circuit. (3 marks)
 - (ii) Determine the current required to establish a magnetic flux density of $B_{gap} = 0.25T$ in the air gap. (7 marks)
- (b) A balanced positive-sequence wye-connected 60-Hz 3 ϕ supply source has line-to-line voltages of 1,000 V. This source is in turn connected to a balanced wye-connected load. Each phase of the load consists of a 0.2 H inductance in series with a 100 Ω resistance. Assuming that V_R is zero, find: -
- (i) Line-to-neutral voltages. (3 marks)
 - (ii) Line currents. (3 marks)
 - (iv) The power delivered to the load. (4 marks)

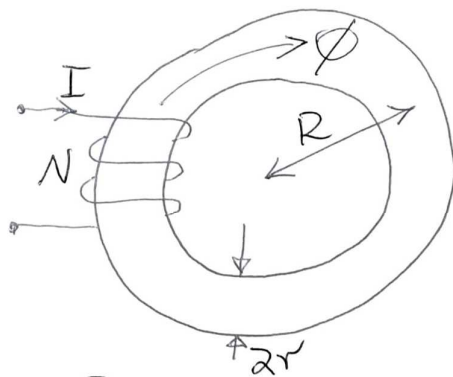


Fig Q1(a)

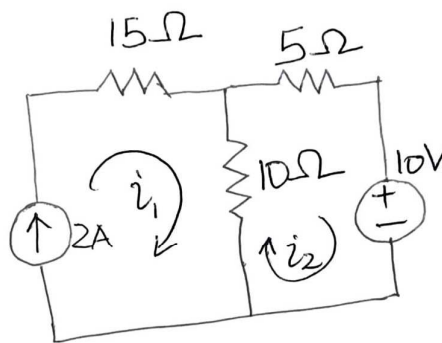


Fig Q1(c)

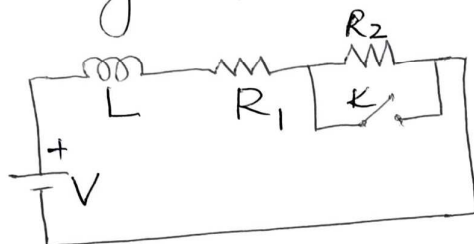


Fig Q2(a)

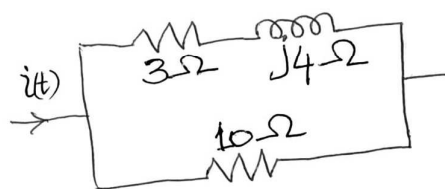


Fig Q2(b)

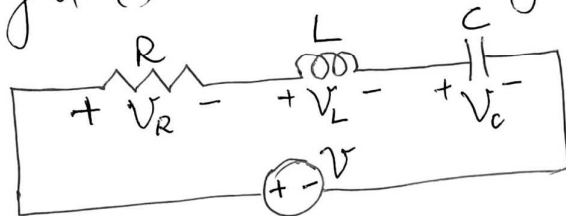


Fig Q3(a)

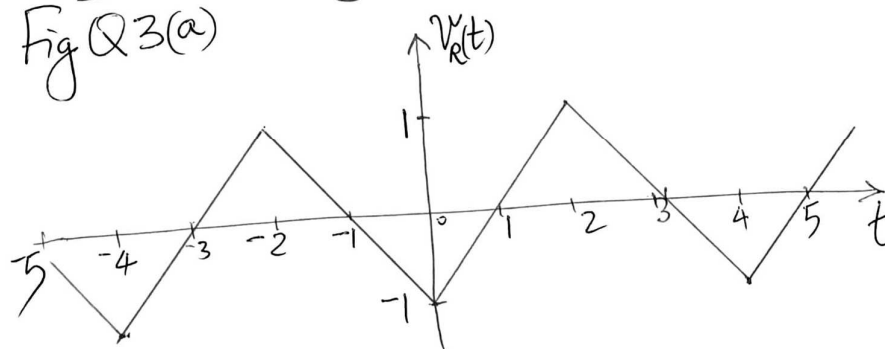


Fig Q3(b)

