



MACHAKOS UNIVERSITY

University Examinations 2017/2018

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION DIPLOMA IN ELECTRICAL
ENGINEERING

EED 211: ELECTRICAL ENGINEERING PRINCIPLES IV

DATE: 19/12/2017

TIME: 8.30-10.30 AM

INSTRUCTIONS

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS

SECTION A: COMPULSORY QUESTION.

1. (a) Define the following terms with regard to a d.c series L – R circuit;
 - (i) Rise time
 - (ii) Settling time (4 marks)
- (b) With the aid of a plotted graph and using differential equations, derive the expression of the resultant current in a d.c series L – R circuit suddenly connected to a supply voltage V after being switched on. (7 marks)
- (c) The winding of an electromagnet, with an inductance value of 3 H and a resistance of 15 Ω , is connected to a 120 V d.c supply. Calculate the following values;
 - (i) The induced emf after 0.1 sec
 - (ii) The time for the current to rise to 85% of its final value
 - (iii) The current after 0.3sec. (8 marks)

- (d) Explain with the aid of circuit and phasor diagrams the operation of a single – phase practical transformer on no – load. (8 marks)
- (e) State any three advantages of an Autotransformer. (3 marks)

SECTION B – ATTEMPT ANY TWO QUESTIONS

2.
 - (a) Define the term “ Time constant ” with regard to a d.c series L – R circuit. (2 marks)
 - (b) Explain with regard to a.c series L –R –C circuits the following terms
 - (i) Overdamped
 - (ii) Critically damped. (4 marks)
 - (c)
 - (i) Derive the emf equation of a single – phase ideal transformer. (5 marks)
 - (ii) Describe the Iron losses of a power transformer. (3 marks)
 - (d) A transformer has a primary winding of 800 turns and a secondary winding of 200 turns. When the load current on the secondary is 80 A at 0.8 power factor lagging, the primary current is 25 A at 0.707 power factor lagging. Determine with the aid of a phasor diagram;
 - (i) the no – load current and
 - (ii) the phase angle of the no – load current with respect to the voltage. (6 marks)
3.
 - (a) Define the following terms with regard to unbalanced 3 – phase system of vectors;
 - (i) A positive – sequence component
 - (ii) A negative – sequence component
 - (iii) Zero – sequence component. (6 marks)
 - (b) Describe with the aid of a connection diagram a method of measuring zero – sequence component of voltage in an unbalanced 3 – phase, 3 – wire system. (5 marks)
 - (c) With the aid of sketch diagrams for the respective vectors, calculate the
 - (i) Positive – phase sequence
 - (ii) Negative – phase sequence and
 - (iii) Zero – phase sequence components of the following set of three unbalanced voltage vectors;

$$V_A = 8.66 + j5 \quad ; \quad V_B = 15 - j25.98 \quad ; \quad V_C = -12.29 + j8.60. \quad (9 \text{ marks})$$

4. (a) With regard to zero – sequence components of currents and voltage describe the following 3 – phase circuit connections;
- Four – wire Star connection.
 - Three – wire delta connection. (6 marks)
- (b) A 50Hz sinusoidal voltage of maximum value of 400 V is applied to a series circuit of resistance $10 \, \Omega$ and inductance 0.1 H. assuming that voltage is zero at the instant of application, determine;
- The expression for the value of the current at any instant after the voltage is applied ,
 - The value of the current 0.02 sec after switching on. (8 marks)
- (c) In the no – load test of a single – phase transformer the following test data were obtained;
- Primary voltage : 220 V ; Secondary voltage : 110 V
 Primary current : 0.5 A ; Power input : 30 W
 Resistance of Primary winding : $0.6 \, \Omega$.
- Calculate the following ;
- The turns ratio
 - The magnetizing component of the no – load current
 - The working component of the no – load current
 - The Iron loss (6 marks)
5. (a) (i) State four conditions for satisfactory parallel operation of two single – phase transformers. (4 marks)
- (ii) Explain with a diagram the principle of a current transformer. (5 marks)
- (b) Derive the expression for the capacitor discharging current in a d.c series C – R circuit. (5 marks)
- (c) A 40 V d.c supply is connected across a coil of inductance 25 mH and resistance $5 \, \Omega$. Calculate the following ;
- the value of current after 10 mSec
 - The p.d across the resistor after 5 mSec
 - The value of the voltage across the inductance after 2 mSec.
 - The time when the current reaches 3 A. (6 marks)