



MACHAKOS UNIVERSITY

University Examinations 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD SEMESTER EXAMINATION FOR BACHELOR OF SCIENCE IN
ELECTRICAL AND ELECTRONICS ENGINEERING

SUPPLEMENTARY EXAMINATION

EEE204: CIRCUIT THEORY II

DATE:

TIME:

INSTRUCTIONS:

This paper consists of FIVE questions. Answer Question ONE and any other TWO questions

QUESTION ONE (COMPULSORY-30 marks)

a)(i) State **three** reasons why three phase systems are preferred over single phase systems for transmission of power

(ii) Explain the following as applied to three phase systems

- I. Balanced load
- II. Phase sequence

(5 marks)

(b)(i) Explain the **need for** unity power factor in industrial loads

(ii) State **two approaches** of improving power factor in the industrial loads

(6 marks)

(c) (i) Two sources of emf $200\sin\omega t$ and $200\sin\omega t + \pi/2$ are in series.

- I. Express the resultant vector in vector notation with reference to $200\sin\omega t$
- II. Determine the rms current and power supplied to $(8+j6)\Omega$ impedance

(ii) For the circuit in **Figure 1**, determine the

- I. Real power

- II. Reactive power
- III. Apparent power

(13 marks)

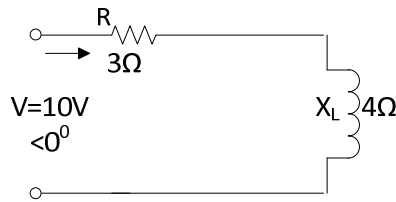


Figure 1

(c) Explain the **dot rule** in coupled circuits

(2 marks)

(d) Distinguish between the **transient** and **steady state** condition of a circuit. Explain why it's important to have knowledge of the two states for a given circuit.

(4 marks)

QUESTION TWO (20 Marks)

(a) For the schematic diagram of the system in Figure 2,

(i) Determine the

- I. total number of watts
- II. total number of volt-ampere reactive
- III. total number of volt-amperes
- IV. power factor, PF

(ii) Draw the power triangle

(iii) Find the current in phasor form

(10 marks)

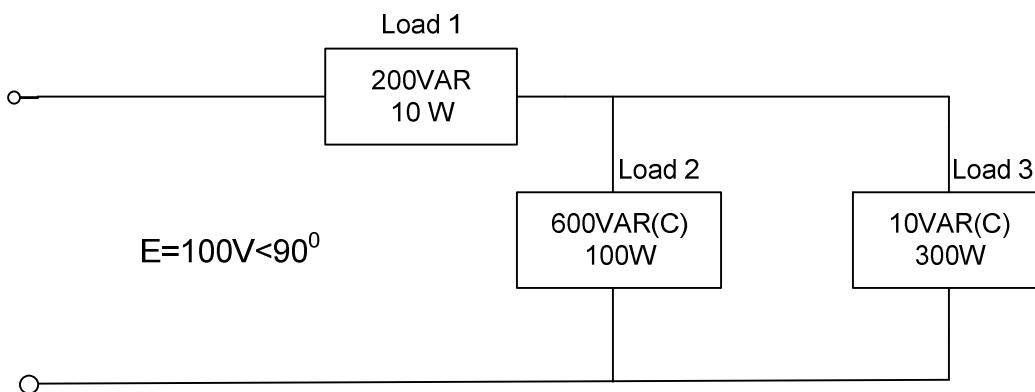


Figure 2

(b) Calculate the phasor currents I_1 and I_2 in the circuit of Figure 1

(10 marks)

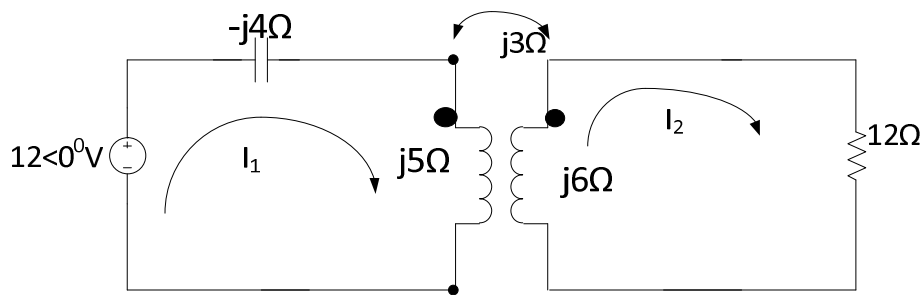


Figure 3

QUESTION THREE (20 MARKS)

- (a) When connected to a 120-V(rms), 60 Hz power line, a load absorbs 4kW at lagging power factor of 0.8. Determine the value of capacitance necessary to raise the power factor to 0.95. (8 marks)
- (b) For a line voltage $V_L = 208\text{ V}$ and wattmeter reading of a balanced system are found to be $P_1 = -560\text{ W}$ and $P_2 = 800\text{ W}$, determine the :
- Total average power
 - Total reactive power
 - Power factor
 - Phase impedance

(12 marks)

QUESTION FOUR (20 MARKS)

- (a) A 400 V 3 phase 50 Hz system supplies the following three loads: 200 h.p (1 h.p=735.5 W), induction motor operating at 0.9 efficiency and 0.8 lagging power factor, a 50 kW resistance heating load and a special load of 40kW at 0.707 p.f lagging. Determine the:
- Total active power
 - Total reactive power
 - Total voltamperes
 - Line current
 - Overall power factor

- (b) Find the resonance frequency of the circuit in Figure 7

(10 marks)

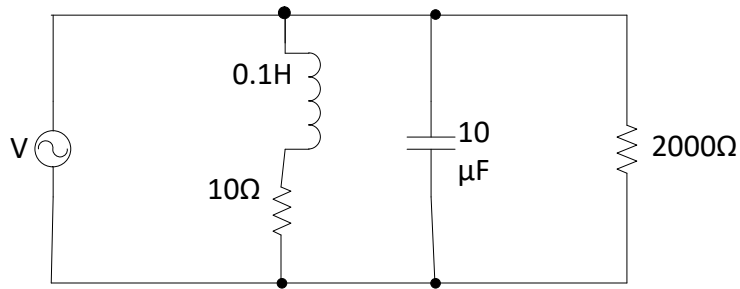


Figure 4

QUESTION FIVE (20 MARKS)

- a) A series resonant circuit has the parameters $R = 2\Omega$, $X_L = 10\Omega$, $X_C = 10\Omega$ and source voltage $E = 10V \angle 0^\circ$. At resonance, determine the :
- Circuit current I , voltage across the resistor, inductor and capacitance V_R , V_L , and V_C respectively;
 - Quality factor at resonance, Q_s ;
 - Bandwidth if the resonance frequency is 5000Hz;
 - Power dissipated in the circuit at half power frequencies.

(10 marks)

- (b) A 3-phase balanced star connected load has impedance $20 + j30 \Omega$ in each phase. It is fed by a 400V 3 phase supply. Determine the:

- Line current
- Power factor
- active power,
- reactive power
- apparent power

(10 marks)