



# MACHAKOS UNIVERSITY

University Examinations 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR BACHELOR OF SCIENCE IN  
ELECTRICAL AND ELECTRONICS ENGINEERING

SUPPLEMENTARY EXAMINATION

EEE 404: POWER SYSTEMS II

DATE: 28/8/2017

TIME: 8.30 - 10.30 AM

---

## INSTRUCTIONS

This paper consists of **Five** questions. Answer question **One** and any other **TWO**

### QUESTION ONE (COMPULSORY) (30 MARKS)

- (a) A 3-phase 20 MVA, 10 kV alternator has internal reactance of 5% and negligible resistance. Find the external reactance per phase to be connected in series with the alternator so that steady current on short circuit does not exceed 8 times the full load current. (8 marks)
- (b) Estimate the distance over which a load of 15000 kW at a p.f of 0.8 lagging can be delivered by a 3-phase transmission line having conductors each of resistance  $1\Omega$  per kilometer. The voltage at the receiving end is to be 132 kV and the loss in the transmission is to be 5% (8 marks)

- (c) A three phase 50 Hz 66 kV overhead line conductor are placed in a horizontal plane as shown in Figure 2. The conductor diameter is 1.25 cm. If the line length is 100 km, calculate
- Capacitance per phase
  - Charging current per phase (8 marks)
- Assume complete transposition
- (d) Explain with the aid of a diagram the following terms as applied to a three phase system.
- Positive sequence component
  - Negative sequence component
  - Zero sequence component (6 marks)

## QUESTION TWO (20 MARKS)

- (a) Starting from the Ampere law, show that the total flux linkages round a conductor of radius  $r$  carrying current  $I$  is given by:

$$\frac{\mu_0 I}{2\pi} \left[ \frac{1}{4} + \int_r^{\infty} \frac{dx}{x} \right] \text{ weber turn / m length}$$

(14 marks)

- (b) Show that the Inductance of a Single phase two wire line with conductor radius of  $r$  metres separated by distance  $d$  is given by:

$$\frac{\mu_0}{\pi} \left[ \frac{1}{4} + \ln \frac{d}{r} \right] \text{ H/m}$$

(8 marks)

- (c) Three conductors, each of diameter 1.24cm, of a 3-phase line are arranged at the corners of a triangle of sides 2m, 2.5m and 4.5m. Calculate the inductance per km of the line when the conductors are regularly transposed. (4 marks)

### QUESTION THREE (20 MARKS)

- (a) Draw the equivalent circuit of a single phase short transmission line explaining all the parameters shown. (4 marks)
- (b) Draw the phasor diagram of the line for lagging power factor (4 marks)
- (c) A single phase overhead transmission line delivers 1100 kW at 33kV at 0.8 pf lagging. The total resistance and inductive reactance of the line are  $10\Omega$  and  $15\Omega$  respectively. Determine:
- i. Sending end voltage (6 marks)
  - ii. Sending end power factor (3 marks)
  - iii. Transmission efficiency. (3 marks)

### QUESTION FOUR (20 MARKS)

- (a) Explain using diagrams, two methods of locating the reactors for control of short circuit current to ensure that minimum voltage drop and power loss during normal operation. (8 marks)
- (b) A 3-phase transmission line operating at 10 kV and having a resistance of  $1\Omega$  and reactance of  $4\Omega$  is connected to the generating station bus-bars through 5MVA step-up transformer having a reactance of 5%. The bus- bars are supplied by a 10 MVA alternator having 10% reactance. Calculate the short-circuit kVA fed to symmetrical fault between phases if it occurs
- i. At the load end of the transmission line (9 marks)
  - ii. At the high voltage terminals of the transformer (3 marks)

### QUESTION FIVE (20 MARKS)

The two generators shown in Figure 1 are identical, each rated 13.8kV and 50MVA with a sub-transient reactance of  $X_d'' = 15\%$ . The two generators are tied to a common bus which is connected to a transmission line with a delta-grounded wye transformer rated at 150MVA, 13.8kV/115kV and an impedance of 9.7%. The transmission line is 30 miles long and has an impedance of  $5.43 + j22.5\Omega$ . At the end of the transmission line is a grounded wye-grounded wye transformer, rated 225MVA, 115kV/230kV with an impedance

of 7.4% that connects the line to a 230kV bus. The remaining power system connected to the 230kV bus is not shown. Each generator has a zero-sequence reactance of 5% and is grounded through a

reactance of  $2\Omega$ . The transmission line has a zero-sequence impedance of  $12.9 + j75.9\Omega$ . The grounded wye-grounded wye transformer has a zero-sequence reactance of 4.8%. Use voltage bases of 13.8kV, 115kV, and 230kV for the corresponding parts of the system, and use a power base of 100MVA for the whole system.

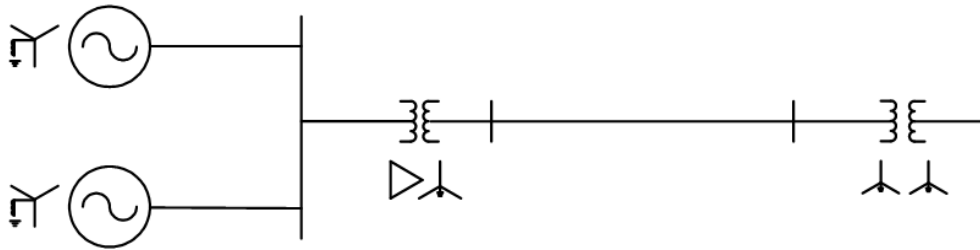


Figure 1

- (a) From the above information, draw the impedance diagram with impedances shown in their per-unit values (8 marks)
- (b) Draw the positive, negative and zero-sequence impedance networks for the power system with impedances shown in their per-unit values. (11 marks)

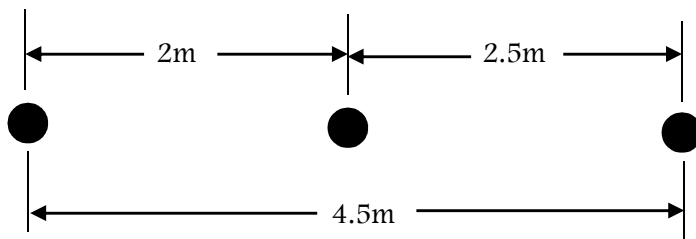


Figure 2