



# MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

THIRD YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS

ENGINEERING)

EEE 308: ANALOGUE ELECTRONICS I

DATE: 16/3/2021

TIME: 2:00 – 4:00 PM

## INSTRUCTIONS:

Answer question **ONE** and **ANY OTHER TWO** questions

## QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Consider the two circuits in Fig.Q1. The parameters of each transistor are  $I_s = 5 \times 10^{-16}$  A and  $\beta = 90$ . Determine  $V_{BB}$  in each circuit such that  $V_{CE} = 1.10$  V.

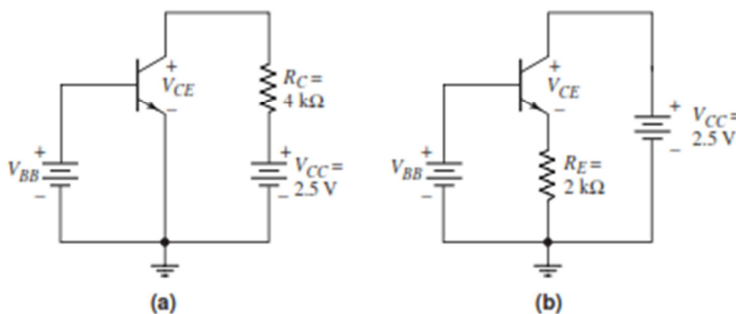


Fig.Q1

(10 marks)

- b) Derive the relationship between base current amplification factor  $\beta$  and emitter current amplification factor  $\alpha$ . (6 marks)

- c) In the circuit shown in Fig.Q2, the values of measured parameters are shown. Determine  $\beta$ ,  $\alpha$ , and the other labeled currents and voltages. Sketch the dc load line and plot the Q-point.

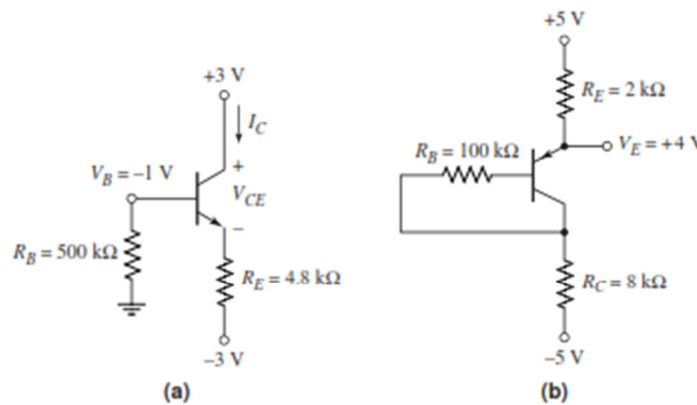


Fig.Q2

- d) Explain the following terms with respect to FETs.

(9 marks)

- Shorted-gate drain current ( $I_{DSS}$ );
- Pinch off voltage ( $V_P$ );
- Gate-source cut off voltage [ $V_{GS(off)}$ ].

(5 marks)

## QUESTION TWO (20 MARKS)

- a) A diode operating at  $300^\circ\text{K}$  at a forward voltage of  $0.4\text{ V}$  carries a current of  $10\text{ mA}$ . When voltage is changed to  $0.42\text{ V}$ , the current becomes twice. Calculate the value of reverse saturation current and  $\eta$  for the diode. (8 marks)
- b) The parameters of the zener diode for the voltage regulator of the circuit of Fig. Q2 (c) are  $V_Z = 4.7\text{ V}$  at test current  $I_{ZT} = 53\text{ mA}$ ,  $R_Z = 8\ \Omega$ , and  $R_{ZK} = 500\ \Omega$  at  $I_{ZK} = 1\text{ mA}$ . The supply voltage  $v_S = V_S = 12 \pm 2\text{ V}$ , and  $R_S = 220\ \Omega$ .
- Find the nominal value of the output voltage  $v_O$  under no-load condition  $R_L = \infty$ ;
  - Find the maximum and minimum value of the output voltage for a load resistance  $R_L = 470\ \Omega$ ;
  - Find the nominal value of the output voltage  $v_O$  for a load resistance  $R_L = 100\ \Omega$ ;
  - Find the minimum value of  $R_L$  for which the zener diode operates in the breakdown region.

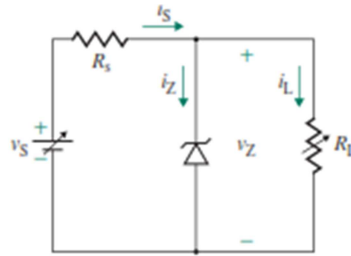


Fig.Q2 (c)

(12 marks)

### QUESTION THREE (20 MARKS)

- a) A full wave bridge rectifier is supplied from 230 V, 50 Hz and uses a transformer of turns ratio of 15: 1. It uses load resistance of 50  $\Omega$ . Calculate load voltage and ripple voltage. Assume ideal diode and transformer. Assume standard value of ripple factor for full wave rectifier. (10 marks)
- b) A full wave rectifier circuit is fed from a transformer having a center-tapped secondary winding. The r.m.s. voltage from either end of secondary to center tap is 30 V. If the diode forward resistance is 2  $\Omega$  and that of the half secondary is 8  $\Omega$ , for a load of 1 k $\Omega$ , calculate,
- Power delivered to load,
  - % Regulation at full load,
  - Efficiency of rectification,
  - T.U.F. of secondary.
- (10 marks)

### QUESTION FOUR (20 MARKS)

- a) A PNP transistor is used in self-biasing arrangement the circuit components are  $V_{cc} = 4.5$  V;  $R_2 = 2.7$  K $\Omega$ ;  $R_E = 0.27$  K $\Omega$  ;  $R_1 = 27$  K $\Omega$  of  $\beta = 44$ . Find
- Stability factor.
  - Quiescent point
  - Recalculate these values if the base – spreading resistance of 690  $\Omega$  is taken in account.
- (10 marks)
- b) Derive the expression for the stability factor for the potential divider method of biasing. (10 marks)

### QUESTION FIVE (20 MARKS)

- a) In a self-bias n-channel JFET, the operating point is to be set at  $I_D = 1.5 \text{ mA}$  and  $V_{DS} = 10 \text{ V}$ . The JFET parameters are  $I_{DSS} = 5 \text{ mA}$  and  $V_{GS(off)} = -2 \text{ V}$ . Find the values of  $R_S$  and  $R_D$  given that  $V_{DD} = 20 \text{ V}$ . (6 marks)
- b) With the aid of a diagram, describe the operation of n-channel JFET. (10 marks)
- c) In an n-channel JFET biased by potential divider method, it is desired to set the operating point at  $I_D = 2.5 \text{ mA}$  and  $V_{DS} = 8 \text{ V}$ . If  $V_{DD} = 30 \text{ V}$ ,  $R_1 = 1 \text{ M}\Omega$  and  $R_2 = 500 \text{ k}\Omega$ , find the value of  $R_S$ . The parameters of JFET are  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -5 \text{ V}$ . (4 marks)