



MACHAKOS UNIVERSITY COLLEGE

**(A Constituent College of Kenyatta University)
University Examinations for 2015/2016 Academic Year**

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**FIRST SEMESTER EXAMINATION FOR DIPLOMA IN TELECOMMUNICATION
ENGINEERING**

EED 205: DIGITAL ELECTRONICS 1

DATE: 5/8/2016

TIME: 8:30 – 10:30 AM

INSTRUCTIONS

- 1. You should have an examination booklet for this examination**
- 2. Question ONE is compulsory**
- 3. Answer ANY other TWO questions.**
- 4. Maximum marks for each part of a question are as shown.**

QUESTION ONE COMPULSORY (30 Marks)

1. a) (i) Explain why binary numbering system is widely used in digital systems.
(4 marks)
- (ii) With the aid of a full adder truth table prove that $S = A \text{ EXCLUSIVE-OR } B \text{ EXCLUSIVE-OR } C_{in}$ and $C_o = C_{in}(A \text{ EXCLUSIVE-OR } B) \text{ OR } AB$.
(6 marks)
- b) (i) Convert the following numbers as instructed:
- 67_8 to binary;
 - $9C8_{16}$ to decimal.
- (ii) Perform the following operations:
- Add BCD numbers 12 and 14;
 - Convert gray code 111101 to binary.
- (10 marks)
- c) A chemical processing plant uses four sensors A, B, C, and D to control the conveyor belt at the packing bay. The conveyor belt will move when any of the following conditions are met.
- (i) ALL sensors are low;
 - (ii) ONLY one sensor output is high;
 - (iii) Sensor A and D are low; B C are high;
 - (iv) Sensor A and D are high; B C are low.
- Draw a truth table to represent these conditions;
 - Deduce a Boolean expression from the truth table and reduce it using a K – map;
 - Implement this control circuit using logic gates.
- (10 marks)
2. a) (i) Express the following decimal number into 8421 BCD;
 $(6347)_{10}$
(2 marks)

(ii) Using the 8421 BCD arithmetic, perform the following operation of decimal numbers $243 + 317$ (4 marks)

(iii) Express the following XS – 3 number in decimal;

1011011010010 (2 marks)

(iv) Perform the following conversions;

- 1011101011 binary to gray code
 - 011001111000 BCD to XS – 3
- (2 marks)

b) (i) With the aid of symbols, name the **seven** logic gates used in digital systems. (7 marks)

(ii) Table 1 shows the classification of logic families:

Table 1

Category	Number of equivalent basic logic gates on a single chip
1	12 – 99
2	100 – 999
3	10,000 and above

Name the corresponding category of the logic families. (3 marks)

3. a) For the logic circuit in figure 1, prepare a truth table and hence obtain the output expression at Y. (10 marks)

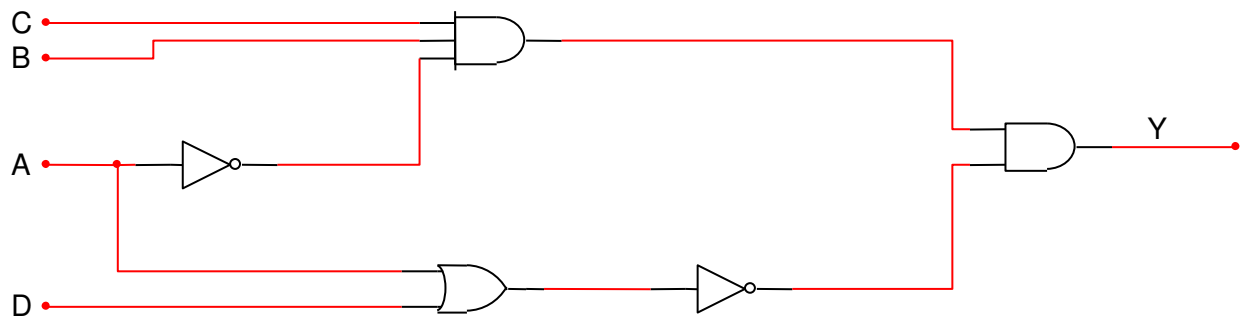


Figure 1

b) Differentiate between even and odd parity as used in error detection codes.

(4 marks)

c) Simplify using K map the following Boolean expression;

$$f(A,B,C,D) = \sum(0,1,2,3,4,5,6,7,8,9,12,13) \quad (6 \text{ marks})$$

4. a) Design a binary to gray code decoder. (10 marks)

b) A digital system is to be designed with three switches ABC to control the operation of a motor. The motor can run when;

- Switches A and B are ON
- Switches A and C are ON
- ALL switches are ON

Draw a simplified logic circuit diagram to facilitate this operation. (10 marks)

5. a) With the aid of a truth table, verify that $M.(D + F) = M.D + M.F$ (4 marks)

b) Design a full adder logic circuit using a 8-to-1 multiplexer. (6 marks)

c) Use Quine MC Clusky method to minimize the function given by;

$$F(A, B, C, D) = \sum(0,5,6,9,10,13,14,15,7) \quad (10 \text{ marks})$$