



# MACHAKOS UNIVERSITY

University Examinations 2017/2018

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

SECOND YEAR FIRST SEMESTER EXAMINATION DIPLOMA IN ELECTRICAL  
ENGINEERING

EED 216: POWER ELECTRONICS

DATE: 13/12/2017

TIME: 8.30-10.30 AM

---

## INSTRUCTIONS

1. Question 1 is compulsory  
Do any other TWO Questions
2. Neat work required

## QUESTION ONE (30 MARKS)

- (a) Define the following Electronic Components
- (i) Power Diode
  - (ii) Photo Diode
  - (iii) Light Emitting Diode (LED)
  - (iv) Varactor Diode
  - (v) Pin Diode (10 marks)
- (b) In any THREE of the diodes in Q1(a) explain their respective operations (9 marks)
- (c) Optic fibre cable Technology is the most advanced system all over world today.  
Describe its operations (11 marks)

### **QUESTION TWO (20 MARKS)**

- (a) Differentiate between Silicon controlled rectifiers (SCRs) and power diodes (4 marks)
- (b) With an aid of characteristics curves, explain the operation of an SCR (10 marks)
- (c) Define the following
  - i. Modulation
  - ii. Demodulation in communication electronics (6 marks)

### **QUESTION THREE (20 MARKS)**

- (a) Explain briefly an operational Amplifier ( OPAMP)
- (b) Show how an OPAMP is connected in an electronic circuit (10 marks)
- (c) Describe a cyclo converter in A.C Circuit (10 marks)

### **QUESTION FOUR (20 MARKS)**

- (a) Briefly explain the following circuits
  - (i) Analogue circuits
  - (ii) Digital circuits (8 marks)
- (b) Analyze how a signal is processed in a Digital/Analogue and vice –versa (10 marks)
- (c) State any TWO applications of analogue to digital converters ( A/D) (2 marks)

### **QUESTION FIVE (20 MARKS)**

- (a) Filters are divided into two types. Name them (4 marks)
- (b) Explain any two other types of filters applied in the electrical Engineering Industry (9 marks)
- (c) State any FOUR advantages of using optic fibres in communication Engineering (7 marks)