



MACHAKOS UNIVERSITY

University Examinations 2018/2019

SCHOOL OF PURE AND APPLIED SCIENCES

DEPARTMENT OF PHYSICAL SCIENCES

THIRD YEAR SECOND SEMESTER SUPPLEMENTARY EXAMINATION FOR
BACHELOR OF EDUCATION (SCIENCE)

SPH 340: SEMICONDUCTOR PHYSICS AND DEVICES

DATE: 25/7/2019

TIME: 8:30 – 10:30 AM

IMPORTANT CONSTANTS

Charge on an electron, $e = 1.6 \times 10^{-19} \text{ C}$

Boltzmann's constant, $k_B = 8.62 \times 10^{-5} \text{ eV/K}$

INSTRUCTIONS TO CANDIDATES

- I. Answer **QUESTION ONE** and **ANY OTHER TWO** questions in this paper.
- II. Cheating will lead to automatic disqualification.

QUESTION ONE

- a) Distinguish between the following materials using energy band diagrams clearly showing the forbidden gap
 - (i) A semiconductor (3 marks)
 - (ii) A metal (3 marks)
 - (iii) An insulator (3 marks)
- b) State the values of forbidden energy gap for silicon *Si* and germanium *Ge* at a room temperature of 27°C . (2 marks)
- c) Explain the operation of a Field Effect Transistor. (4 marks)
- d) State two advantages of a FET over a BJT. (2 marks)
- e) For the JFET circuit of Figure 1, $I_{DSS} = 9 \text{ mA}$ and $V_P = -3 \text{ V}$. Find the value of R_L for setting the value of V_{DS} at 7 V . Given: $V_{GS} = -2 \text{ V}$, $I_G = 0$ (3 marks)

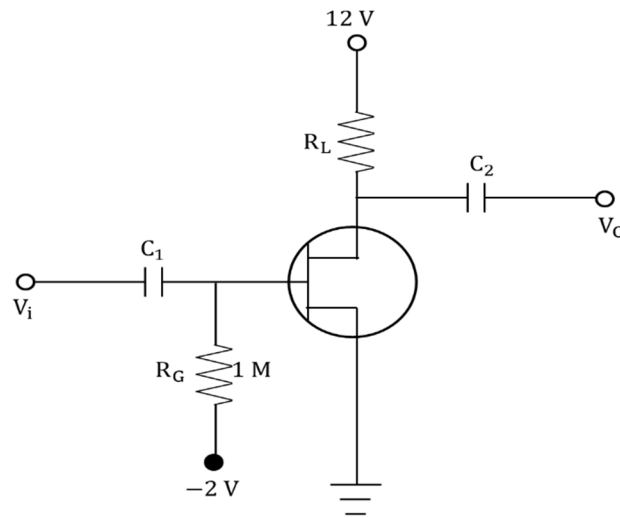


Figure 1

- f) The resistivity of an intrinsic silicon semiconductor at 27°C is $2.3 \times 10^5 \Omega\text{-cm}$. Calculate the intrinsic concentration of silicon at 127°C . (5 marks)
 Given: $\mu_n = 0.14 \text{ m}^2/\text{V.s}$ (At 27°C)
 $\mu_p = 0.05 \text{ m}^2/\text{V.s}$ (At 27°C)
 $E_{G0} = 1.21 \text{ eV}$
- g) Design a fixed biased circuit using a silicon transistor having β value of 100. V_{CC} is 10 V and dc bias conditions are to be $V_{CE} = 5 \text{ V}$ and $I_C = 5 \text{ mA}$. Label your circuit with all correct values. (5 marks)

QUESTION TWO

- a) Draw and explain the V-I characteristic of a PN junction. (4 marks)
- b) Describe using energy bands how a PN junction behaves under forward bias and reverse bias conditions. (4 marks)
- c) The following measurements were made in a certain transistor, $I_C = 5.202 \text{ mA}$, $I_B = 50 \text{ mA}$, $I_{CBO} = 2 \text{ mA}$. Determine,
 (i) α , β and I_E (6 marks)
 (ii) New value of the required to make $I_C = 10 \text{ mA}$. (3 marks)
- d) What is Fermi-Dirac probability function? State its significance. (3 marks)

QUESTION THREE

- a) With the help of energy band theory, define the following terms
- (i) Conduction band (2 marks)
 - (ii) Valence band (2 marks)
 - (iii) Forbidden energy gap (2 marks)
- h) Explain the mechanism of conduction in an intrinsic semiconductor, by free electrons and holes. (3 marks)

- i) A bar of intrinsic silicon semiconductor has a cross-sectional area of $2.5 \times 10^{-4} \text{ m}^2$. The electron density is $1.5 \times 10^{16} / \text{m}^3$. Current through the bar is 1.2 mA when 9 V is applied across it, how long is the bar?
Given that $\mu_n = 0.14 \text{ m}^2/\text{V.s}$ and $\mu_p = 0.05 \text{ m}^2/\text{V.s}$. (5 marks)
- j) Calculate the Q - point values (I_C and V_{CE}) for the circuit in Figure 2 hence show the point on the DC load line. (6 marks)

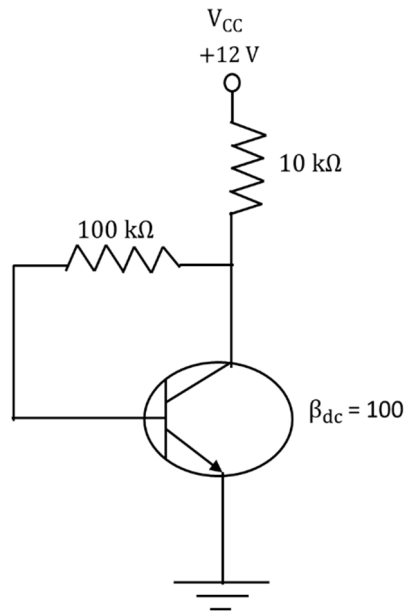


Figure 2

QUESTION FOUR

- a) What do you understand by the following terms as used in semiconductor devices,
- (i) Recombination (2 marks)
 - (ii) Load line (3 marks)
 - (iii) Quiescent point (3 marks)
- b) Explain the formation of the following semiconductors and explain how conduction takes place in each.
- (i) An N-type semiconductor. (3 marks)
 - (ii) A P-type semiconductor. (3 marks)
- c) Find the DC and AC load lines for common emitter circuit shown in Figure 3, assuming $V_{BE} = 0.7 \text{ V}$. (6 marks)

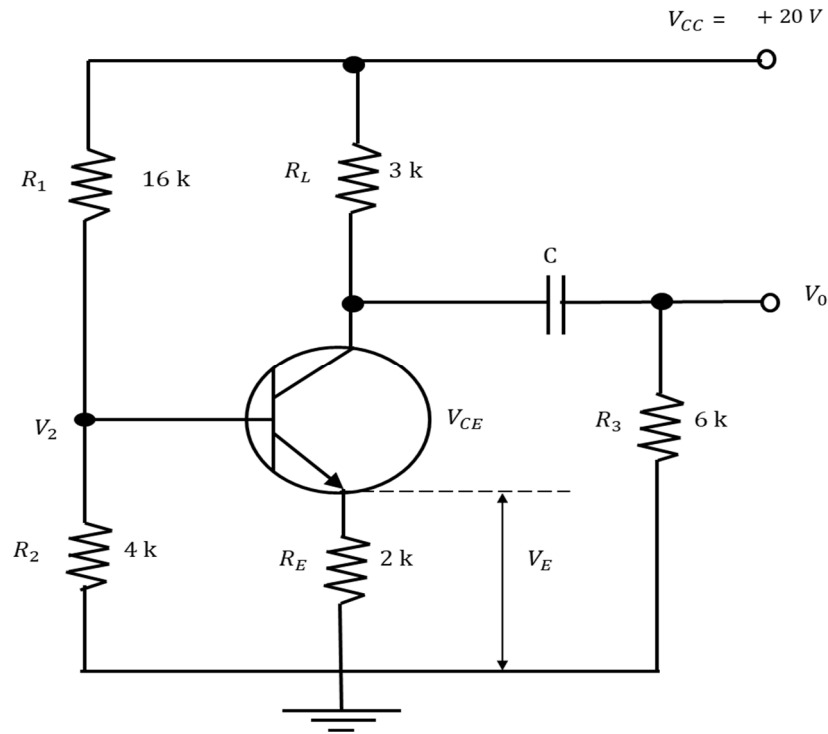


Figure 3

QUESTION FIVE

- (a) Explain with aid of diagrams the meaning of the following terms
 - ii. *Pinch off voltage* (3 marks)
 - iii. *Cut off voltage* (3 marks)
- (b) Describe with the aid of a diagram how a combination of an LED and a photodiode can be used as *raindrop sensor* for automobile windscreen. (6 marks)
- (c) The collector current of a transistor is found to be 9.9 mA for an emitter current of 10 mA in the common base mode. Calculate the transistor parameters and the base current. (4 marks)
- (d) The pinch off voltage of a depletion layer type MOSFET is -4 V and the drain current at zero gate voltage is 10mA . Find the mutual conductance when the gate voltage is +6V. (4 marks)