



MACHAKOS UNIVERSITY

University Examinations for 2019/2020 Academic Year

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (MECHANICAL ENGINEERING)

EMM 214: ELECTRICAL ENGINEERING II

DATE: 15/12/2020

TIME: 8:30 – 10:30 AM

INSTRUCTIONS

Answer Question One and Any Other Two Questions

QUESTION ONE (30 MARKS) (COMPULSORY)

- a) Give two types of DC machines and draw their equivalent circuit. (2 marks)
- b) A four-pole dc machine has an armature of radius 12.5cm and an effective length of 25cm. The poles cover 75% of the armature periphery. The armature winding consists of 33 coils each having seven turns. The coils are accommodated in 33 slots. The average flux density under each pole is 0.75T: If the armature is lap wound,
- i. Determine the value of K_a . (2 marks)
 - ii. Determine the induced armature voltage when the armature rotates at 1000 rpm. (3 marks)
 - iii. Determine the current in the coil and the electromagnetic torque developed when the armature current is 400A. (3 marks)
 - iv. Determine the power developed by the armature. (3 marks)
- c) Explain the functions of the following parts of a DC machine. (5 marks)
- i. The commutator,
 - ii. The brushes,
 - iii. The electric circuit of the motor,
 - iv. The magnetic circuit,
 - v. Why is the rotor/stator laminated?

- d) A single-phase transformer with a ratio of 6600/600V has a load impedance of $(4+j3)$ Ohms connected across the terminals LV side. Calculate the kW delivered to the load neglecting the losses. (4 marks)
- e) A six-pole lap connected generator has a useful flux/pole of 0.045Wb. If the no load voltage at 400rpm is 300V, find the conductors on the armature periphery. (4 marks)
- f) With aid of a diagram, show the power flows and losses in an induction motor from the three phase power supply to the shaft power. (4 marks)

QUESTION TWO (20MARKS)

- a) Tests are performed on a 1 ϕ , 10kVA, 2200/220V; 60Hz transformer and the following data in table 2a were obtained.

Table 2a

	Open-Circuit Test (HV side open)	Short-Circuit Test (LV side shorted)
Voltmeter	220V	150V
Ammeter	2.5A	4.55A
Wattmeter	100W	215W

- Derive the parameters for the approximate equivalent circuits referred to the low-voltage side and high-voltage side. (12 marks)
 - Express the excitation current as a percentage of the rated current. (2 marks)
 - Determine the power factor for the no load and short-circuit test. (2 marks)
- b) An ideal transformer has 1000 turns on its primary and 500 turns its secondary. The driving voltage on the primary side is 100V and the load resistance is 5Ω . Calculate V_2 , I_1 and I_2 . (4 marks)

QUESTION THREE (20MARKS)

- a) Give four different types of transformers. (2 marks)
- b) With the aid of a diagram, show how transformers are connected in parallel. (2 marks)
- c) Three 1 ϕ , 50kVA, 2300/230V, 60Hz transformers are connected to form a 3 ϕ , 4000/230 V transformer bank. The equivalent impedance of each transformer referred to low voltage is $0.012 + j0.016 \Omega$. The 3 ϕ transformer supplies a 3 ϕ , 120kVA, 230V, 0.85 PF (lag) load.
- Draw a schematic diagram showing the transformer connection (2 marks)
 - Determine the transformer winding currents (2 marks)
 - Determine the primary voltage (line-line) required. (3 marks)

- iv. Determine the voltage regulation. (2 marks)
- d) A 10kW, 100V, 1000 rpm dc machine has $R_a = 0.1 \Omega$ and is connected to a 100V dc supply.
- Determine the starting current if no starting resistance is used in the armature circuit. (2 marks)
 - Determine the value of the starting resistance if the starting current is limited to twice the rated current. (2 marks)
 - This dc machine is to be run as a motor, using a starter box. Determine the values of resistances required in the starter box such that the armature current I_a is constrained within 100 to 200% of its rated value (i.e., 1 to 2 pu) during start-up. (3 marks)

QUESTION FOUR (20MARKS)

- a) A 4500/16000V, 1500kVA, 50Hz transformer has the following parameters:
 $R_1 = 0.03\Omega$; $R_2 = 0.44\Omega$, $R_0 = 1688\Omega$; $X_1 = 0.092\Omega$; $X_2 = 1.34\Omega$; $X_0 = 256\Omega$:
 The transformer is supplying full load at a power factor of 0.8 lagging. Using the equivalent circuit, find the input current. (10 marks)
- b) A 3 ϕ , 230V, 27kVA, 0.9p.f (lag) load is supplied by three 10kVA, 1330/230V, 60Hz transformers connected in Y- Δ by means of a common 3 ϕ feeder whose impedance is $0.003 + j0.015\Omega$ per phase. The transformers are supplied from a 3 ϕ source through a 3 ϕ feeder whose impedance is $0.8 + j5.0\Omega$ per phase. The equivalent impedance of one transformer referred to the low-voltage side is $0.12 + j0.25 \Omega$. Determine the required supply voltage if the load voltage is 230V. (10 marks)

QUESTION FIVE (20MARKS)

- Derive the equation of the developed torque in a dc machine. (10 marks)
- Give the names of two types of induction motors based on their rotor structure. (1 mark)
- A three phase, 460V, 100hp, 60Hz, 6-pole induction machine operates at 3% slip (positive) at full load.
 - Determine the speeds of the motor and its direction relative to the rotating field. (2 marks)
 - Determine the rotor frequency (1 mark)
 - Determine the speed of the stator field. (1 mark)
 - Determine the speed of the rotating airgap field. (1 mark)
 - Determine the speed of the rotor relative to
 - The rotor structure. (1 mark)

- II. The stator structure (1 mark)
- III. The stator rotating field (1 mark)