



MACHAKOS UNIVERSITY

University Examination 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS ENGINEERING)

EEE 204: CIRCUIT THEORY II

DATE: 20/5/2019

TIME: 8.30-10.30 AM

INSTRUCTIONS

Answer Question ONE and any other TWO Questions.

Show calculations where applicable

QUESTION ONE (30 MARKS) (COMPULSORY)

- a) Find the forced response for the voltage (v_f) in Fig.Q1a). when $R = 5\text{ k}\Omega$, $C = 100\text{ }\mu\text{F}$ and $i = 2t\text{ mA}$. (6 marks)


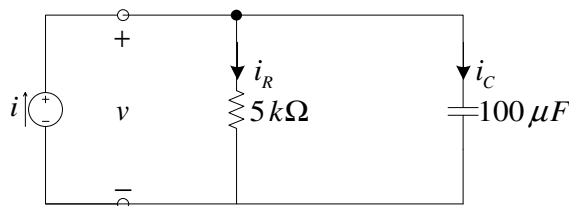


Fig. Q1a)

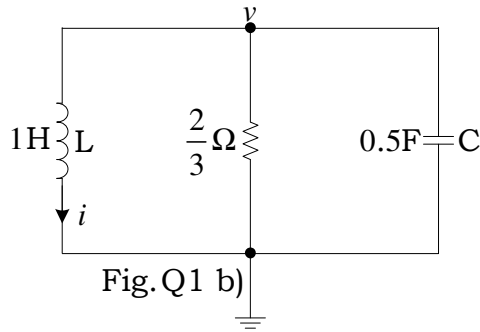- b) Find the natural response of $v(t)$ for $t > 0$ for the parallel RLC circuit shown in Fig.Q1 b) given that $v(0) = 10\text{ V}$ and $i(0) = 2\text{ A}$. (8 marks)



- c) A parallel circuit with quality factor 120 has a resonance frequency of 6×10^6 rad/s . Calculate the bandwidth and half-power frequencies. (6 marks)
- d) Find $i(t)$ for the circuit shown in Fig. Q1 d) when $v_c(0) = 10\text{V}$ and $i(0) = 0$ using Laplace transform method. (10 marks)

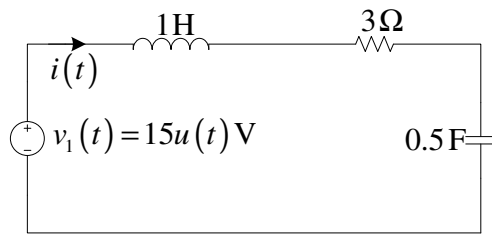



Fig. Q1 d)

QUESTION TWO (20 MARKS)


- a) A delta connected three phase load has a resistance of 15Ω and an inductive reactance of 30Ω in each phase. It is fed from a 400 V 3 phase balanced supply. Find
- the line current
 - total amperes
 - active power
 - reactive power
 - Draw phasor diagram showing phase voltages, line voltages and currents.
- (14 marks)
- b) A series-connected circuit has $R = 4\Omega$ and $L = 25\text{mH}$.
- Calculate the value of C that will produce a quality factor of 50
 - Find ω_1, ω_2 and BW
- (6 marks)

QUESTION THREE (20 MARKS)

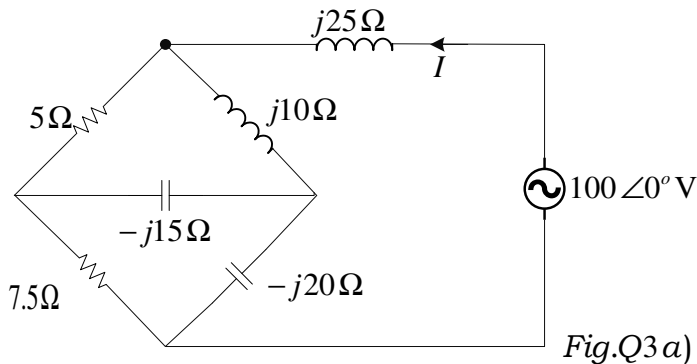
- a) In the circuit shown below, find
- The total circuit impedance
 - The current supplied by the source
 - The apparent power of the circuit
 - The active power of the circuit
- (10 marks)



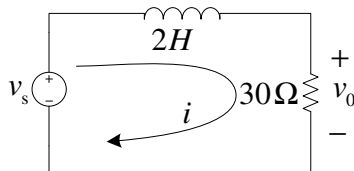- b) The input to the circuit shown in Fig. Q3 b) is the source voltage v_s , and the response is the mesh current i . What are the values of the gain and phase shift when the input frequency is $\omega = 20\text{ rad/s}$?
- (5 marks)



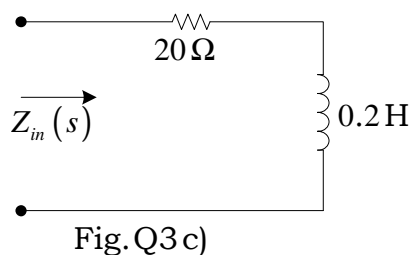- c) Obtain the Bode plot of the input impedance of the network shown in Fig. Q3 c).
- (5 marks)



QUESTION FOUR (20 MARKS)

- a) For the circuit shown in Fig. Q4 a), find the complete response of the circuit given that $i(t) = 0$ for $t < 0$ and that $v(t) = 200\sin 240t$ V for $t > 0$. (12 marks)

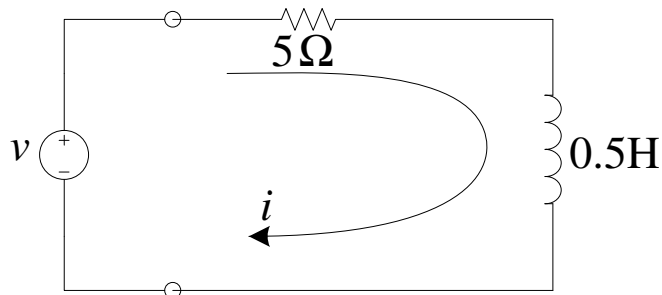


Fig.Q4 a)

- b) Find v_{in} , i_1 , and i_2 in Fig. Q4 b) under dc steady-state conditions with $i_{in} = 2$ A. Then calculate the total stored energy when $L = 5$ mH and $C = 25$ μ F. (5 marks)

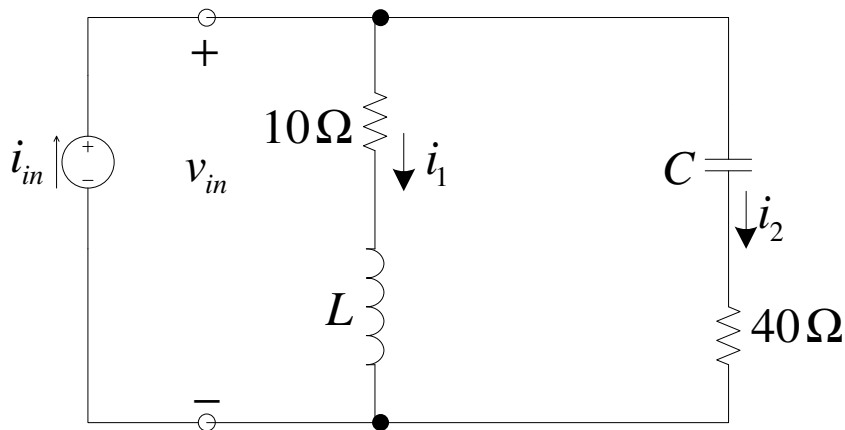


Fig. Q4 b)

- c) Explain the following terms as used in circuit theory:
- Natural response
 - Dynamic circuit
- (3 marks)

QUESTION FIVE (20 MARKS)

- a) Using Fourier transform, determine and plot the spectrum of the response $V_o(\omega)$ of the circuit of Fig.Q5 a) when $v(t) = 10e^{-2t}u(t)$ V

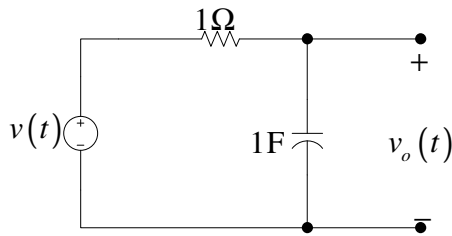


Fig. Q5 a)

(8 marks)

- b) A 3 phase balanced star connected load is connected to a 240 V 3 phase supply. The total volt amperes are 6000 VA and total active power is 4800 W. Find
- Power factor
 - Line current
 - Phase current
 - Resistance and reactance of load in each phase
- (6 marks)
- c) It is expected that a parallel resonant circuit has a mid-band admittance of 25×10^3 S, quality factor of 80, and a resonant frequency of $200 \text{ krad} / \text{s}$. Calculate the value of R, L, and C. Find the bandwidth and the half-power frequencies.
- (6 marks)