



MACHAKOS UNIVERSITY

University Examinations for 2022/2023

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

FIRST YEAR FIRST SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (COMPUTER SCIENCE)

SCO 106: ELECTRONICS

DATE:

TIME:

INSTRUCTIONS:

Answer question one and any other two questions

QUESTION ONE (COMPULSARY) (30 MARKS)

- a) Outline the two main classification of electronic components, giving examples in each case (4 marks)
- b) A resistor with an electrical resistance value of $10\ \Omega$ is connected to another with a resistance value of $20\ \Omega$. The two resistors are connected in parallel. What is the total resistance across the network (2 marks)
- c) With the aid of circuit diagrams, differentiate between forward biased and reverse biased connection of general purpose p-n junction diode (4 marks)
- d) Convert the following numbers:
 - i. 300_{10} into the binary number system (2 marks)
 - ii. 100111_2 into the decimal number system (2 marks)
 - iii. 4320_{10} into the octal number system (2 marks)
 - iv. 1010111100_2 to the hexadecimal system (4 marks)
- e) With the aid of a circuit diagram and a truth table, explain the operation of a NOT-gate (5 marks)
- f) Outline three applications of electronic component (3 marks)
- g) Differentiate between a word and a byte (2 marks)

QUESTION TWO (20 MARKS)

- a) From the Boolean expression $F = A\bar{B} + \bar{A}B$, realize a logical circuit of an XOR-gate (3 marks)
- b) Minimize the Boolean expression, $F = ABC\bar{C} + A\bar{B}\bar{C} + B\bar{C}$ and implement using basic logic gates the minimized expression (6 marks)
- c) Compare asynchronous and synchronous counters using logical block diagram (4 marks)
- d) Design a 3-bit synchronous up-counter using J-K flip flops (7 marks)

QUESTION THREE (20 MARKS)

- a) Implement and show the truth table of a multiplication operation equivalence using a network of a resistor, light emitting diode, a transistor and power source (5 marks)
- b) Describe the operation of a half adder circuit with two variables A and B, showing the possible outputs on a truth table (6 marks)
- c) Given two binary numbers 10111 and 110001, perform binary addition (2 marks)
- d) Define combinational logic circuit as used in digital electronics (1 mark)
- e) Design a digital logic circuit that takes 1-bit A and 1-bit B, returning a sum bit S and a carry out bit C as outputs. The design should include:
 - i) Truth table
 - ii) Logic functions
 - iii) Circuit symbols (6 marks)

QUESTION FOUR (20 MARKS)

- a) Construct an OR-gate using two NPN bipolar junction transistors, showing its truth table (5 marks)
- b) Differentiate between combinational and sequential logic circuits (4 marks)
- c) Minimize the following Boolean function using Karnaugh map method
 $F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$ (6 marks)
- d) With the aid of diagrams, explain the difference between forward bias diode and reverse bias diode (4 marks)
- e) With reference to sequential circuits, define flip flop (1 mark)

QUESTION FIVE (20 MARKS)

- a) With reference to memories, differentiate between ROM and RAM (2 marks)
- b) Using Boolean algebra properties, minimize the Boolean expression
 $F = \overline{A}\overline{B}(A + C) + \overline{A}B(A + B + \overline{C})$ and implement the minimized expression using basic logic gates (6 marks)
- c) With the help of a logic circuit explain the operation of S-R flip flop (6 marks)
- d) Design and implement a 2-to-4 decoder with basic logic gates, showing the truth table (6 marks)