



MACHAKOS UNIVERSITY

University Examinations 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF BUILDING AND CIVIL ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION FOR DEGREE IN
BACHELOR OF SCIENCE IN CIVIL ENGINEERING

ECV 211: ELECTROMECHANICAL ENGINEERING

DATE: 20/6/2017

TIME: 8:30 – 10:30 AM

INSTRUCTIONS

- This paper comprises of **five** questions
- Question **one** is **compulsory** and carry 30 marks
- Answer any **other two** questions

QUESTION ONE (COMPULSORY) (30 MARKS)

Explain the following terms

- | | | | |
|------|-----------------|------|-----------------------------------|
| i | Current | ix | Parallel arrangement of resistors |
| ii | Voltage | x | Series arrangement of resistor |
| iii | Resistance | xi | Parallel circuit |
| iv | Joule's law | xii | Series circuit |
| v | Ohm's law | xiii | Direct current, D.C |
| vi | Impedance | xiv | Alternating current, A.C |
| vii | Admittance | xv | Step-up and step-down transformer |
| viii | Kirchoff's laws | | |

(30 marks)


QUESTION TWO (20 MARKS)

- a) In Kenya the domestic supply of electricity is 240V stepped down from the national grid. Find the peak voltage values V_0 . Why would you consider this more dangerous than a d.c supply of an equivalent voltage? (8 marks)

- b) Domestic supply for country B is 220V. The frequency is 50Hz. Calculate the periodic time? If an appliance of 20 ohms is used, calculate the mean power? (4 marks)
- c) Prove the following in alternating current supply. (8 marks)
- $I_{\text{mean}} = 0.637I_0$
 - $I_{\text{rms}} = 0.707I_0$

QUESTION THREE (20 MARKS)

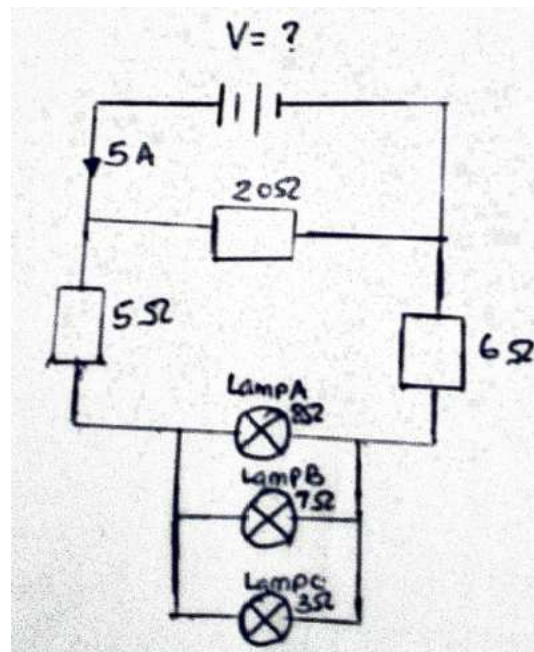- a) Calculate the voltage V across the cell in the diagram below. (10 marks)



- b) If the cell had an internal resistance of 2 ohms repeat a). Find the emf and the p.d across the cell. Are the e.m.f and p.d across the cell equal? Justify. Would the lamps A, B and C light brighter or not? Justify. (10 marks)

QUESTION FOUR (20 MARKS)

- a) Distinguish between 3 phase A.C and single phase A.C (4 marks)
- b) What are the advantages of 3-phase A.C (6 marks)
- c) Describe the components and the working of a hot wire ammeter. What advantage does this ammeter have over ordinary ammeters? (10 marks)

QUESTION FIVE (20 MARKS)

- a) Differentiate between macerator equipment and garchery systems (8 marks)
- b) Describe how electrical systems are useful in lifts, excavators, air conditioning and Refrigeration. (12 marks)