



MACHAKOS UNIVERSITY

University Examinations for 2016/2017

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

FOURTH YEAR FIRST SEMESTER EXAMINATION FOR BACHELOR OF SCIENCE
IN ELECTRICAL AND ELECTRONICS ENGINEERING

EEE 403: ANALOGUE ELECTRONICS III

DATE: 12/6/2017


TIME: 2 HOURS

INSTRUCTIONS

Answer Question One and Any Other Two Questions

QUESTION ONE (COMPULSORY) (30 MARKS)

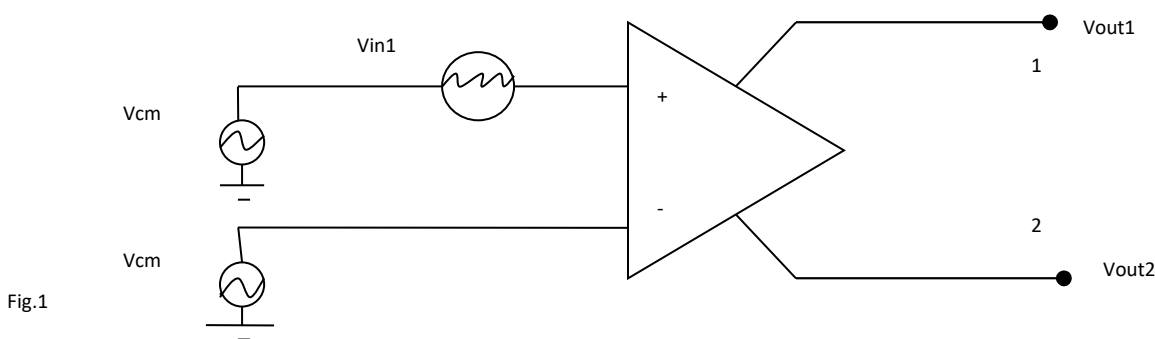
- a) With aid of a well labeled diagram derive the expression of output voltage of a current to voltage converter using OPAMP. (4 marks)
- b) The differential amplifier shown in fig.1 has differential voltage gain of 2500 and CMRR of 30000. A single ended input signal of $500\mu\text{V}$ rms is applied. At the same time, 1 volt, 50Hz interference signal appears on both inputs and as a result radiated pick-up from the a.c. power system.
 - i. Determine the common mode gain.
 - ii. Express CMRR in dB.
 - iii. Determine the rms output signal on output terminal.
 - iv. Determine the rms interference voltage on the output. (8 marks)



- c) Derive the transfer function of a difference amplifier. (5 marks)
- d) With aid of a diagram derive the output expression of diode based op amp antilog circuit. (3 marks)
- e) Determine the maximum rate of change in volts per microsecond of the following signals:
 - (i) $v = 10\sin 4000t$ volts
 - (ii) $v = 5\sin 2\pi 1000t$ volts (4 marks)
- f) With aid of labeled diagrams, describe the working of voltage clampers and voltage clippers. (6 marks)

Question 2 (20 marks)

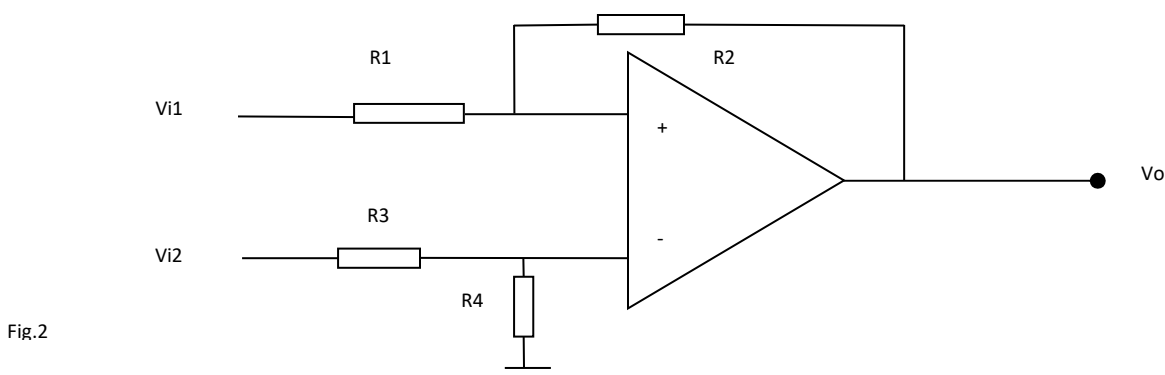
- a) With aid of a well labeled diagram, derive the expression of load current of a voltage to current converter using OPAMP. (4 marks)
- b) Briefly discuss the importance of common mode rejection ratio (CMRR). (3 marks)




- c) Calculate the common mode rejection ratio (CMRR) of the difference amplifier given in fig.2, given $(R2/R1) = 12$ and $(R4/R3) = 15$. (6 marks)
- d) With aid of a labeled diagram, derive the expression of a log amplifier using OPAMP and a diode. (4 marks)
- e) Derive the output expression of an ideal active integrator. (3 marks)

QUESTION THREE (20 MARKS)

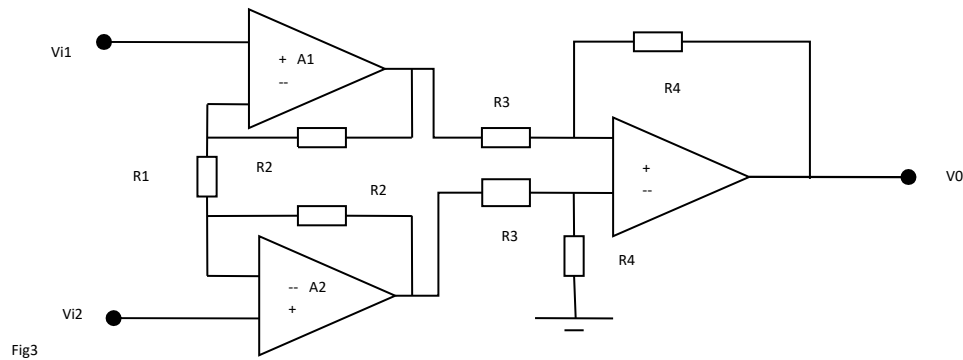- a) Define slew rate. (2 marks)
- b) Briefly discuss the advantages of instrument amplifiers in comparison with difference amplifiers. (3 marks)
- c) Instrumentation amplifier in fig.3 is fabricated using ideal OPAMPs. $R_1=25K\Omega$, $R_2=120K\Omega$, $R_3=60K\Omega$ and $R_4=240K\Omega$. The input voltages are $v_{i2} = 0.6 + 0.04\sin\omega t$ and $v_{i1} = 0.6 - 0.04\sin\omega t$. Determine:
- V_{o1}
 - V_{o2}
 - V_o
- (9 marks)




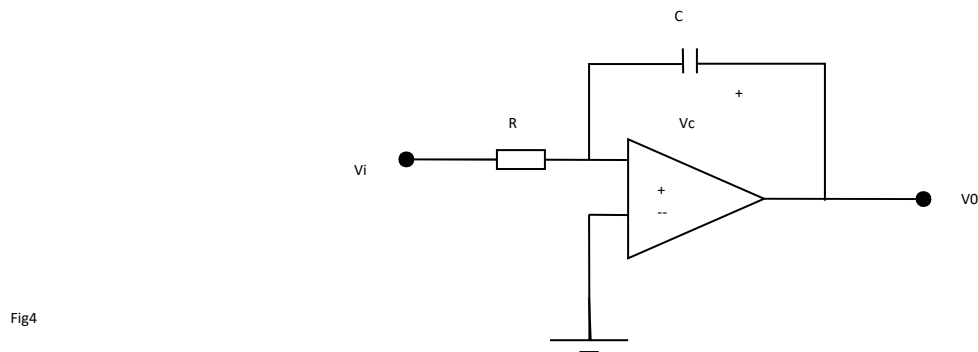- d) The circuit in fig.4 is an active integrator. $V_C=0$ at $t=0$. A step input of $V_i=-2$ is applied at $t=0$. Determine the time constant such that the output reaches $+20$ volts at $t=2mS$. (6 marks)



QUESTION FOUR (20 MARKS)

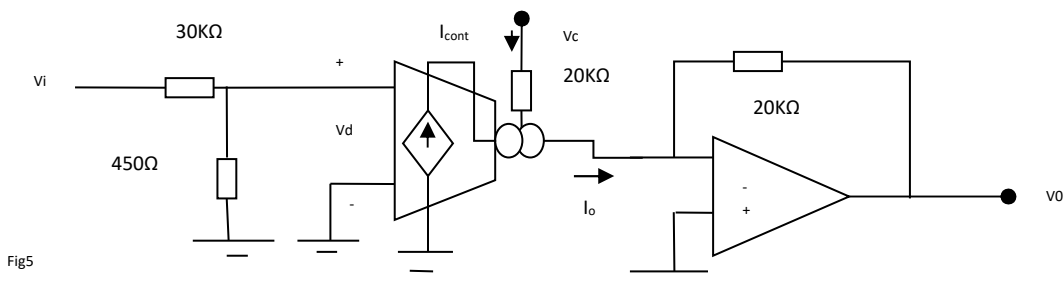
- a) Describe an operational transconductance amplifier (OTA). (2 marks)
- b) The circuit in fig.5 is a voltage controlled voltage amplifier using an OTA. Given temperature dependent voltage $V_T=0.026$ at room temperature and v_c is 10 volts, determine the voltage gain $A_v=V_o/V_i$. (8 marks)



- c) State four characteristics of ideal Opamp. (4 marks)
- d) With aid of diagram derive the expression Wien-bridge based opamp sine wave generator. (6 marks)

QUESTION FIVE (20 MARKS)

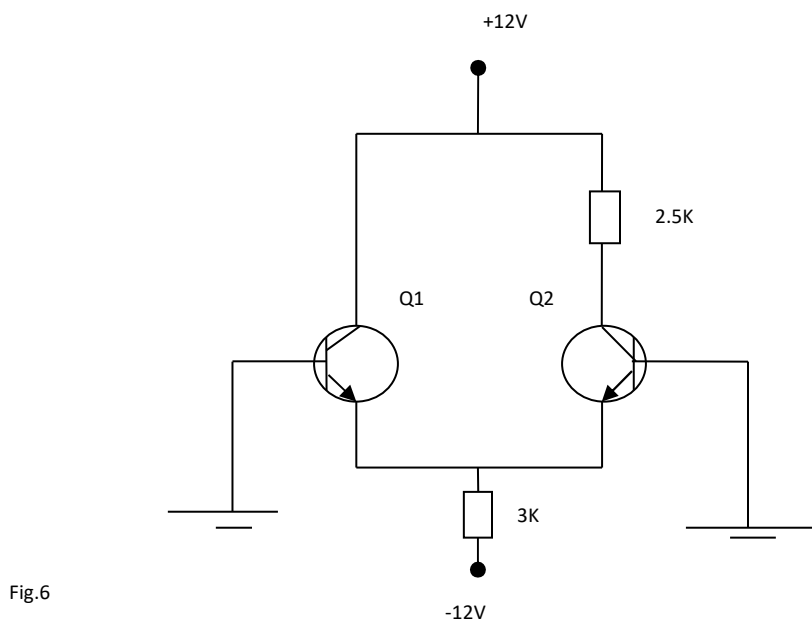- a) Sketch a typical opamp magnitude Bode plot. (2 marks)
- b) With aid of diagrams show how logarithmic multiplier and logarithmic divider performs arithmetic multiplication and division. (8 marks)
- c) Determine the values of I_{C1} , I_{C2} , V_{CE1} and V_{CE2} for the circuit in fig.6. (6 marks)



- d) With aid of a diagram explain how a sample and hold opamp circuit works. (4 marks)