



MACHAKOS UNIVERSITY

University Examinations for 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF COMPUTING AND INFORMATION TECHNOLOGY

FIRST YEAR SPECIAL/SUPPLEMENTARY EXAMINATION FOR
BACHELOR OF SCIENCE (INFORMATION TECHNOLOGY)

SIT 107: INTRODUCTION TO DIGITAL ELECTRONICS

DATE:

TIME:

INSTRUCTIONS

Answer **question ONE** and any other **TWO** questions.

QUESTION ONE (30 MARKS) (COMPULSORY)

- a) Discuss common logic hazards including relevant diagrams and symbols (10 marks)
- b) Minimize the function and realize it using minimum number of gates.
 $F = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$ (8 marks)
- c) Explain common types of counters (6 marks)
- d) Using block diagrams, explain operations of the following logic circuits
 - i. 8-to-3 line Encoder (3 marks)
 - ii. 1 x 4 Demultiplexer (3 marks)

QUESTION TWO (20 MARKS)

- a) Implement a circuit that takes four inputs and outputs a one(1) when any two of the inputs are both ones(1) or three zeros (0). (10 marks)
- b) Discuss Full Adder (4 marks)
- c) Flip flop triggering (6 marks)

QUESTION THREE (20 MARKS)

- a) Perform the binary arithmetic $18.75_{10} - A9_{16}$ (6 marks)
- b) Discuss the conversion of SR into JK flip flop (8 marks)
- c) Compare SRAM and DRAM capacitor (6 marks)

QUESTION FOUR (20 MARKS)

- a) Discuss the ROM (6 marks)
- b) Design 3 Mod counters using J-K Flip Flop and implement it (8 marks)
- c) Discuss boolean algebra laws (6 marks)

QUESTION FIVE (20 MARKS)

- a) A student is taking a project on traffic light. In his display he would like to use a seven segment display. Using relevant diagrams explain how this would be achieved (10 marks)
- b) Explain the working of a Shift-register (6 marks)
- c) Using circuit symbols, truth tables, and boolean expressions, describe NOR gate (4 marks)