



MACHAKOS UNIVERSITY

University Examinations for 2020/2021

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

FIRST YEAR SECOND SEMESTER EXAMINATION FOR

DIPLOMA MODULE I (POWER & TELECOMMUNICATION)

ELECTRICAL ENGINEERING PRINCIPLES

DATE: 1/9/2021

TIME: 2.30-5.30 PM

INSTRUCTIONS TO CANDIDATES:

ATTEMPT ALL QUESTIONS

1.
 - (a) State the Kirchhoff's Laws (4 marks)
 - (b) A coil of $20\ \Omega$ resistance is joined in parallel with a coil of $R\ \Omega$ resistance. This combination is then joined in series with an apparatus A, and the whole circuit is connected to a 120V source. Determine;
 - (i) The value of R so that apparatus A shall dissipate 500 Watts with a current of 10 amperes passing through it.
 - (ii) Energy supplied if the circuit is operated for 2 minutes. (7 marks)
 - (c) Three resistors of $6\ \Omega$, $9\ \Omega$ and $15\ \Omega$ are connected in parallel to a 12 Vdc supply. Determine the:
 - (i) Total effective resistance of the network;
 - (ii) Supply current;
 - (iii) Current in each branch of the circuit. (9 marks)
2.
 - (a) State Superposition theorem (3 marks)
 - (b) Figure 1 shows an electrical network. Determine the values of currents I_1 , I_2 and I_3 by using each of the following methods
 - (i) Kirchhoff's laws
 - (ii) Superposition theorem

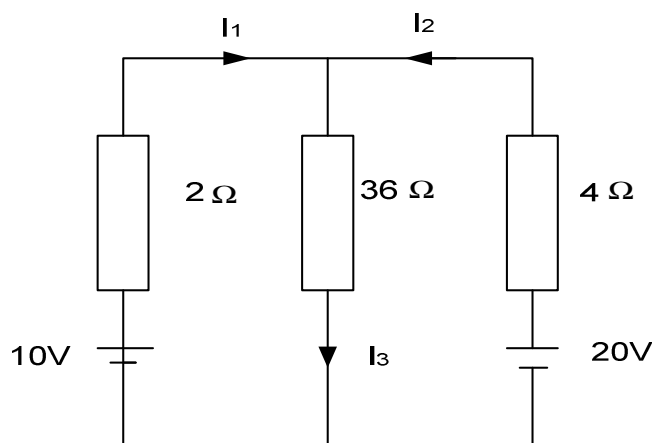


Fig 1

(17 marks)

3. (a) Define the following terms with respect to electrostatics;
 - (i) Capacitance
 - (ii) Dielectric (2 marks)
- (b) A capacitor consists of two parallel metal plates, each of area 200 cm^2 and 5.0 mm apart. The space between the plates is filled with a layer of paper 2.0 mm thick and a sheet of glass 3.0 mm thick. The relative permittivities of the paper and glass are 2 and 8 respectively. A potential difference of 5 kV is applied between the plates. Calculate the:
 - (i) capacitance of the capacitor;
 - (ii) potential gradient in each dielectric in kV/mm ;
 - (iii) total energy stored in the capacitor (14 marks)
- (c) A $20 \mu\text{F}$ capacitor is charged at a constant current of $5 \mu\text{A}$ for 10 min . Calculate the:
 - (i) corresponding charge in coulombs ;
 - (ii) final p.d. across the capacitor. (4 marks)
4. (a) Three capacitors of values $12 \mu\text{F}$, $8 \mu\text{F}$ and $2 \mu\text{F}$ are connected in series across a of 24 V dc source. Determine the:
 - (i) capacitance of the combination;
 - (ii) charge on the $8 \mu\text{F}$ capacitor;
 - (iii) voltage across the $2 \mu\text{F}$ capacitor.
 - (iv) energy stored in the $2 \mu\text{F}$ capacitor. (10 marks)
- (b) A capacitor consists of two parallel plates each of area 750 mm^2 and 5 mm apart. The space between the plates is filled with a sheet of glass with relative permittivity

8. A potential difference of 5kV is applied between the plates. Given absolute permittivity as 8.85×10^{-12} F/m. Calculate the :

- (i) capacitance of the capacitor
- (ii) charge
- (iii) electric flux density
- (iv) potential gradient in kV/mm in the dielectric
- (v) total energy stored in the capacitor (10 marks)

5. (a) State five properties of lines of magnetic flux (5 marks)
- (b) A conductor 2 meters long carrying a current of 0.5 amperes is placed in a magnetic field of 0.5 wb/m^2 . Determine the force exerted on the conductor. (4 marks)
- (c) State the Faraday's electromagnetic laws (6 marks)
- (d) State five applications of magnets. (5 marks)