



# MACHAKOS UNIVERSITY

University Examination 2018/2019

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (MECHANICAL ENGINEERING)

EMM 300: ENGINEERING ELECTRONICS

DATE: 16/5/2019

TIME: 8.30-10.30 AM

---

## INSTRUCTIONS

Answer Question ONE and any other TWO Questions.

### QUESTION ONE (30 MARKS)

- a) i Design a four-resistor bias network for an *npn* transistor to give  $I_C = 10 \mu\text{A}$  and  $V_{CE} = 6 \text{ V}$  if  $V_{CC} = 18 \text{ V}$  and  $\beta_F = 75$ .
- ii. Replace your exact values with the nearest values from the resistor table in Appendix and find the resulting Q-point. (10 marks)
- b) Derive the relationship between base current amplification factor  $\beta$  and emitter current amplification factor  $\alpha$ . (6 marks)
- i. State the two types of complement for a number system whose radix = r.
- ii. Find the 2's complement of the decimal number 1/16.
- ii. Determine the nine's complement of the decimal number 25.638? [7 marks]
- c) For the network of Fig.Q1 (c)
- i. Determine  $I_{CQ}$  and  $V_{CEQ}$ ;
- ii. Find  $V_B$ ,  $V_C$ ,  $V_E$  and  $V_{BC}$ .

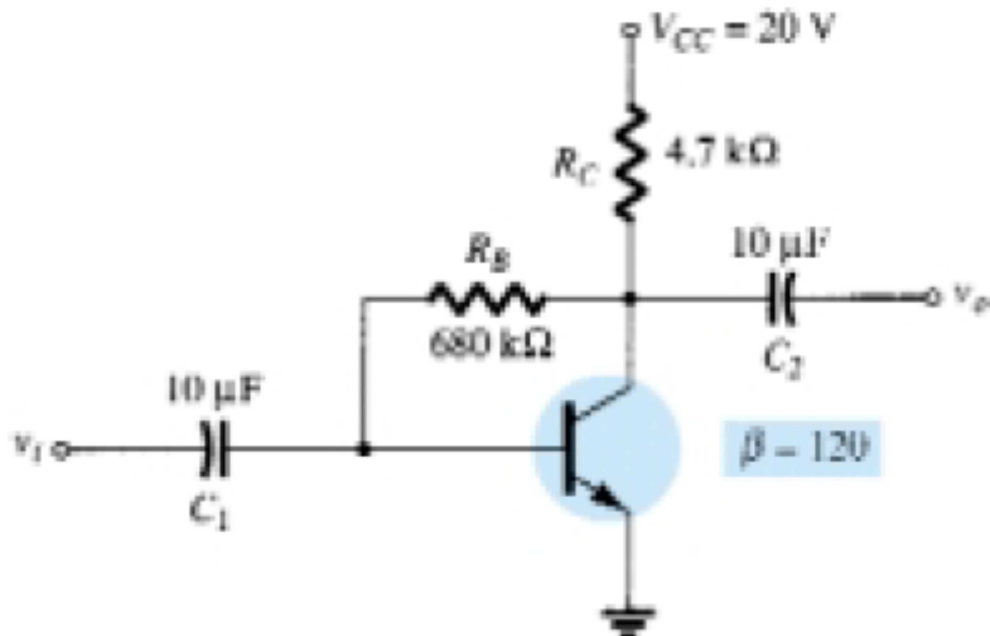


Fig.Q1 (c)

(7

marks)

## QUESTION TWO (20 MARKS)

- a) Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for the voltage-divider configuration of Fig.Q2 (a).

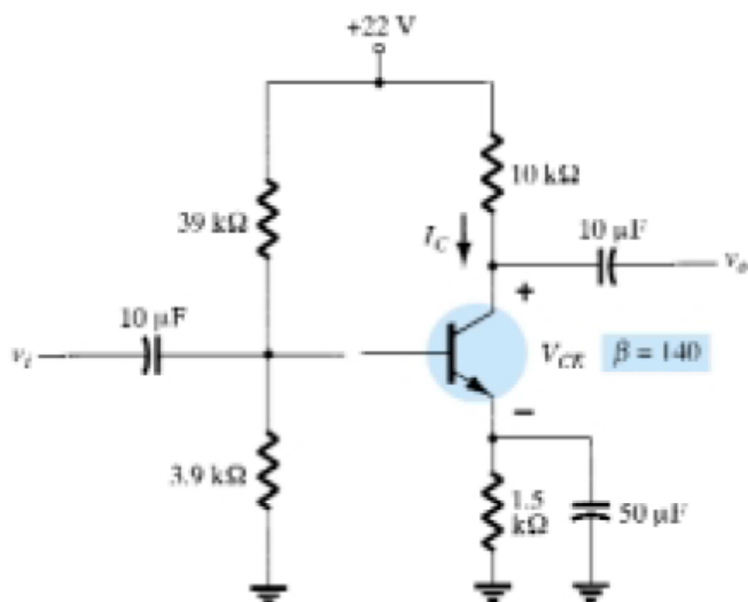


Fig.Q2 (a).

(8

marks)

- b) The parameters of the zener diode for the voltage regulator of the circuit of Fig. Q2 (b) are  $V_Z = 4.7 \text{ V}$  at test current  $I_{ZT} = 53 \text{ mA}$ ,  $R_Z = 8 \Omega$ , and  $R_{ZK} = 500 \Omega$  at  $I_{ZK} = 1 \text{ mA}$ . The supply voltage  $v_S = V_S = 12 \pm 2 \text{ V}$ , and  $R_S = 220 \Omega$ .
- Find the nominal value of the output voltage  $v_O$  under no-load condition  $R_L = \infty$ ;
  - Find the maximum and minimum value of the output voltage for a load resistance  $R_L = 470 \Omega$ ;
  - Find the nominal value of the output voltage  $v_O$  for a load resistance  $R_L = 100 \Omega$ ;
  - Find the minimum value of  $R_L$  for which the zener diode operates in the breakdown region.

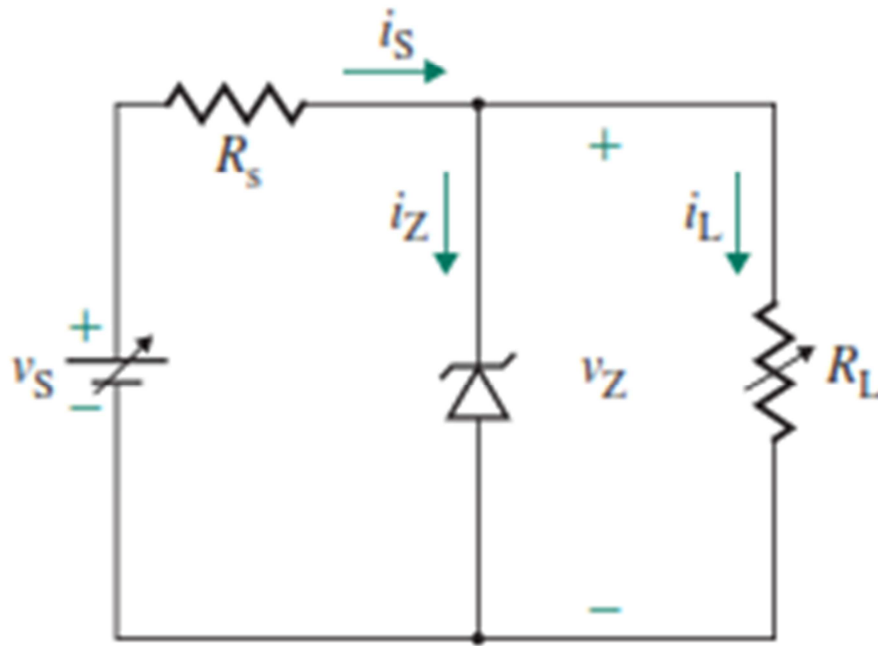



Fig.Q2 (b)

(12

marks)

### QUESTION THREE (20 MARKS)

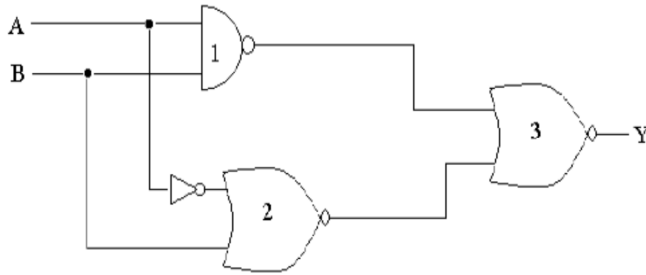a) Find the Boolean expression for the logic circuit in FigQ3 (a).



FigQ3 (a)

(6

marks)

b) A single-phase rectifier can be employed as a battery charger, as shown in Fig. Q3 (b). The battery capacity is 100 Wh, and the battery voltage is  $E = 12$  V. The average charging current should be  $I_{o(av)} = 5$  A. The primary AC input voltage is  $V_p = 120$  V (rms), 60 Hz, and the transformer has a turns ratio of  $n = 2:1$ .

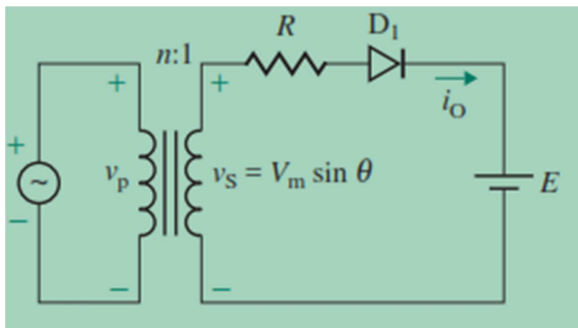


Fig.Q3 (b).

Calculate

- the angle  $\delta$  over which the diode conducts;
- The current limiting resistance  $R$ ;
- The power rating  $P_R$  of the resistance  $R$ ;
- The charging time  $h$  in hours;
- the rectifier efficiency  $\eta_R$ ;

- vi. The peak inverse voltage PIV of the diode. (14 marks)

#### QUESTION FOUR (20 MARKS)

- a) Consider the ac equivalent circuit of the Hartley oscillator in Fig.Q4 (a)
- Derive the expression for the frequency of oscillation;
  - Determine the condition for sustained oscillations.

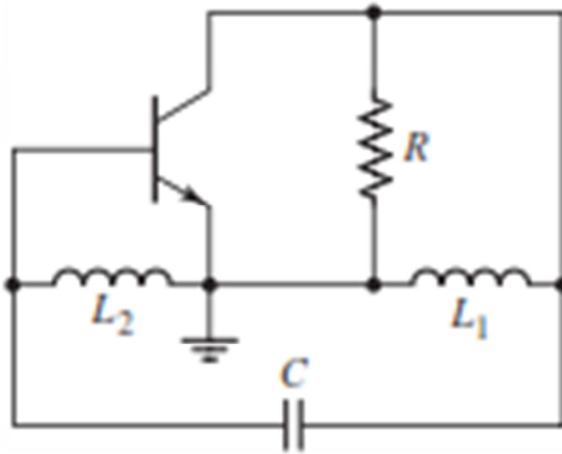



Fig.Q4 (a) (14 marks)

- b) Draw a block diagram of a BCD-to-7 segment decoder indicating the output given that the input is 0101. (6 marks)

#### QUESTION FIVE (20 MARKS)

- a) i Define synchronous counters. (13 marks)
- ii Design a **MODULO-5** synchronous counter using **JK** flip-flops. (7 marks)
- b) Explain how a shift register can be used as a ring counter giving the wave forms at the output of the flip-flops. (7 marks)

## **Appendix**

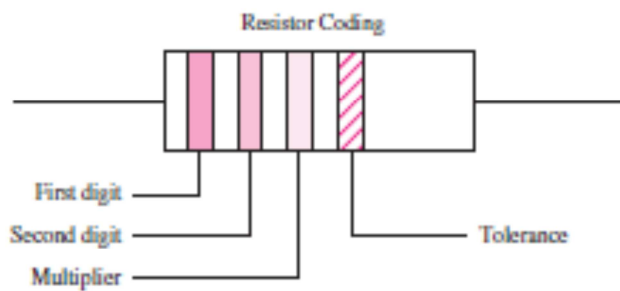

| Resistor Color Code |       |                 |              |
|---------------------|-------|-----------------|--------------|
| COLOR               | DIGIT | MULTIPLIER      | TOLERANCE, % |
| Silver              | ---   | 0.01            | 10           |
| Gold                | ---   | 0.1             | 5            |
| Black               | 0     | 1               |              |
| Brown               | 1     | 10              |              |
| Red                 | 2     | 10 <sup>2</sup> |              |
| Orange              | 3     | 10 <sup>3</sup> |              |
| Yellow              | 4     | 10 <sup>4</sup> |              |
| Green               | 5     | 10 <sup>5</sup> |              |
| Blue                | 6     | 10 <sup>6</sup> |              |
| Violet              | 7     | 10 <sup>7</sup> |              |
| Gray                | 8     | 10 <sup>8</sup> |              |
| White               | 9     | 10 <sup>9</sup> |              |

*Standard resistor values:* All values available with a 5 percent tolerance. Bold values are available with 10 percent tolerance.

| OHMS |            |            |            |             |              |               |               | MEGOHMS |            |
|------|------------|------------|------------|-------------|--------------|---------------|---------------|---------|------------|
| 1.0  | 5.6        | 33         | 180        | 1000        | 5600         | 33000         | 180000        | 1.0     | 5.6        |
| 1.1  | 6.2        | 36         | 200        | 1100        | 6200         | 36000         | 200000        | 1.1     | 6.2        |
| 1.2  | <b>6.8</b> | <b>39</b>  | <b>220</b> | <b>1200</b> | <b>6800</b>  | <b>39000</b>  | <b>220000</b> | 1.2     | <b>6.8</b> |
| 1.3  | 7.5        | 43         | 240        | 1300        | 7500         | 43000         | 240000        | 1.3     | 7.5        |
| 1.5  | <b>8.2</b> | <b>47</b>  | <b>270</b> | <b>1500</b> | <b>8200</b>  | <b>47000</b>  | <b>270000</b> | 1.5     | <b>8.2</b> |
| 1.6  | 9.1        | 51         | 300        | 1600        | 9100         | 51000         | 300000        | 1.6     | 9.1        |
| 1.8  | <b>10</b>  | <b>56</b>  | <b>330</b> | <b>1800</b> | <b>10000</b> | <b>56000</b>  | <b>330000</b> | 1.8     | <b>10</b>  |
| 2.0  | 11         | 62         | 360        | 2000        | 11000        | 62000         | 360000        | 2.0     | 11         |
| 2.2  | <b>12</b>  | <b>68</b>  | <b>390</b> | <b>2200</b> | <b>12000</b> | <b>68000</b>  | <b>390000</b> | 2.2     | <b>12</b>  |
| 2.4  | 13         | 75         | 430        | 2400        | 13000        | 75000         | 430000        | 2.4     | 13         |
| 2.7  | <b>15</b>  | <b>82</b>  | <b>470</b> | <b>2700</b> | <b>15000</b> | <b>82000</b>  | <b>470000</b> | 2.7     | <b>15</b>  |
| 3.0  | 16         | 91         | 510        | 3000        | 16000        | 91000         | 510000        | 3.0     | 16         |
| 3.3  | <b>18</b>  | <b>100</b> | <b>560</b> | <b>3300</b> | <b>18000</b> | <b>100000</b> | <b>560000</b> | 3.3     | <b>18</b>  |
| 3.6  | 20         | 110        | 620        | 3600        | 20000        | 110000        | 620000        | 3.6     | 20         |
| 3.9  | <b>22</b>  | <b>120</b> | <b>680</b> | <b>3900</b> | <b>22000</b> | <b>120000</b> | <b>680000</b> | 3.9     | <b>22</b>  |
| 4.3  | 24         | 130        | 750        | 4300        | 24000        | 130000        | 750000        | 4.3     |            |
| 4.7  | <b>27</b>  | <b>150</b> | <b>820</b> | <b>4700</b> | <b>27000</b> | <b>150000</b> | <b>820000</b> | 4.7     |            |
| 5.1  | 30         | 160        | 910        | 5100        | 30000        | 160000        | 910000        | 5.1     |            |

| PRECISION (±%) RESISTORS |      |      |      |     |     |     |       |       |       |       |       |       |       |       |      |      |       |
|--------------------------|------|------|------|-----|-----|-----|-------|-------|-------|-------|-------|-------|-------|-------|------|------|-------|
| 10.0                     | 19.1 | 36.5 | 69.8 | 133 | 255 | 487 | 931   | 1.78K | 3.40K | 6.49K | 12.4K | 23.7K | 45.3K | 84.5K | 158K | 294K | 549K  |
| 10.2                     | 19.6 | 37.4 | 71.5 | 137 | 261 | 499 | 953   | 1.82K | 3.48K | 6.65K | 12.7K | 24.3K | 46.4K | 86.6K | 162K | 301K | 562K  |
| 10.5                     | 20.0 | 38.3 | 73.2 | 140 | 267 | 511 | 976   | 1.87K | 3.57K | 6.81K | 13.0K | 24.9K | 47.5K | 88.7K | 165K | 309K | 576K  |
| 10.7                     | 20.5 | 39.2 | 75.0 | 143 | 274 | 523 | 1.00K | 1.91K | 3.65K | 6.98K | 13.3K | 25.5K | 48.7K | 90.9K | 169K | 316K | 590K  |
| 11.0                     | 21.0 | 40.2 | 76.8 | 147 | 280 | 536 | 1.02K | 1.96K | 3.74K | 7.15K | 13.7K | 26.1K | 49.9K | 93.1K | 174K | 324K | 604K  |
| 11.3                     | 21.5 | 41.2 | 78.7 | 150 | 287 | 549 | 1.05K | 2.00K | 3.83K | 7.32K | 14.0K | 26.7K | 51.1K | 95.3K | 178K | 332K | 619K  |
| 11.5                     | 22.1 | 42.2 | 80.6 | 154 | 294 | 562 | 1.07K | 2.05K | 3.92K | 7.50K | 14.3K | 27.4K | 52.3K | 97.6K | 182K | 340K | 634K  |
| 11.8                     | 22.6 | 43.2 | 82.5 | 158 | 301 | 576 | 1.10K | 2.10K | 4.02K | 7.68K | 14.7K | 28.0K | 53.6K | 100K  | 187K | 348K | 649K  |
| 12.1                     | 23.2 | 44.2 | 84.5 | 162 | 309 | 590 | 1.13K | 2.15K | 4.12K | 7.87K | 15.0K | 28.7K | 54.9K | 102K  | 191K | 357K | 665K  |
| 12.4                     | 23.7 | 45.3 | 86.6 | 165 | 316 | 604 | 1.15K | 2.21K | 4.22K | 8.06K | 15.4K | 29.4K | 56.2K | 105K  | 196K | 365K | 681K  |
| 12.7                     | 24.3 | 46.4 | 88.7 | 169 | 324 | 619 | 1.18K | 2.26K | 4.32K | 8.25K | 15.8K | 30.1K | 57.6K | 107K  | 200K | 374K | 698K  |
| 13.0                     | 24.9 | 47.5 | 90.9 | 174 | 332 | 634 | 1.21K | 2.32K | 4.42K | 8.45K | 16.2K | 30.9K | 59.0K | 110K  | 205K | 383K | 715K  |
| 13.3                     | 25.5 | 48.7 | 93.1 | 178 | 340 | 649 | 1.24K | 2.37K | 4.53K | 8.66K | 16.5K | 31.6K | 60.4K | 113K  | 210K | 392K | 732K  |
| 13.7                     | 26.1 | 49.9 | 95.3 | 182 | 348 | 665 | 1.27K | 2.43K | 4.64K | 8.87K | 16.9K | 32.4K | 61.9K | 115K  | 215K | 402K | 750K  |
| 14.0                     | 26.7 | 51.1 | 97.6 | 187 | 357 | 681 | 1.30K | 2.49K | 4.75K | 9.09K | 17.4K | 33.2K | 63.4K | 118K  | 221K | 412K | 768K  |
| 14.3                     | 27.4 | 52.3 | 100  | 191 | 365 | 698 | 1.33K | 2.55K | 4.87K | 9.31K | 17.8K | 34.0K | 64.9K | 121K  | 226K | 422K | 787K  |
| 14.7                     | 28.0 | 53.6 | 102  | 196 | 374 | 715 | 1.37K | 2.61K | 4.99K | 9.53K | 18.2K | 34.8K | 66.5K | 124K  | 232K | 432K | 806K  |
| 15.0                     | 28.8 | 54.9 | 105  | 200 | 383 | 732 | 1.40K | 2.67K | 5.11K | 9.76K | 18.7K | 35.7K | 68.1K | 127K  | 237K | 442K | 825K  |
| 15.4                     | 29.4 | 56.2 | 107  | 205 | 392 | 750 | 1.43K | 2.74K | 5.23K | 10.0K | 19.1K | 36.5K | 69.8K | 130K  | 243K | 453K | 845K  |
| 15.8                     | 30.1 | 57.6 | 110  | 210 | 402 | 768 | 1.47K | 2.80K | 5.36K | 10.2K | 19.6K | 37.4K | 71.5K | 133K  | 249K | 464K | 866K  |
| 16.2                     | 30.9 | 59.0 | 113  | 215 | 412 | 787 | 1.50K | 2.87K | 5.49K | 10.5K | 20.0K | 38.3K | 73.2K | 137K  | 255K | 475K | 887K  |
| 16.5                     | 31.6 | 60.4 | 115  | 221 | 422 | 806 | 1.54K | 2.94K | 5.62K | 10.7K | 20.5K | 39.2K | 75.0K | 140K  | 261K | 487K | 909K  |
| 16.9                     | 32.4 | 61.9 | 118  | 226 | 432 | 825 | 1.58K | 3.01K | 5.76K | 11.0K | 21.0K | 40.2K | 76.8K | 143K  | 267K | 499K | 931K  |
| 17.4                     | 33.2 | 63.4 | 121  | 232 | 443 | 845 | 1.62K | 3.09K | 5.90K | 11.3K | 21.5K | 41.2K | 78.7K | 147K  | 274K | 511K | 953K  |
| 17.8                     | 34.0 | 64.9 | 124  | 237 | 453 | 866 | 1.65K | 3.16K | 6.04K | 11.5K | 22.1K | 42.2K | 80.6K | 150K  | 280K | 523K | 976K  |
| 18.2                     | 34.8 | 66.5 | 127  | 243 | 464 | 887 | 1.69K | 3.24K | 6.19K | 11.8K | 22.6K | 43.2K | 82.5K | 154K  | 287K | 536K | 1.00M |
| 18.7                     | 35.7 | 68.1 | 130  | 249 | 475 | 909 | 1.74K | 3.32K | 6.34K | 12.1K | 23.2K | 44.2K |       |       |      |      |       |