

MACHAKOS UNIVERSITY

ISO 9001:2008 Certified 

University Examination for 2015/2016

**SCHOOL OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
THIRD YEAR SUPPLEMENTARY EXAMINATION FOR BACHELOR OF SCIENCE IN
ELECTRICAL AND ELECTRONICS ENGINEERING**

EEE 305: DIGITAL ELECTRONICS I

DATE: __2017__

TIME: 2 HRS

INSTRUCTIONS.

Answer **QUESTION ONE** and **any other TWO**.


Do **NOT** answer **MORE** than **three** questions.

QUESTION ONE (30 MARKS)

- (a) What is a universal gate? Give examples. Realize the basic gates (AND, OR, NOT gates) with NAND gate. (8mks)
- (b) When simplified with Boolean Algebra $(x + y)(x + z)$ simplifies to? (3mks)
- (c) What is the decimal equivalent of Binary number 110101101? (2mk)
- (d) For the function below, write the truth table, then simplify using Karnaugh map and realize the function using NAND gates only. $F = A.B.C + B.C.\overline{D} + \overline{A}.B.C$ (7mks)
- (e) Convert the octal number 7401 to Binary. (3mks)
- (f) With the help of a suitable diagram, explain how you convert a JK flip flop to T type flip flop. Also draw the excitation tables of both flip flops. (7mks)

QUESTION TWO (20 MARKS)

 - (a) Find the Boolean expression for logic circuit shown in Fig.1 below and reduce it using Boolean algebra. (5mks)



- (b) Perform 2's complement subtraction of the following: $(7)_{10} - (11)_{10}$ (3mks)
- (c) Draw the circuit diagram of a Master-slave J-K flip-flop using NAND gates. What is race around condition? How is it eliminated in a Master-slave J-K flip-flop? (5mks)
- (d) Simplify the following expression into sum of products using Karnaugh map:

$$F(A, B, C, D) = \sum (1, 3, 4, 5, 6, 7, 9, 12, 13)$$
 (7mks)

QUESTION THREE (20 MARKS)

- (a) Simplify using Boolean algebra and draw the combinational logic diagram for the given expression:

$$F = \overline{A}BC + \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}C$$
 (7mks)

- (b) Distinguish between combinational logic circuits and sequential logic circuits. How are the design requirements of combinational circuits specified? (4mks)
- (c) Distinguish between min terms and max terms. (3mks)
- (d) Prove the following Boolean identities using the laws of Boolean algebra: (6mks)

(i) $(A + B)(A + C) = A + BC$

(ii) $ABC + A\overline{B}C + A\overline{B}\overline{C} = A(B + C)$

QUESTION FOUR (20 MARKS)

- (a) Perform the following operations using the 2's complement method: (7mks)


(i) $23 - 48$

(ii) $-48 - 23$

- (b) The Karnaugh map for a SOP function is given below in Fig below. Determine the simplified SOP Boolean expression. (4mks)

		CD →			
		00	01	11	10
AB ↓	00	1	1		1
	01		1		
	11				
	10	1	1		1

 (c) Find the reduced Boolean expression for the logic circuit shown below using Boolean algebra .
(4mks)



(d) Reduce the following equation using k-map. (5mks)

$$Y = B\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}D + \bar{A}BCD + ABCD$$


QUESTION FIVE (20 MARKS)

(a) What is a flip-flop? What is the difference between a latch and a flip-flop? List out the application of flip-flop. (4mks)

(b) Give the truth table of S-R and D-flip flops. Convert the given S-R flip flop to a D-flip flop. (5mks)

 (c) The voltage waveforms shown in Fig. below are applied at the inputs of 2-input AND and OR gates.

Determine the output waveforms for each. (6mks)



(d) What are the advantages of CMOS logic? Explain CMOS Inverter with the help of a neat circuit diagram.
(5mks)