



# MACHAKOS UNIVERSITY

University Examinations 2017/2018

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

SECOND YEAR SECOND SEMESTER EXAMINATION DIPLOMA IN  
ELECTRICAL ENGINEERING

EED 215: DIGITAL ELECTRONICS II

DATE: 18/12/2017

TIME: 8:30 – 10:30 AM

## INSTRUCTIONS:

*This paper consists of **FIVE** Questions. Answer Question ONE and ANY OTHER TWO questions.*

### QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Simplify the Boolean expression below (4 marks)
- b) Distinguish between combinational logic circuits and sequential logic circuits. (6 marks)
- c) How are the design requirements of combinational and sequential circuits specified? (8 marks)
- d) Reduce the following equation using k-map (6 marks)  
$$Y = \overline{A}BC + A\overline{C}D + A\overline{B} + ABCD + \overline{A}BC$$
- e) Implement the following SOP function using NAND gate only  $F = XZ + Y'Z + X'YZ$  (6 marks)

### QUESTION TWO (20 MARKS)


- a) What is a decoder? (2 marks)
- b) Draw the logic circuit of a 3 line to 8 line decoder and explain its working (10 marks)
- c) What is a shift register? Can a shift register be used as a counter? If yes, explain how? (8 marks)

### QUESTION THREE

- a) With the aid of a diagram, explain the working of a Clocked SR Flip-Flop (8 marks)
- b) Storage components store data and perform simple data transformations, explain the following components (6 marks)
- i. Register:
  - ii. Counter:
  - iii. Memory unit:
- c) Draw the logic circuit of a 3 line to 8 line decoder and explain its working. (6 marks)

### QUESTION FOUR (20 MARKS)

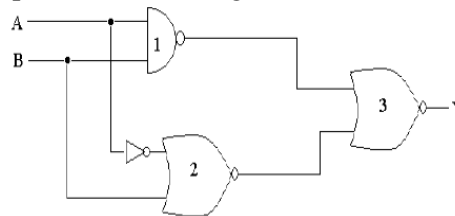- a) With the aid of a logic circuit of a TTL NAND gate briefly explain its operation. (10 marks)
- b) Find the Boolean expression for the logic circuit shown below. (5 marks)



- c. What is the equivalent of the following Boolean Expression? (5 marks)
- $$\overline{A}.B + A.\overline{B} + A.B$$

### QUESTION FIVE (20 MARKS)

- a) What is Tri-state logic (2 marks)
- b) Explain Tri-state logic inverter with the help of a circuit diagram. (8 marks)
- c) Provide the Tri-state logic Truth Table. (6 marks)
- d) Simplify the following boolean expression (4 marks)

$$(\overline{A}\overline{B}\overline{C}) + (\overline{A}\overline{B}C)$$