



MACHAKOS UNIVERSITY

University Examinations for 2021/2022

SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

THIRD YEAR SECOND SEMESTER EXAMINATION FOR

BACHELOR OF SCIENCE (ELECTRICAL AND ELECTRONICS
ENGINEERING)

EEE 309: ANALOGUE ELECTRONIC II

DATE: 17/12/2021

TIME: 11:00 – 1:00 PM


INSTRUCTIONS

Answer question **ONE** and **ANY OTHER TWO** questions

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) Design a 4-resistor bias circuit for a BJT amplifier with the following parameters: $I_C = 750 \mu A$, $V_{CE} = 5 V$, $\beta = 100$, $V_{CC} = 15 V$, $V_{BE} = 0.7 V$. (10 marks)
- b) A transistor used in common emitter configuration has the following set of h parameters when d.c. operating point is $V_{CE} = 5 V$ and $I_C = 1 mA$. $H_{ie} = 1700 \Omega$; $h_{re} = 1.3 \times 10^{-4}$; $h_{fe} = 48$; $h_{oe} = 9 \times 10^{-6}$ siemens and a.c load as seen by the transistor is $r_L = 2 K\Omega$. Determine:
- Input impedance;
 - Current gain;
 - Voltage gain. (6 marks)
- c) i. A power transistor has thermal resistance $\theta = 300 ^\circ C/W$. If the maximum junction temperature is $95 ^\circ C$ and the ambient temperature is $35 ^\circ C$, determine the maximum permissible power dissipation.
- ii. If a heat sink is used with the above transistor, the value of θ is reduced to $65 ^\circ C/W$. Calculate the maximum permissible power dissipation.

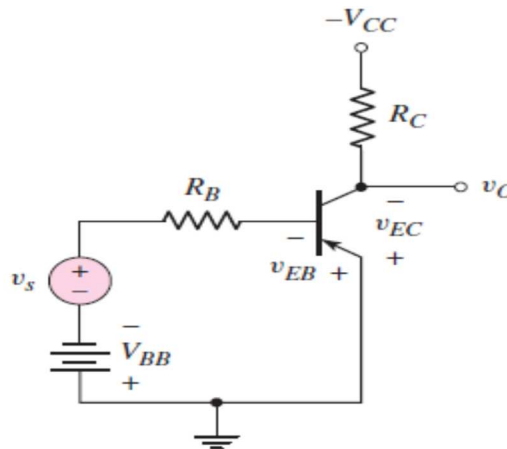- d) For the circuit in Fig.Q1 (d), $\beta = 100$, $V_A = \infty$, $V_{CC} = 10\text{ V}$, $R_B = 50\text{ k}\Omega$.
- Determine V_{BB} and R_C such that $I_{CQ} = 0.5\text{ mA}$ and the Q-point is the center of the load line;
 - Find the small-signal parameters g_m , r_π , and r_o ;
 - Determine the small-signal voltage gain $A_v = v_o/v_s$.



(8 marks)

- e) An amplifier has an open-loop gain of 1000 and a feedback ratio of 0.04. If the open-loop gain changes by 10% due to temperature, find the percentage change in gain of the amplifier with feedback. (2 marks)

QUESTION TWO (20 MARKS)

- a) i. An inverting amplifier with resistors $R_1 = 5.6\text{ k}\Omega$ and $R_2 = 120\text{ k}\Omega$ is fabricated using an op-amp with an open-loop gain of 10^5 . Determine the percentage difference between the actual gain and the ideal gain.
- ii. A non-inverting amplifier with resistors $R_1 = 6.8\text{ k}\Omega$ and $R_2 = 47\text{ k}\Omega$ is fabricated using an op-amp with an open-loop gain of 2×10^4 . Determine the percentage difference between the actual gain and the ideal gain. (10 marks)

- b) i. The circuit in Fig.Q2 (b) is a first – order low-pass active filter. Show that the voltage transfer function is given by

$$A_v = \frac{-R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

- What is the voltage gain at dc ($\omega = 0$)?
- At what frequency is the magnitude of the voltage gain a factor of $\sqrt{2}$ less than the dc value? (This is the – 3 dB frequency)

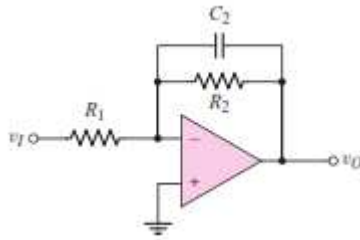


Fig.Q2 (b)

(10 marks)

QUESTION THREE (20 MARKS)

- a) Derive the expression for the resonance frequency of the Phase Shift oscillator shown in Fig.Q3 (a).

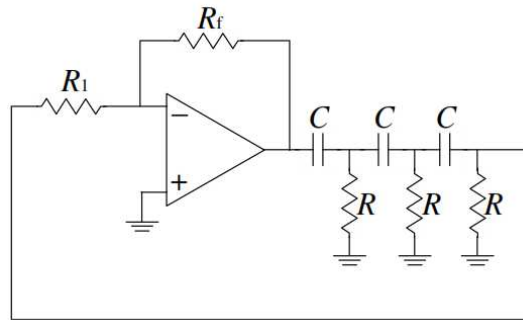


Fig.Q3 (a).

(12 marks)

- b) i. The tuned collector oscillator circuit used in the local oscillator of a radio receiver makes use of an LC tuned circuit with $L_1 = 58.6 \mu\text{H}$ and $C_1 = 300 \text{ pF}$. Calculate the frequency of oscillations;
- ii. Find the capacitance of the capacitor required to build an LC oscillator that uses an inductance of $L_1 = 1 \text{ mH}$ to produce a sine wave of frequency 1 GHz ;
- iii. A Colpitt's oscillator has the following parameters: capacitance $C_1 = 0.001 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$ and inductor $L = 15 \mu\text{H}$. Determine the operating frequency and the feedback fraction for the oscillator.

(8 marks)

QUESTION FOUR (20 MARKS)

- a) An amplifier has a mid-band gain of 125 and a bandwidth of 250 kHz.
- If 4% negative feedback is introduced, find the new bandwidth and gain;
 - If the is to be restricted to 1 MHz, find the feedback ratio. (6 marks)
- b) An amplifier has a voltage gain with feedback is 100.If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, determine the values of the open loop gain A and feedback ratio β . (6 marks)
- c) An voltage – series negative feedback amplifier has a voltage gain without feedback $A = 500$, input resistance $R_i = 3 \text{ k}\Omega$, output resistance $R_o = 20 \text{ k}\Omega$ and feedback ratio $\beta = 0.01$. Determine
- The a voltage gain with feedback A_f ;
 - The input resistance with feedback R_{if} ;
 - The output resistance with feedback R_{of} . (6 marks)
- d) Explain the term positive feedback. (2 marks)

QUESTION FIVE (20 MARKS)

- a) Explain the following terms:
- Miller effect;
 - Cutoff frequency;
 - Cascode configuration. (6 marks)
- b) For the common-emitter circuit in Fig.Q5 (a), assume the emitter bypass capacitor C_E is very large, and the transistor parameters are: $\beta_o = 100$ $V_{BE}(\text{on}) = 0.7\text{V}$, $V_A = 8$, $C_\mu = 2\text{pF}$, and $f_T = 400\text{MHz}$. Determine the lower and upper 3 dB frequencies for the small-signal voltage gain. Use the simplified hybrid model for the transistor.

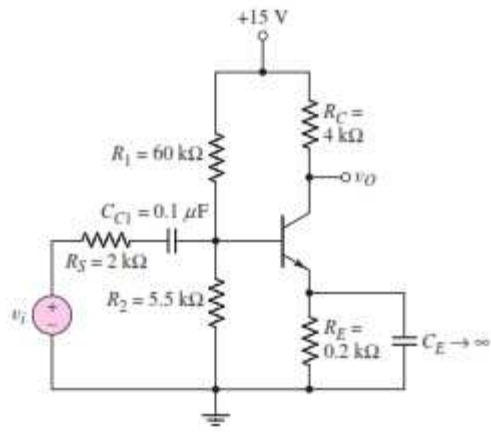


Fig.Q5 (a)

(14 marks)